

CHAPTER 10.7

ATTENUATORS

Arthur B. Williams, Fred, J. Taylor

ATTENUATOR NETWORK DESIGN

Attenuators are passive circuits that introduce a fixed power loss between a source and load while matching impedances. The power loss is independent of the direction of power flow. Figure 10.7.1 shows T , Π , and bridged- T networks. The first two are unbalanced and unsymmetrical, unless $Z_L = Z_S$. In this case, $Z_1 = Z_2$, and the network is symmetrical. To build an unbalanced network, divide Z_1 and Z_2 by 2, and put half of each element in each series arm. The bridged- T shown is only for symmetrical networks.

These design equations are valid for resistive and complex impedances.

$$\begin{aligned}
 Z_S &= \text{source impedance} \\
 Z_L &= \text{load impedance} \\
 A &= \text{ratio of available power to desired load power (dB)} = 10^{B/10} \\
 B &= 10 \log A \\
 \theta &= 1/2 \ln A = 1/2 \ln 10^{B/10}
 \end{aligned} \tag{1}$$

As an example, design an attenuator to match a 75- Ω source to a 300- Ω load and to introduce a 14.0-dB loss. Use a T section. In terms of Eq. (1),

$$\begin{aligned}
 Z_s = 75 \Omega & & Z_L = 300 \Omega & & B = 14.0 \text{ dB} & & A = 25.12 \\
 \theta = 1.612 & & Z_3 = 62.34 \Omega & & Z_1 = 18.88 \Omega & & Z_2 = 262.54 \Omega
 \end{aligned}$$

Figure 10.7.2 shows the network.

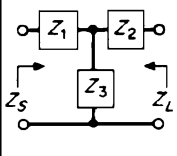
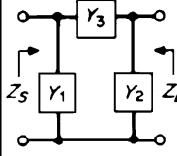
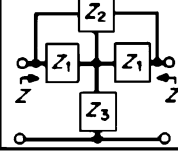
Circuit name	Circuit diagram	Equations
T-Network		$Z_3 = \sqrt{Z_s Z_L} / \sinh \theta = \frac{2\sqrt{Z_s Z_L} \cdot A}{A-1}$ $Z_1 = Z_s \coth \theta - Z_3 = Z_s \left(\frac{A+1}{A-1} \right) - Z_3$ $Z_2 = Z_L \coth \theta - Z_3 = Z_L \left(\frac{A+1}{A-1} \right) - Z_3$
π -Network		$Y_3 = \frac{1}{\sqrt{Z_s Z_L} \sinh \theta}$ $= \frac{2}{A-1} \sqrt{\frac{A}{Z_s Z_L}}$ $Y_1 = \frac{\tanh \theta}{Z_s} - Y_3 = \frac{1}{Z_s} \left(\frac{A+1}{A-1} \right) - Y_3$ $Y_2 = \frac{\tanh \theta}{Z_L} - Y_3 = \frac{1}{Z_L} \left(\frac{A+1}{A-1} \right) - Y_3$
Bridged-T		$Z_1 = Z$ $Z_2 = Z(A-1)$ $Z_3 = \frac{Z}{A-1}$

FIGURE 10.7.1 Attenuator networks and equations.

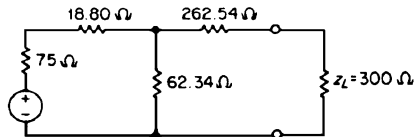


FIGURE 10.7.2 A 14.0-dB attenuator between a 75- Ω source and a 300- Ω load.