

# SECTION 11

# AMPLIFIERS AND OSCILLATORS

Amplifiers serve a number of purposes from allowing us to hear beautiful music to accurately positioning elements of complicated systems using control technologies. Oscillators are found in a number of applications from the watch on your wrist to the transmitter and receiver in your cell phone. We look at audio-frequency amplifiers and oscillators and radio-frequency amplifiers and oscillators.

The most versatile amplifier has to be the operational amplifier (op amp). The key to its success is that it is perhaps the most ideal device in analog electronics. Because of this it is found in a number of amplifier designs.

High-power amplifiers are necessary where significant amounts of power need to be used to accomplish activities such as radio and television broadcasts. Just imagine what a rock concert might sound like without power amplifiers. Microwave amplifiers and oscillators represent a special part of the high-power amplifier and oscillator field. C.A.

## **In This Section:**

<b>CHAPTER 11.1 AMPLIFIER AND OSCILLATOR PRINCIPLES OF OPERATION</b>	<b>11.5</b>
AMPLIFIERS: PRINCIPLES OF OPERATION	11.5
OSCILLATORS: PRINCIPLES OF OPERATION	11.14
<b>CHAPTER 11.2 AUDIO-FREQUENCY AMPLIFIERS AND OSCILLATORS</b>	<b>11.18</b>
AUDIO-FREQUENCY AMPLIFIERS	11.18
AUDIO OSCILLATORS	11.25
<b>CHAPTER 11.3 RADIO-FREQUENCY AMPLIFIERS AND OSCILLATORS</b>	<b>11.35</b>
RADIO-FREQUENCY AMPLIFIERS	11.35
RADIO-FREQUENCY OSCILLATORS	11.43
BROADBAND AMPLIFIERS	11.47
TUNNEL-DIODE AMPLIFIERS	11.60
PARAMETRIC AMPLIFIERS	11.64
MASER AMPLIFIERS	11.66
ACOUSTIC AMPLIFIERS	11.70
MAGNETIC AMPLIFIERS	11.79
<b>CHAPTER 11.4 OPERATIONAL AMPLIFIERS</b>	<b>11.87</b>
DIRECT-COUPLED AMPLIFIERS	11.87
OPERATIONAL AMPLIFIERS FOR ANALOG ARITHMETIC	11.93
LOW-NOISE OPERATIONAL AMPLIFIERS	11.97
POWER OPERATIONAL AMPLIFIERS	11.99

<b>CHAPTER 11.5 HIGH-POWER AMPLIFIERS</b>	<b>11.102</b>
THERMAL CONSIDERATIONS	11.102
HIGH-POWER BROADCAST-SERVICE AMPLIFIERS	11.102
CLASS B LINEAR RF AMPLIFIERS	11.102
HIGH-EFFICIENCY POWER AMPLIFIERS	11.103
INDUCTION HEATING CIRCUITS	11.103
DIELECTRIC HEATING	11.103
TRANSISTORS IN HIGH-POWER AMPLIFIERS	11.104
MOSFET AUDIO AMPLIFIERS AND SWITCHING APPLICATIONS	11.105
<b>CHAPTER 11.6 MICROWAVE AMPLIFIERS AND OSCILLATORS</b>	<b>11.107</b>
MICROWAVE SOLID-STATE DEVICES	11.107
IMPATT DIODE CIRCUITS	11.107
TRAPATT DIODE CIRCUITS	11.110
BARITT AND DOVETT DIODES	11.112
TRANSFERRED ELECTRON EFFECT DEVICE (TED) CIRCUITS	11.113
TRANSISTOR AMPLIFIER AND OSCILLATOR MICROWAVE CIRCUITS	11.115
NOISE PERFORMANCE OF MICROWAVE BIPOLAR TRANSISTOR CIRCUITS	11.118
HIGH-POWER MICROWAVE TRANSISTOR AMPLIFIERS (USING BIPOLAR TRANSISTORS)	11.119
GaAs FIELD-EFFECT TRANSISTOR CIRCUITS	11.122
NOISE PERFORMANCE OF MICROWAVE FET CIRCUITS	11.122
HIGH ELECTRON MOBILITY TRANSISTORS	11.122
HIGH-POWER MICROWAVE FET AMPLIFIERS	11.122
MONOLITHIC MICROWAVE INTEGRATED CIRCUITS	11.123
TRANSISTOR OSCILLATORS	11.123
TRAVELING-WAVE-TUBE CIRCUITS	11.124
KLYSTRON OSCILLATORS AND AMPLIFIERS	11.126
CROSSED-FIELD-TUBE CIRCUITS	11.127
GYROTRON CIRCUITS	11.128

## Section Bibliography:

### Classic General References

- Bode, H. W., "Network Analysis and Feedback Amplifier Design," Van Nostrand, 1959. (Reprinted 1975 by R. E. Krieger).
- Ghausi, M. S., and D. O. Pederson, "A new approach to feedback amplifiers," *IRE Trans. Circuit Theory*, Vol. CT-4, September 1957.
- Ginzton, E. L., W. R. Hewlett, J. H. Jasberg, and J. D. Noe, "Distributed amplification," *Proc. IRE*, Vol. 20, August 1948.
- Glasford, G. M., "Fundamentals of Television Engineering," McGraw-Hill, 1955.
- Hines, M. E., "High-frequency negative-resistance circuit principles for Esaki diodes," *Bell Syst. Tech. J.*, Vol. 39, May 1960.
- Hutson, A. R., J. H. McFee, and D. L. White, "Ultrasonic amplification in CdS," *Phys. Rev. Lett.*, September 15, 1961.
- Kim, C. S., and A. Brandli, "High frequency high power operation of tunnel diodes," *IRE Trans. Circuit Theory*, December 1962.
- Millman, J., "Vacuum Tube and Semiconductor Electronics," McGraw-Hill, 1958.
- Read, W. T., "A proposal high-frequency negative resistance diode," *Bell Syst. Tech. J.*, Vol. 37, 1958.
- Reich, H. J., "Functional Circuits and Oscillators," Van Nostrand, 1961.
- Seely, S., "Electron Tube Circuits," McGraw-Hill, 1950.
- Shea, R. F. (ed.), "Amplifier Handbook," McGraw-Hill, 1968.
- Singer, J. R., "Masers," Wiley, 1959.
- Storm, H. F., "Magnetic Amplifiers," Wiley, 1955.
- Truxal, J. C., "Automatic Feedback Control System Synthesis," McGraw-Hill, 1955.

**Specific-Topic and Contemporary References**

- Bahl, I. (ed.), "Microwave Solid State Circuit Design," Wiley, 1988.
- Wilson, F. A., "An Introduction to Microwaves," Babani, 1992.
- Blackwell, L. A., and K. L. Kotzebue, "Semiconductor-Diode Parametric Amplifiers," Prentice Hall, 1961.
- Blotekjaer, K., and C. F. Quate, "The coupled modes of acoustic waves and drifting carriers in piezoelectric crystals," *Proc. IEEE*, Vol. 52, No. 4, pp. 360–377, April 1965.
- Cate, T., "Modern techniques of analog multiplication," *Electron. Eng.*, pp. 75–79, April 1970.
- Chang, K. K. N., "Parametric and Tunnel Diodes," Prentice Hall, 1964.
- Coldren, L. A., and G. S. Kino, "Monolithic acoustic surface-wave amplifier," *Appl. Phys. Lett.*, Vol. 18, No. 8, p. 317, 1971.
- Cunningham, D. R., and J. A. Stiller, "Basic Circuit Analysis," Houghton Mifflin, 1991.
- Curtis, F. W., "High-Frequency Induction Heating," McGraw-Hill, 1964.
- Datta, S., "Surface Acoustic Wave Devices," Prentice Hall, Vol. 72, 1986.
- Duenas, J. A., and A. Serrano, "Directional coupler design graphs for parallel coupled lines and interdigitated 3 dB couplers," *RF Design*, pp. 62–64, February 1986.
- Evaluating, Selecting, and Using Multiplier Circuit Modules for Signal Manipulation and Function Generation, Analog Devices, 1970.
- Garmand, P. A., "Complete small size 2 to 30 GHz hybrid distributed amplifier using a novel design technique," *IEEE MTT-S Digest*, pp. 343–346, 1986.
- Hagt, W. H., Jr., and J. E. Kemmerly, "Engineering Circuit Analysis," 5th ed., McGraw-Hill, 1993.
- Helms, H. L., "Contemporary Electronics Circuit Deskbook," McGraw-Hill, 1986.
- Helszajn, J., "Microwave Planar Passive Circuits and Filters," Wiley, 1994.
- Ingebritsen, K. A., "Linear and nonlinear attenuation of acoustic surface waves in a piezoelectric coated with a semiconducting film," *J. Appl. Phys.*, Vol. 41, p. 454, 1970.
- Inglis, A. F., "Video Engineering," McGraw-Hill, 1993.
- Kino, G. S., and T. M. Reeder, "A normal mode theory for the Rayleigh wave amplifier," *IEEE Trans. Electron Devices*, Vol. ED-18, p. 909, 1971.
- Kotelyanski, I. M., A. I. Kribunov, A. V. Edved, R. A. Mishkinis, and V. V. Pantelev, "Fabrication of LiNbO<sub>3</sub>-InSb layer structures and their use in amplification of surface acoustic waves," *Sov. Phys. Semicon*, Vol. 12, No. 7, pp. 751–754, July 1978.
- Kouril, F., "Non-linear and Parametric Circuits: Principles, Theory, and Applications," Chichester/Wiley, 1988.
- Ladbrooke, P. H., "MMIC Design: GaAs FETs and HEMTs," Artech House, 1989.
- Lakin, K. M., and H. J. Shaw, "Surface wave delay line amplifiers," *IEEE Trans. Microwave Theory Techniques*, MTT-17, p. 912, 1969.
- Lange, L., "Interdigitated stripline quadrature hybrid," *IEEE Trans. MTT*, December 1969.
- Liff, A. A., "Color and Black and White Television," Regents/Prentice Hall, 1993.
- Lin, Y., "Ion Beam Sputtered InSb Thin Films and Their Application to Surface Acoustic Wave Amplifiers," Ph.D. Dissertation, Polytechnic University of 1995.
- May, J. E., Jr., "Electronic signal amplification in the UHF range with the ultrasonic traveling wave amplifier," *Proc. IEEE*, Vol. 53, No. 10, October 1965.
- McFee, J. H., "Transmission and amplification of acoustic waves," in: *Physical Acoustics*, Vol. 4A, Academic Press, 1964.
- Middlebrook, R. D., "Differential Amplifiers," Wiley, 1963.
- Mizuta, H., "The Physics and Applications of Resonant Tunneling Diodes," Cambridge University Press, 1995.
- Nelson, J. C. C., "Operational Amplifier Circuits: Analysis and Design," Butterworth-Heinemann, 1995.
- Optical Pumping and Masers, *Appl. Opt.*, Vol. 1, No. 1, January 1962.
- Pauley, R. G., P. G. Asher, J. M. Schellenberg, and H. Yamasaki, "A 2 to 40 GHz monolithic distributed amplifier," *GaAs IC Symp.*, pp. 15–17, November 1985.
- Penfield, P. Jr., and R. P. Rafuse, "Varactor Applications," The MIT Press, 1962.
- Petruzzella, F. D., "Industrial Electronics," Glencoe/McGraw-Hill, 1996.
- "Power Op-amp Handbook," Apex Microtechnology, 85741, 1987.
- Pucel, R. A., "Monolithic Microwave Integrated Circuits," IEEE Press, 1985.

- Robertson, I. D., "MMIC Design," IEE, London, 1995.
- Rutkowski, G. B., "Operational Amplifiers: Integrated and Hybrid Circuits," Wiley, 1993.
- Simpson, C. D., "Industrial Electronics," Prentice Hall, 1996.
- Southgate, P. D., and H. N. Spector, "Effect of carrier trapping on the Weinreich relation in acoustic amplification," *J. Appl. Phys.*, vol. 36, pp. 3728–3730, December 1965.
- Tehon, S. W., "Acoustic wave amplifiers," Chap. 30, *Amplifier Handbook*, McGraw-Hill, 1968.
- Tobey, G. E., L. P. Huelsman, and J. G. Graeme, "Operational Amplifiers," McGraw-Hill, 1971.
- Traister, R. J., "Operational Amplifier Circuit Manual," Academic Press, 1989.
- Viztmuller, P., "RF Design Guide: Systems, Circuits and Equations," Artech House, 1995.
- Wang, W. C., "Strong electroacoustic effect in CdS," *Phys. Rev. Lett.*, Vol. 9, No. 11, pp. 443–445, December 1, 1962.
- Wang, W. C., and Y. Lin, "Acousto-electric Attenuation Determined by Transmission Line Technique," International Workshop on Ultrasonic Application, September 1–3, 1996.
- Wanuga, S., "CW acoustic amplifier," *Proc. IEEE (Corres.)*, Vol. 53, No. 5, p. 555, May 1965.
- White, D. L., "Amplification of ultrasonic waves in piezoelectric semiconductors," *J. Appl. Phys.*, Vol. 33, No. 8, pp. 2547–2554, August 1962.
- White, R. M., "Surface elastic-wave propagation and amplification," *IEEE Trans. Electron Devices*, ED-14, 181 (1967).
- Wilkinson, E. J., "An N-way hybrid power divider," *IRE MTT*, January 1960.
- Wilson, T. G., "Series connected magnetic amplifier with inductive loading," *Trans. AIEE*, Vol. 71, 1952.

# CHAPTER 11.1

## AMPLIFIER AND OSCILLATOR PRINCIPLES OF OPERATION

G. Burton Harrold

### AMPLIFIERS: PRINCIPLES OF OPERATION

#### Gain

In most amplifier applications the prime concern is gain. A generalized amplifier is shown in Fig. 11.1.1. The most widely applied definitions of gain using the quantities defined there are:

$$\text{Voltage gain } A_v = e_{22}/e_{11} \quad \text{Current gain } A_i = i_2/i_1$$

$$\text{Available power from source } P_{\text{avs}} = \frac{|e_s|^2}{4 \operatorname{Re} Z_s} \quad \text{where Re = real part of complex impedance}$$

$$\text{Output load power } P_L = \frac{|e_{22}|^2}{\operatorname{Re} Z_L} \quad \text{Input power } P_I = \frac{|e_{11}|^2}{\operatorname{Re} Z_{\text{in}}}$$

$$\text{Available power at output } P_{\text{avo}} = \frac{|e_{22}|^2}{4 \operatorname{Re} Z_{\text{out}}} \quad \text{Transducer gain } G_T = P_L/P_{\text{avs}}$$

$$\text{Available power gain } G_A = P_{\text{avo}}/P_{\text{avs}} \quad \text{Power gain } G = P_L/P_I$$

$$\text{Insertion power gain } G_I = \frac{\text{power into load with network inserted}}{\text{power into load with source connected to load}}$$

#### Bandwidth and Gain-Bandwidth Product

Bandwidth is a measure of the range of frequencies within which an amplifier will respond. The frequency range (passband) is usually measured between the half-power (3-dB) points on the output-response-versus-frequency curve, for constant input. In some cases it is defined at the quarter-power points (6 dB). See Fig. 11.1.2.

The gain-bandwidth product of a device is a commonly used figure of merit. It is defined for a bandpass amplifier as

$$F_a = A_r B$$

11.6 AMPLIFIERS AND OSCILLATORS

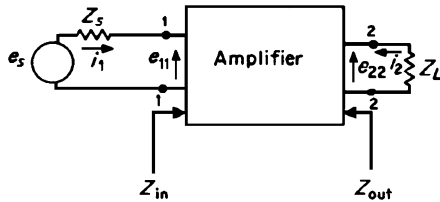


FIGURE 11.1.1 Input and output quantities of generalized amplifier.

where  $F_a$  = figure of merit (rad/s)  
 $A_r$  = reference gain, either the maximum gain or the gain at the frequency where the gain is purely real or purely imaginary  
 $B$  = 3-dB bandwidth (rad/s)

For low-pass amplifiers

$$F_a = A_r W_H$$

where  $F_a$  = figure of merit (rad/s)  
 $A_r$  = reference gain  
 $W_H$  = upper cutoff frequency (rad/s)

In the case of vacuum tubes and certain other active devices this definition is reduced to

$$F_a = g_m / C_T$$

where  $F_a$  = figure of merit (rad/s)  
 $g_m$  = transconductance of active device  
 $C_T$  = total output capacitance, plus input capacitance of subsequent stage

Noise

The major types of noise are illustrated in Fig. 11.1.3. Important relations and definitions in noise computations are:

Noise factor

$$F = \frac{S_i / N_i}{S_o / N_o}$$

where  $S_i$  = signal power available at input  
 $S_o$  = signal power available at output  
 $N_i$  = noise power available at input at  $T = 290$  K  
 $N_o$  = noise power available at output

Available noise power

$$P_{n.av} = \frac{e_n^2}{4R} = KTB \quad \text{for thermal noise}$$

where the quantities are as defined in Fig. 11.1.3.

Excess noise factor

$$F - 1 = N_e / N_i$$

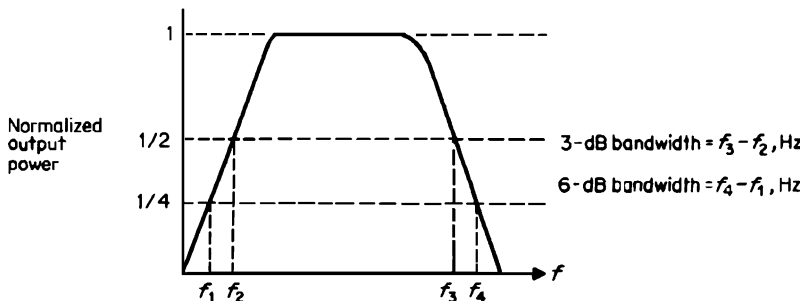


FIGURE 11.1.2 Amplifier response and bandwidth.

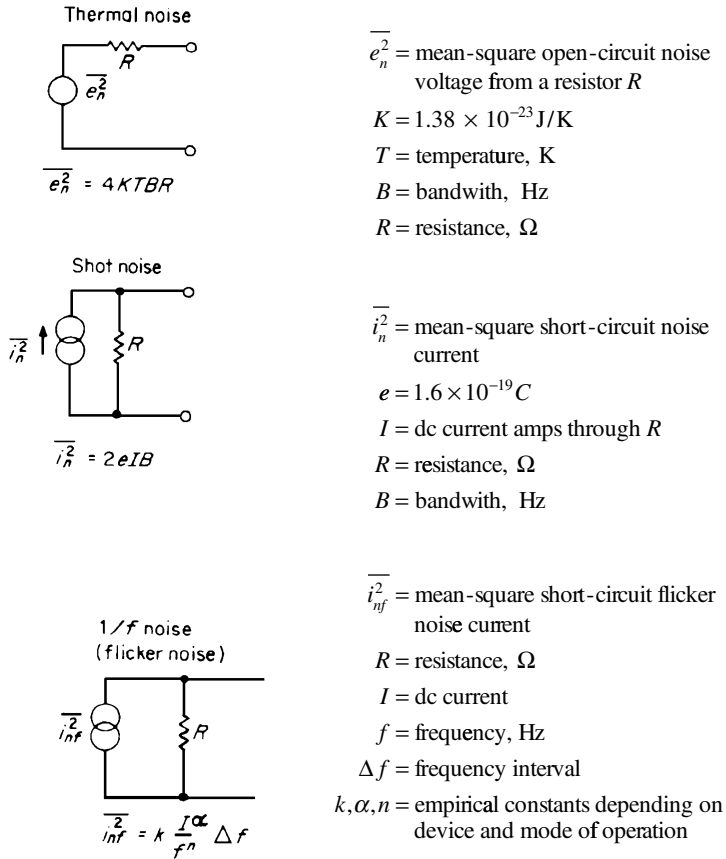


FIGURE 11.1.3 Noise-equivalent circuits.

where  $F - 1$  = excess noise factor

$N_e$  = total equivalent device noise referred to input

$N_i$  = thermal noise of source at standard temperature

Noise temperature

$$T = P_{n,av} / KB$$

where  $P_{n,av}$  is the average noise power available.

At a single input-output frequency in a two-port,

Effective input noise temperature

$$T_e = 290(F - 1)$$

**Noise Factor of Transmission Lines and Attenuators.** The noise factor of two ports composed entirely of resistive elements at room temperature (290 K) and an impedance matched loss of  $L = 1/G_A$  is  $F = L$ .

Cascaded noise factor

$$F_T = F_1 + (F_2 - 1)/G_A$$

11.8 AMPLIFIERS AND OSCILLATORS

where  $F_T$  = overall noise factor  
 $F_1$  = noise factor of first stage  
 $F_2$  = noise factor of second stage  
 $G_A$  = available gain of first stage

**System Noise Temperature.** Space probes and satellite communication systems using low-noise amplifiers and antennas directed toward outer space make use of system noise temperatures. When we define  $T_A$  = antenna temperature,  $L$  = waveguide numeric loss (greater than 1),  $T_{E1}$  = amplifier noise temperature,  $G_A$  = amplifier available gain,  $F$  = postamplifier noise factor, and  $B$  = postamplifier bandwidth, this temperature can be calculated as

$$T_{\text{sys}} = T_A + |L - 1| 290^\circ + LT_{E1} + \frac{(F - 1)(290L)}{G_{A1}}$$

The quantity of interest is the output signal-to-noise ratio where  $S_A$  is available signal power at the antenna (assuming the antenna is matched to free space)

$$S/N = S_A / K T_{\text{sys}} B \quad K = 1.38 \times 10^{-23}$$

**Generalized Noise Factor.** A general representation of noise performances can be expressed in terms of Fig. 11.1.4. This is the representation of a noisy two-port in terms of external voltage and current noise sources with a correlation admittance. In this case the noise factor becomes

$$F = 1 + \frac{G_u}{G_s} - \frac{R_N}{G_s} [(G_s + G_\gamma)^2 + (B_s + B_\gamma)^2]$$

where  $F$  = noise factor  
 $G_s$  = real part of  $Y_s$   
 $B_s$  = imaginary part of  $Y_s$   
 $G_u$  = conductance owing to the uncorrelated part of the noise current  
 $Y_\gamma$  = correlation admittance between cross product of current and voltage noise sources  
 $G_\gamma$  = real part of  $Y_\gamma$   
 $B_\gamma$  = imaginary part of  $Y_\gamma$   
 $R_N$  = equivalent noise resistance of the noise voltage

The optimum source admittance is  $Y_{\text{opt}} = G_{\text{opt}} + jB_{\text{opt}}$

$$G_{\text{opt}} = \left( \frac{G_u + R_N G_\gamma^2}{R_N} \right)^{1/2}$$

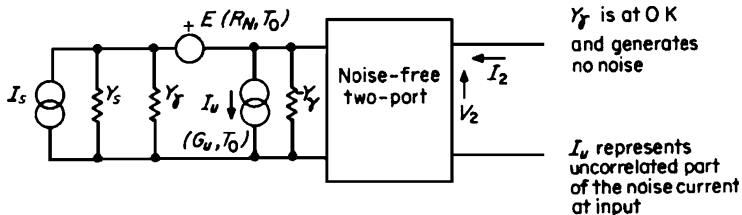


FIGURE 11.1.4 Noise representation using correlation admittance.



where  $B_{\text{opt}} = -B_{\text{gg}}$  and the value of the optimum noise factor  $F_{\text{opt}}$  is

$$F_{\text{opt}} = 1 + 2R_N(G_\gamma + G_0)$$

The noise factor for an arbitrary source impedance is

$$F = F_{\text{opt}} + \frac{R_N}{G_s} [(G_s - G_0)^2 + (B_s - B_0)^2]$$

The values of the parameters of Fig. 11.1.4 can be determined by measurement of (1) noise figure versus  $B_s$  with  $G_s$  constant and (2) noise figure versus  $G_s$  with  $B_s$  at its optimum value.

### Dynamic Characteristic, Load Lines, and Class of Operation

Most active devices have two considerations involved in their operation. The first is the dc bias condition that establishes the operating point (the *quiescent point*). The choice of operating point is determined by such considerations as signal level, uniformity of the device, and temperature of operation.

The second consideration is the ac operating performance, related to the slope of the dc characteristic and to the parasitic reactances of the device. These ac variations give rise to the *small-signal parameters*. The ac parameters may also influence the choice of dc bias point when basic constraints, such as gain and noise performance, are considered.

For frequencies of operation where these parasites are not significant, the use of a load line is valuable. The class of amplifier operation is dependent on its quiescent point, its load line, and input signal level. The types of operation are shown in Fig. 11.1.5.

### Distortion

Distortion takes many forms, most of them undesirable. The basic causes of distortion are nonlinearity in amplitude response and nonuniformity of phase response. The most commonly encountered types of distortion are as follows:

*Harmonic distortion* is a result of nonlinearity in the amplitude transfer characteristics. The typical output contains not only the fundamental frequency but integer multiples of it.

*Crossover distortion* is a result of the nonlinear characteristics of a device when changing operating modes (e.g., in a push-pull amplifier). It occurs when one device is cut off and the second turned on if the crossover is not smooth between the two modes.

*Intermodulation distortion* is a spurious output resulting from the mixing of two or more signals of different frequencies. The spurious output occurs at the sum or difference of integer multiples of the original frequencies.

*Cross-modulation distortion* occurs when two signals pass through an amplifier and the modulation of one is transferred to the other.

*Phase distortion* results from the deviation from a constant slope of the output-phase-versus-frequency response of an amplifier. This deviation gives rise to echo responses in the output that precede and follow the main response, and a distortion of the output signal when an input signal having a large number of frequency components is applied.

### Feedback Amplifiers

Feedback amplifiers fall into two categories: those having positive feedback (usually oscillators) and those having negative feedback. The positive-feedback case is discussed under oscillators. The following discussion is concerned with negative-feedback amplifiers.


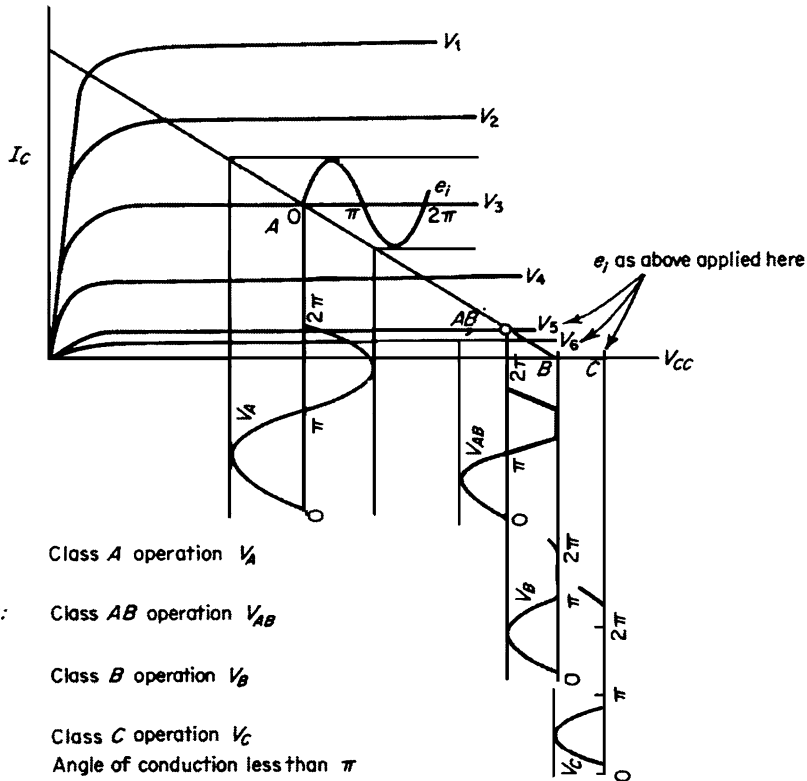


FIGURE 11.1.5 Classes of amplifier operation. Class S operation is a switching mode in which a square-wave output is produced by a sine-wave input.

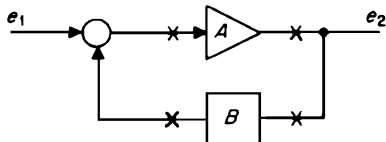**Negative Feedback**

A simple representation of a feedback network is shown in Fig. 11.1.6. The closed-loop gain is given by



$$e_2/e_1 = A/(1 - BA)$$

where  $A$  is the forward gain with feedback removed and  $B$  is the fraction of output returned to input.

For negative feedback,  $A$  provides a  $180^\circ$  phase shift in mid-band, so that

FIGURE 11.1.6 Amplifier with feedback loop.

$$1 - AB > 1 \quad \text{in this frequency range}$$

The quantity  $1 - AB$  is called the *feedback factor*, and if the circuit is cut at any  $X$  point in Fig. 11.1.6, the open-loop gain is  $AB$ .

It can be shown that for large loop gain  $AB$  the closed-loop transfer function reduces to

$$e_2/e_1 \approx 1/B$$

The gain then becomes essentially independent of variations in  $A$ . In particular, if  $B$  is passive, the closed-loop gain is controlled only by passive components. Feedback has no beneficial effect in reducing unwanted signals

at the input of the amplifier, e.g., input noise, but does reduce unwanted signals generated in the amplifier chain (e.g., output distortion).

The return ratio can be found if the circuit is opened at any point  $X$  (Fig. 11.1.6) and a unit signal  $P$  is injected at that  $X$  point. The return signal  $P'$  is equal to the return ratio, since the input  $P$  is unity. In this case the return ratio  $T$  is the same at any point  $X$  and is

$$T = -AB$$

The minus sign is chosen because the typical amplifier has an odd number of phase reversals and  $T$  is then a positive quantity. The return difference is by definition

$$F = 1 + T$$

It has been shown by Bode that

$$F = \Delta / \Delta^0$$

where  $\Delta$  is the network determinant with  $XX$  point connected and  $\Delta^0$  is the network determinant of amplifier when gain of active device is set to zero.

### Stability

The stability of the network can be analyzed by several techniques. Of prime interest are the Nyquist, Bode, Routh, and root-locus techniques of analyzing stability.

**Nyquist Method.** The basic technique of Nyquist involves plotting  $T$  on a polar plot as shown in Fig. 11.1.7 for all values  $s = j\omega$  for  $\omega$  between minus and plus infinity. Stability is then determined by the following method:

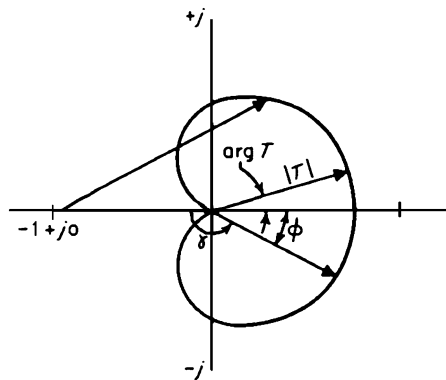


FIGURE 11.1.7 Nyquist diagram for determining stability.

1. Draw a vector from the  $-1 + j0$  point to the plotted curve and observe the rotation of this vector as  $\omega$  varies from  $-\infty$  to  $+\infty$ . Let  $R$  be the net number of counterclockwise revolutions of this vector.
2. Determine the number of roots of the denominator of  $T = -AB$  which have positive real parts. Call this number  $P$ .
3. The system is stable if and only if  $P = R$ . Note that in many systems  $A$  and  $B$  are stable by themselves, so that  $P$  becomes zero and the net counterclockwise revolution  $N$  becomes zero for stability.

**Bode's Technique.** A technique that has historically found wide use in determining stability and performance, especially in control systems, is the Bode diagram. The assumptions used here for this method are that  $T = -AB$ , where  $A$  and  $B$  are stable when the system is open-circuited and consists of minimum-phase networks. It is also necessary to define a phase margin  $\gamma$  such that  $\gamma = 180 + \phi$ , where  $\phi$  is the phase angle of  $T$  and is positive when measured counterclockwise from zero, and  $\gamma$ , the phase margin,

is positive when measured counterclockwise from the  $180^\circ$  line (Fig. 11.1.7). The stability criterion under these conditions reads: Systems having a positive phase margin when their return ratio equal to  $20 \log |T|$  goes through 0 dB (i.e., where  $|T|$  crosses the unit circle in the Nyquist plot) are stable; if a negative  $\gamma$  exists at 0 dB, the system is unstable.

Bode's theorems show that the phase angle of a system is related to the attenuation or gain characteristic as a function of frequency. Bode's technique relies heavily on straight-line approximation.

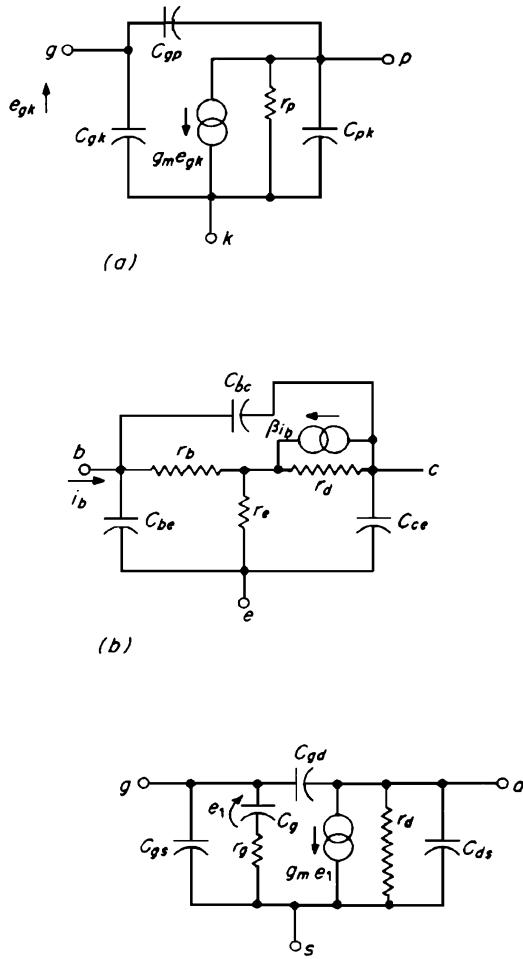


FIGURE 11.1.8 Equivalent circuits of active devices: (a) vacuum tube; (b) bipolar transistor; (c) field-effect transistor (FET).

**Routh's Criterion for Stability.** Routh's method has also been used to test the characteristic equations or return difference  $F = 1 + T = 0$ , to determine whether it has any roots that are real and positive or complex with positive real parts that will give rise to growing exponential responses and hence instability.

**Root-Locus Method.** The root-locus method of analysis is a means of finding the variations of the poles of a closed-loop response as some network parameter is varied. The most convenient and commonly used parameter is that of the gain  $K$ . The basic equation then used is

$$F = 1 + KT(s) = 1 - K \frac{(S - S_2)(S - S_4) \cdots}{(S - S_1)(S - S_3) \cdots} = 0$$

This is a useful technique in feedback and control systems, but it has not found wide application in amplifier design. A detailed exposition of the technique is found in Truxal.

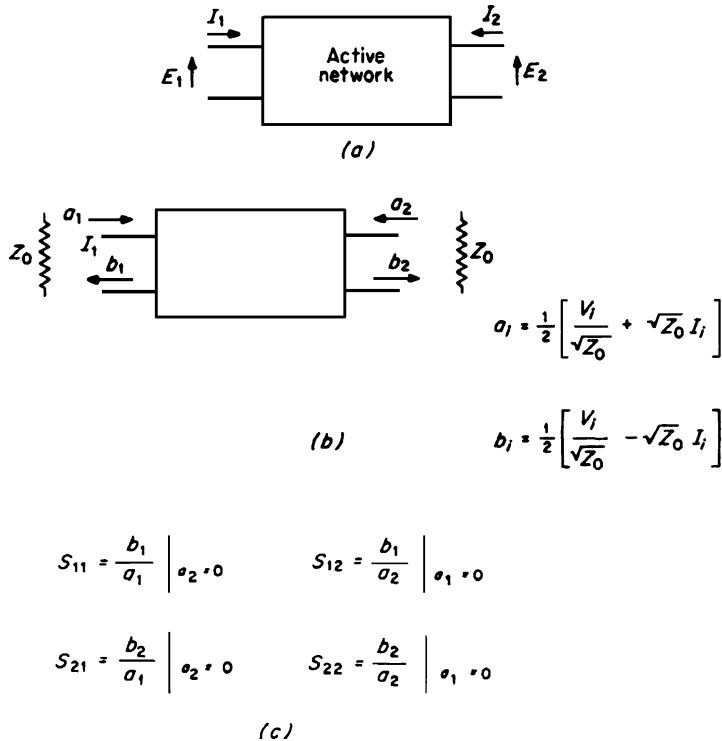


FIGURE 11.1.9 Definitions of active-network parameters: (a) general network; (b) ratios  $a_i$  and  $b_i$  of incident and reflected waves (square root of power); (c)  $s$  parameters.

**Active Devices Used in Amplifiers**

There are numerous ways of representing active devices and their properties. Several common equivalent circuits are shown in Fig. 11.1.8. Active devices are best analyzed in terms of the *immittance* or *hybrid matrices*. Figures 11.1.9 and 11.1.10 show the definition of the commonly used matrices, and their interconnections are shown in Fig. 11.1.11. The requirements at the bottom of Fig. 11.1.11 must be met before the interconnection of two matrices is allowed.

The matrix that is becoming increasingly important at higher frequencies is the  $S$  matrix. Here the network is embedded in a transmission-line structure, and the incident and reflected powers are measured and reflected coefficients and transmission coefficients are defined.

**Cascaded and Distributed Amplifiers**

Most amplifiers are cascaded (i.e., connected to a second amplifier). The two techniques commonly used are shown in Fig. 11.1.12. In the cascade structure the overall response is the product of the individual responses: in the distributed structure the response is one-half the sum of the individual responses, since each stage's output is propagated in both directions. In cascaded amplifiers the frequency response and gain are determined by the active device as well as the interstage networks. In simple audio amplifiers these interstage networks may become simple  $RC$  combinations, while in rf amplifiers they may become critically coupled double-tuned circuits. Interstage coupling networks are discussed in subsequent sections.

$\begin{bmatrix} E_1 \\ E_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \times \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$	$z_{11} = \left( \frac{E_1}{I_1} \right)_{I_2=0}$	$z_{12} = \left( \frac{E_1}{I_2} \right)_{I_1=0}$
$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \times \begin{bmatrix} E_1 \\ E_2 \end{bmatrix}$	$y_{11} = \left( \frac{I_1}{E_1} \right)_{E_2=0}$	$y_{12} = \left( \frac{I_1}{E_2} \right)_{E_1=0}$
$\begin{bmatrix} E_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \times \begin{bmatrix} I_1 \\ E_2 \end{bmatrix}$	$h_{11} = \frac{1}{y_{11}}$	$h_{12} = \left( \frac{E_1}{E_2} \right)_{I_1=0}$
$\begin{bmatrix} I_1 \\ E_2 \end{bmatrix} = \begin{bmatrix} l_{11} & l_{12} \\ l_{21} & l_{22} \end{bmatrix} \times \begin{bmatrix} E_1 \\ I_2 \end{bmatrix}$	$l_{11} = \frac{1}{z_{11}}$	$l_{12} = \left( \frac{I_1}{I_2} \right)_{E_1=0}$
$\begin{bmatrix} E_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \times \begin{bmatrix} E_2 \\ -I_2 \end{bmatrix}$	$a_{11} = \frac{1}{l_{21}}$	$a_{12} = -\frac{1}{y_{21}}$
$\begin{bmatrix} E_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} \times \begin{bmatrix} E_1 \\ -I_1 \end{bmatrix}$	$a_{21} = \frac{1}{z_{21}}$	$a_{22} = -\frac{1}{h_{21}}$
$\begin{bmatrix} b_1 \\ b_2 \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{bmatrix} \times \begin{bmatrix} a_1 \\ a_2 \end{bmatrix}$	$b_{11} = \frac{1}{h_{12}}$	$b_{12} = -\frac{1}{y_{12}}$
	$b_{21} = \frac{1}{z_{12}}$	$b_{22} = -\frac{1}{l_{12}}$
	$S_{11} = \left( \frac{b_1}{a_1} \right)_{a_2=0}$	$S_{12} = \left( \frac{b_1}{a_2} \right)_{a_1=0}$
	$S_{21} = \left( \frac{b_2}{a_1} \right)_{a_2=0}$	$S_{22} = \left( \frac{b_2}{a_2} \right)_{a_1=0}$

FIGURE 11.1.10 Network matrix terms.

In distributed structures (Fig. 11.1.12b), actual transmission lines are used for the input to the amplifier, while the output is taken at one end of the upper transmission line. The propagation time along the input line must be the same as that along the output line, or distortion will result. This type of amplifier, noted for its wide frequency response, is discussed later.

## OSCILLATORS: PRINCIPLES OF OPERATION

### Introduction

An oscillator can be considered as a circuit that converts a dc input to a time-varying output. This discussion deals with oscillators whose output is sinusoidal, as opposed to the relaxation oscillator whose output exhibits abrupt transitions (see Section 14). Oscillators often have a circuit element that can be varied to produce different frequencies.

An oscillator's frequency is sensitive to the stability of the frequency-determining elements as well as the variation in the active-device parameters (e.g., effects of temperature, bias point, and aging). In many instances

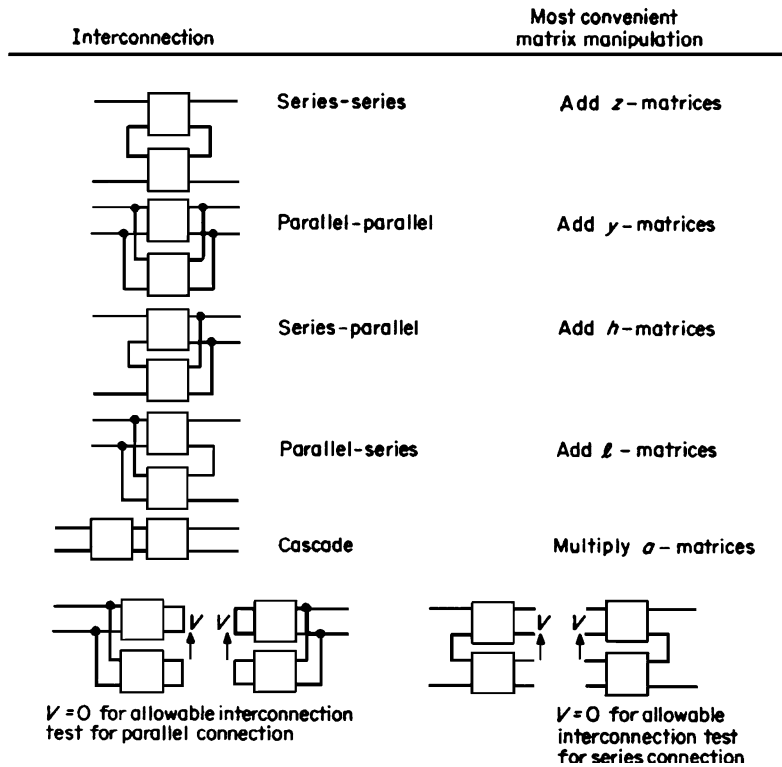


FIGURE 11.1.11 Matrix equivalents of network interconnections.

the oscillator is followed by a second stage serving as a buffer, so that there is isolation between the oscillator and its load. The amplitude of the oscillation can be controlled by automatic gain control (AGC) circuits, but the nonlinearity of the active element usually determines the amplitude. Variations in bias, temperature, and component aging have a direct effect on amplitude stability.

### Requirements for Oscillation

Oscillators can be considered from two viewpoints: as using positive feedback around an amplifier or as a one-port network in which the real component of the input immittance is negative. An oscillator must have frequency-determining elements (generally passive components), an amplitude-limiting mechanism, and sufficient closed-loop gain to make up for the losses in the circuit. It is possible to predict the operating frequency and conditions needed to produce oscillation from a Nyquist or Bode analysis. The prediction of output amplitude requires the use of nonlinear analysis.

### Oscillator Circuits

Typical oscillator circuits applicable up to ultra high frequencies (UHF) are shown in Fig. 11.1.13. These are discussed in detail in the following subsections. Also of interest are crystal oscillators. In this case the crystal is used as the passive frequency-determining element. The frequency range of crystal oscillators extends from a few hundred hertz to over 200 MHz by use of overtone crystals. The analysis of crystal oscillators is best done using the equivalent circuit of the crystal.

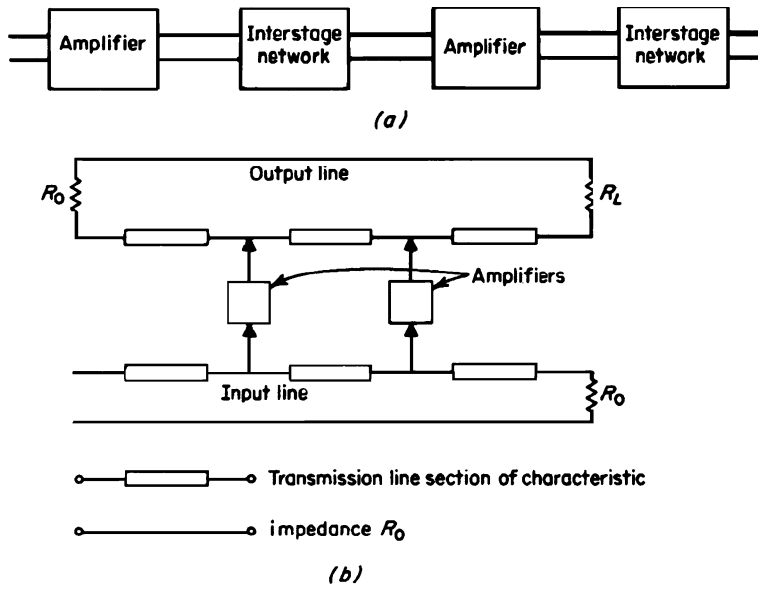


FIGURE 11.1.12 Multi-amplifier structures: (a) cascade; (b) distributed.

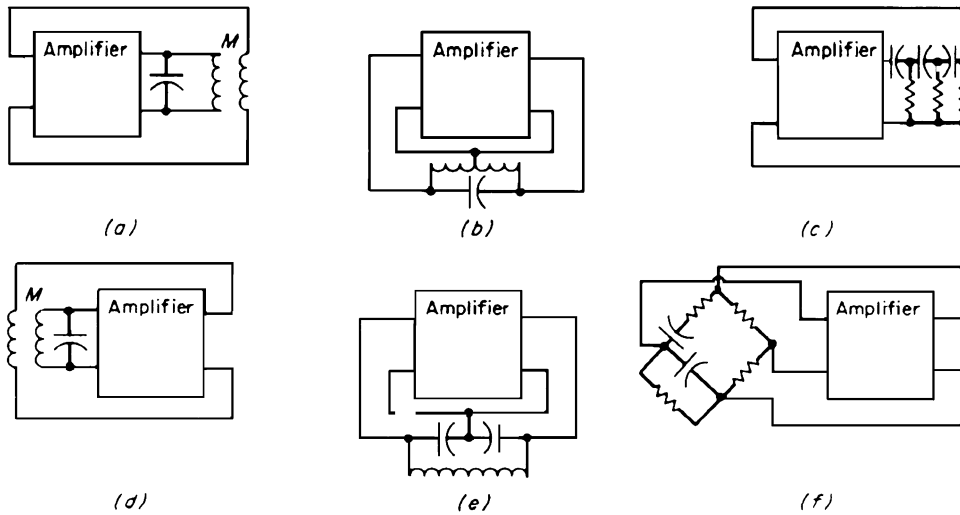


FIGURE 11.1.13 Types of oscillators: (a) tuned-output; (b) Hartley; (c) phase-shift; (d) tuned-input; (e) Colpitts; (f) Wien bridge.

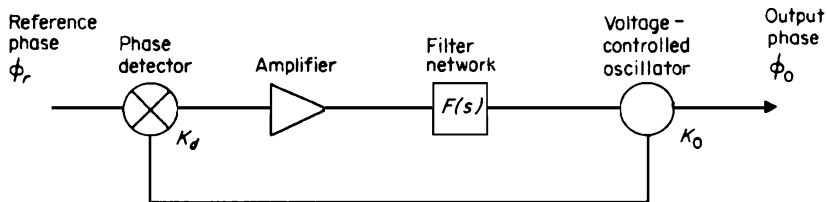


FIGURE 11.1.14 Phase-locked-loop oscillator.



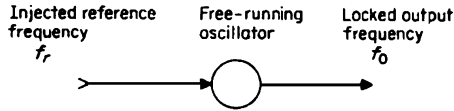


FIGURE 11.1.15 Injection-locked oscillator.

### Synchronization

Synchronization of oscillators is accomplished by using phase-locked loops or by direct low-level injection of a reference frequency into the main oscillator. The diagram of a phase-locked loop is shown in Fig. 11.1.14 and that of an injection-locked oscillator in Fig. 11.1.15.

### Harmonic Content

The harmonic content of the oscillator output is related to the amount of oscillator output power at frequencies other than the fundamental. From the viewpoint of a negative-conductance (resistance) oscillator, better results are obtained if the curve of the negative conductance (or resistance) versus amplitude of oscillation is smooth and without an inflection point over the operating range. Harmonic content is also reduced if the oscillator's operating point  $Q$  is chosen so that the range of negative conductance is symmetrical about  $Q$  on the negative conductance-versus-amplitude curve. This can be done by adjusting the oscillator's bias point within the requirement of  $|G_C| = |G_D|$  for sustained oscillation (see Fig. 11.1.16).

### Stability

The stability of the oscillator's output amplitude and frequency from a negative-conductance viewpoint depends on the variation of its negative conductance with operating point and the amount of fixed positive conductance in the oscillator's associated circuit. In particular, if the change of bias results in vertical translation of the conductance-(resistance)-versus-amplitude curve, the oscillator's stability is related to the change of slope at the point where the circuit's fixed conductance intersects this curve (point  $Q$  in Fig. 11.1.16). If the  $|G_D|$  curve is of the shape of  $|G_D|_2$ , the oscillation can stop when a large enough change in bias point occurs for  $|G_D|$  to be less than  $|G_C|$  for all amplitudes of oscillation. Stabilization of the amplitude of oscillation may occur in the form of modifying  $G_C$ ,  $G_D$ , or both to compensate for bias changes.

Particular types of oscillators and their parameters are discussed later in this section.

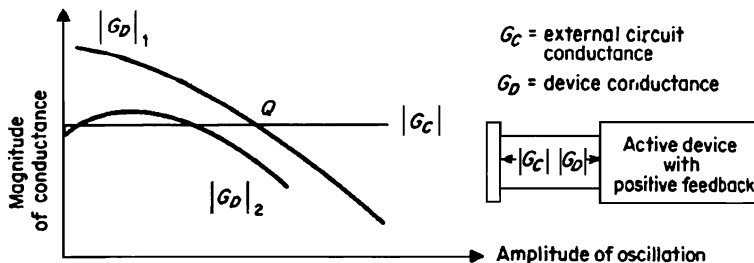


FIGURE 11.1.16 Device conductance vs. amplitude of oscillation.