

$$\underline{i_m(t)} = \underline{-\frac{1}{Z_c} v_m(t) + I_m}$$



$\frac{d}{c}$


$$I_m = \underline{i_k(t - \frac{d}{c}) + \frac{1}{Z_c} v_k(t - \frac{d}{c})}$$

$$i_k(t) = \frac{v_m(t)}{Z_c} + I_k$$

'v_p' is the same as 'c' (velocity of propagation)
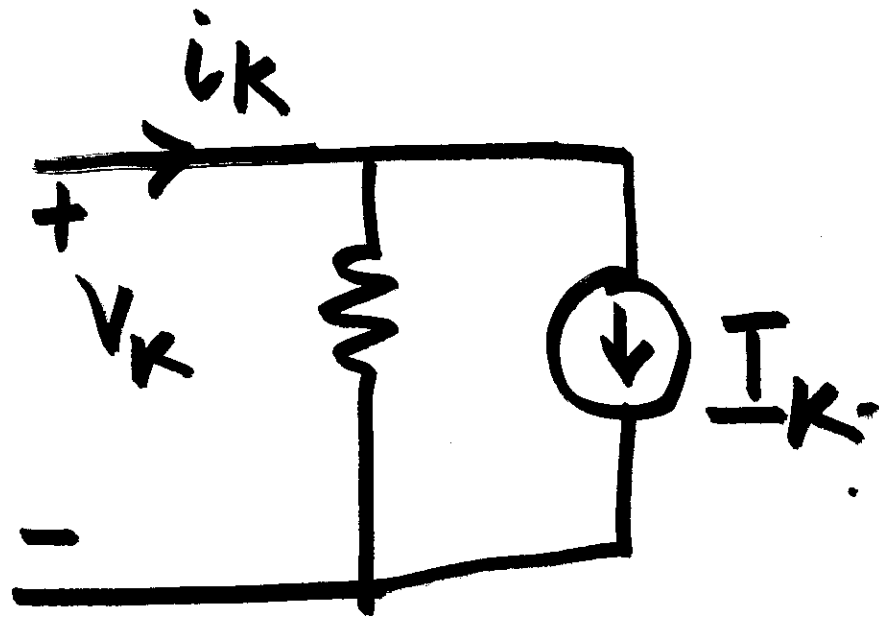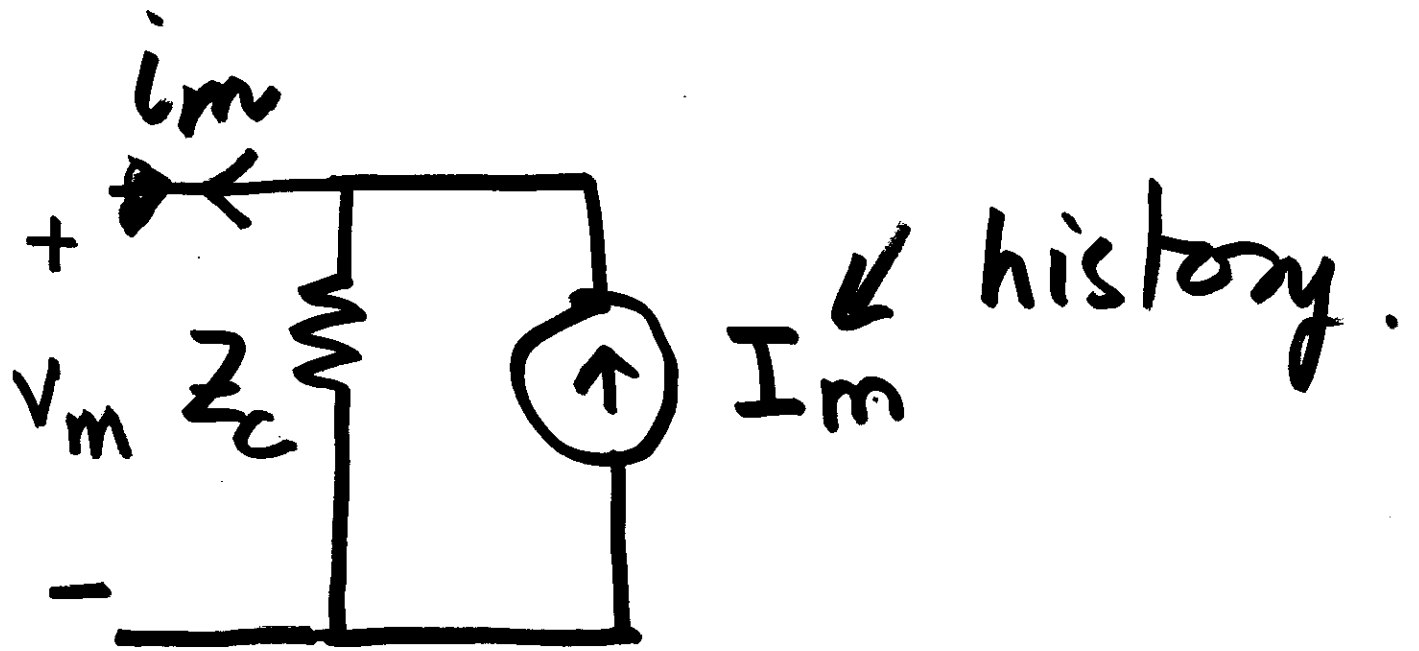
$$I_k = i_m(t - \frac{d}{c}) - \frac{1}{Z_c} v_m(t - \frac{d}{c})$$



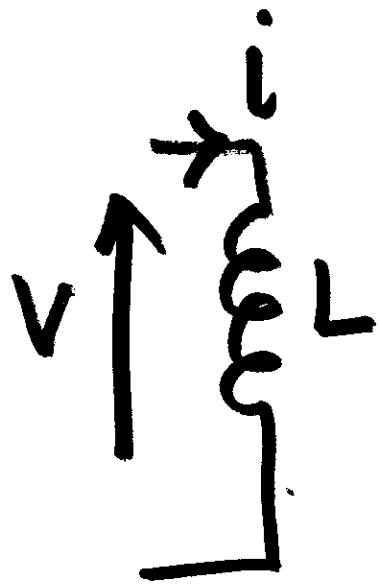


$$\left(\frac{d}{e}\right)$$


$$L \frac{di}{dt} = v$$

$$L \left\{ \frac{i((k+1) \cdot h) - i(k \cdot h)}{h} \right\} = \frac{1}{2} [V((k+1) \cdot h) + V(k \cdot h)]$$

$$\frac{d}{c} = h.$$

$$\underline{\underline{h}}$$

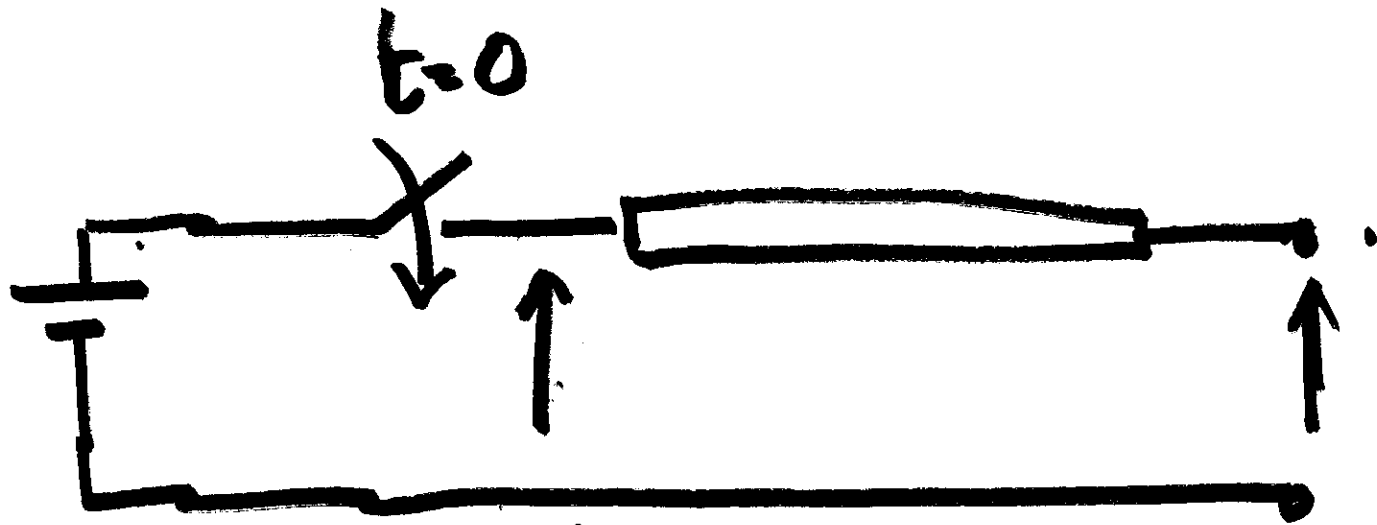



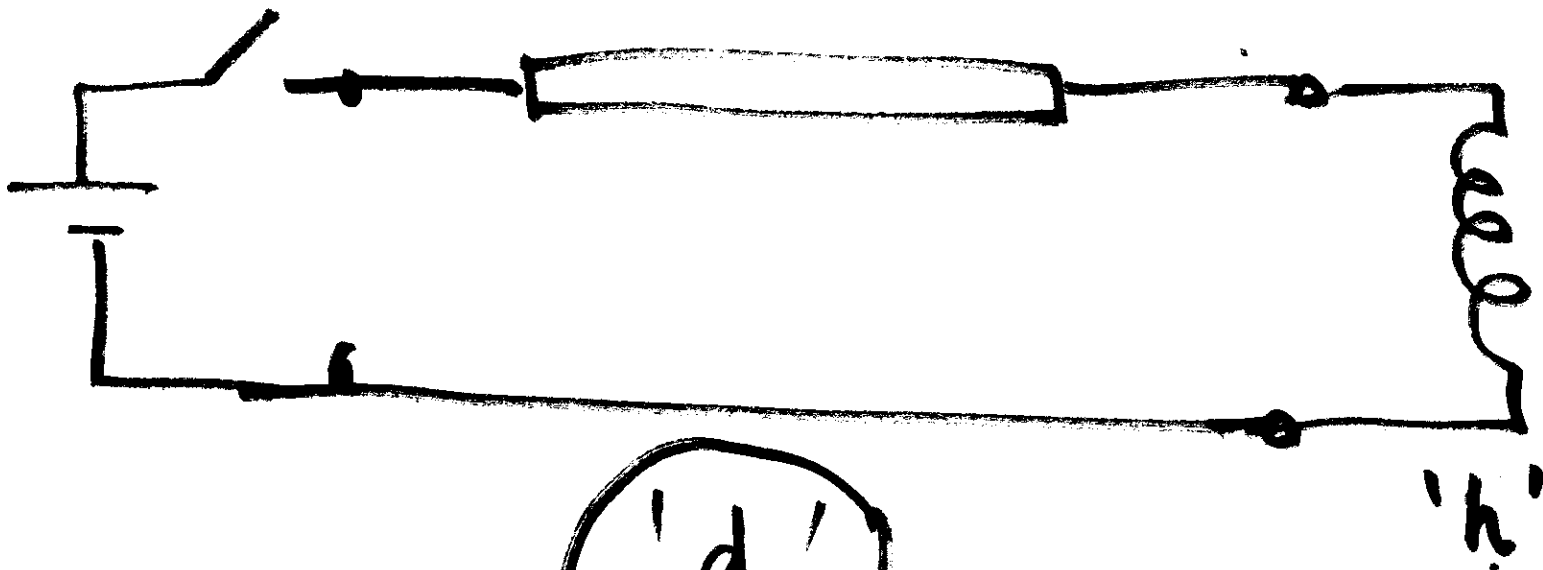


'k'

?

$$\frac{d}{c} \approx kh$$

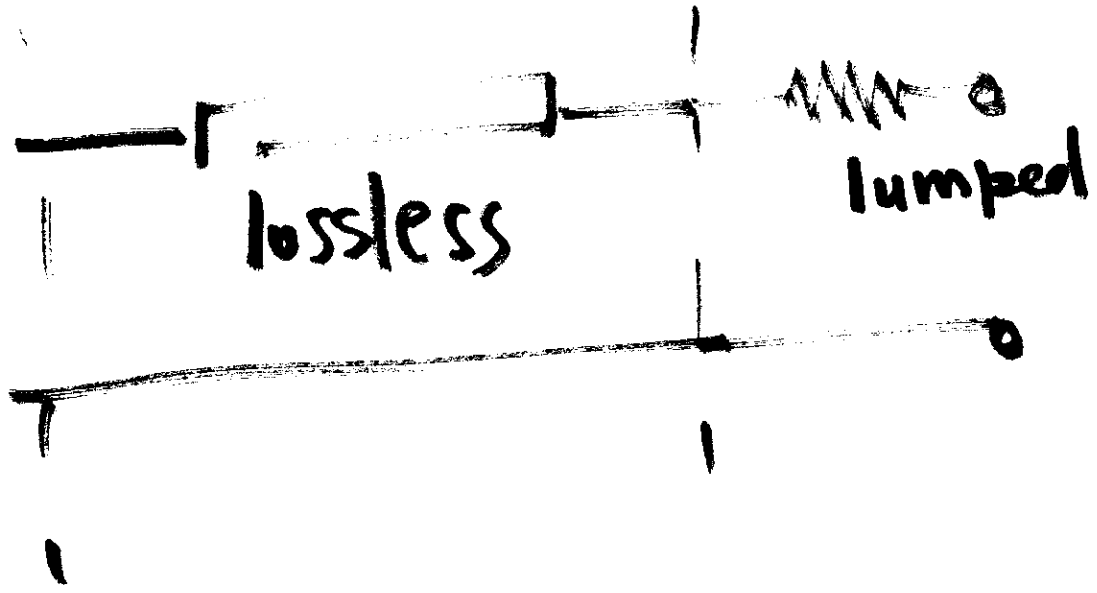

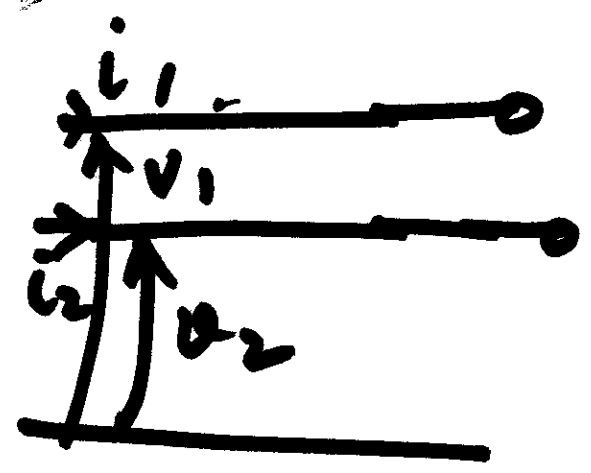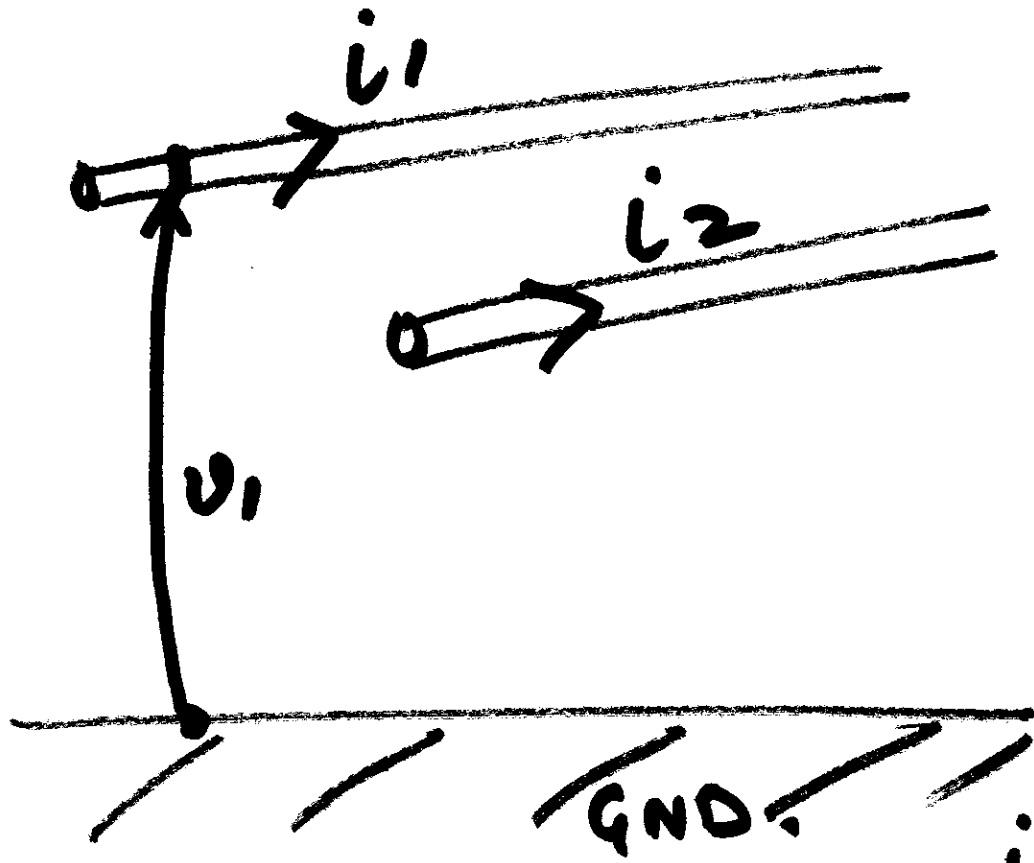

$$\begin{bmatrix} \frac{ze}{ze} \\ \frac{ze}{ze} \\ \frac{ze}{ze} \\ \frac{ze}{ze} \end{bmatrix}$$

$$v_{\text{diff}} = v_1 - v_2.$$

$$v_{\text{com}} = \frac{v_1 + v_2}{2}.$$

$$i_{\text{diff}} = i_1 - i_2.$$

$$i_{\text{com}} = \frac{i_1 + i_2}{2}$$

$$\begin{bmatrix} C_m \\ C_s \end{bmatrix} \begin{bmatrix} \frac{\partial v_1}{\partial t} \\ \frac{\partial v_2}{\partial t} \end{bmatrix} = \begin{bmatrix} \frac{\partial i_1}{\partial x} \\ \frac{\partial i_2}{\partial x} \end{bmatrix}$$

$$\underline{i_g = (i_1 + i_2)}$$

$$\begin{bmatrix} L_s & L_m \\ L_m & L_s \end{bmatrix} \begin{bmatrix} \frac{di_1}{dt} \\ \frac{di_2}{dt} \end{bmatrix} = \begin{bmatrix} \frac{v_1}{R} \\ \frac{v_2}{R} \end{bmatrix}$$



$$\begin{bmatrix} L_s - L_m & 0 \\ 0 & L_s + L_m \end{bmatrix} \begin{bmatrix} \frac{\partial i_{diff}}{\partial t} \\ \frac{\partial i_{com}}{\partial t} \end{bmatrix} = \begin{bmatrix} \frac{\partial v_{diff}}{\partial x} \\ \frac{\partial v_{com}}{\partial x} \end{bmatrix}$$

diagonal

i_{diff} , v_{diff}


v_{com} , i_{com} .
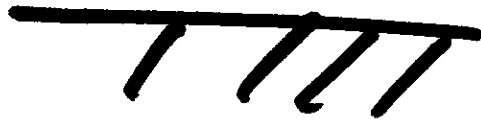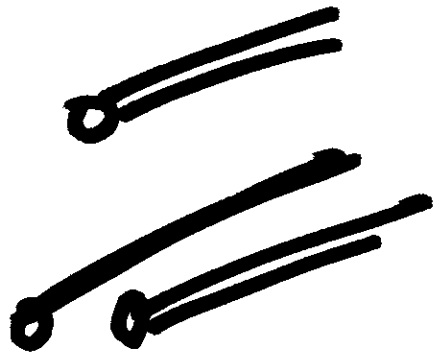
$$\begin{bmatrix} C_s - C_m & 0 \\ 0 & C_s + C_m \end{bmatrix} \begin{bmatrix} \frac{\partial v_{diff}}{\partial t} \\ \frac{\partial v_{com}}{\partial t} \end{bmatrix} = \begin{bmatrix} \frac{\partial i_{diff}}{\partial x} \\ \frac{\partial i_{com}}{\partial x} \end{bmatrix}$$



GND
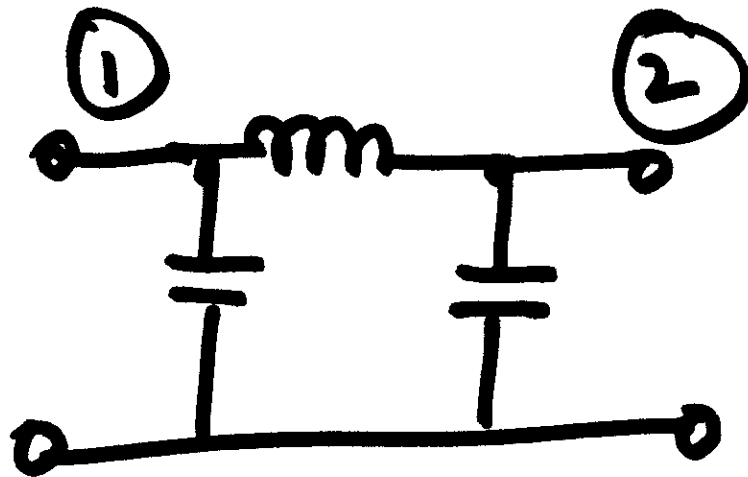
$$\begin{bmatrix} L_s & L_m & L_m \\ L_m & L_s & L_m \\ L_m & L_m & L_s \end{bmatrix} \begin{bmatrix} \frac{di_a}{dt} \\ \frac{di_b}{dt} \\ \frac{di_c}{dt} \end{bmatrix} = \begin{bmatrix} V_{a1} - V_{a2} \\ V_{b1} - V_{b2} \\ V_{c1} - V_{c2} \end{bmatrix}$$



$C_p(\theta)$

$$L \frac{di^{abc}}{dt} = \underline{V_1^{abc}} - \underline{V_2^{abc}}$$

$$\frac{d\phi}{dt} i^{dq0} + L C_p \frac{di^{dq0}}{dt} = C_p V_1^{dq0} - C_p V_2^{dq0}$$

$$\therefore \underline{\underline{C_p^{-1} L C_p}} \frac{di^{dq0}}{dt} = V_1^{dq0} - V_2^{dq0}$$

$$\begin{aligned}
 & \begin{matrix} \nearrow \\ \left[\begin{array}{ccc} L_s - L_m & 0 & 0 \\ 0 & L_s - L_m & 0 \\ 0 & 0 & L_s + 2L_m \end{array} \right] \begin{bmatrix} \frac{di_d}{dt} \\ \frac{di_q}{dt} \\ \frac{di_o}{dt} \end{bmatrix} \\
 \leftarrow \\
 L^{-1} & = \begin{bmatrix} v_{d1} - v_{d2} \\ v_{q1} - v_{q2} \\ v_{o1} - v_{o2} \end{bmatrix} + L^{-1} \begin{bmatrix} 0 & -\omega \\ \omega & 0 \\ 0 & 0 \end{bmatrix} \begin{bmatrix} i_d \\ i_q \\ i_o \end{bmatrix}
 \end{aligned}$$