

LAYOUT GUIDELINES

1. Circuit Schematic
gEDA,
2. Physical dimensions to components
3. LAYOUT //
4. Routing
5. Gerber files

1. Dimensions of PWB
2. Card guide space
3. Mounting
4. Connectors.
5. Components (criticality, sensitivity, shorted interconnection length)


Routing


1. Supply and Ground


↑↑ STABILITY ↑↑

$$W_{\text{GROUND}} > W_{\text{SUPPLY}} > W_{\text{SIGNAL}}$$


SUPPLY -	Layer 1	(top layer)
GROUND -	Layer 2	(bot layer)

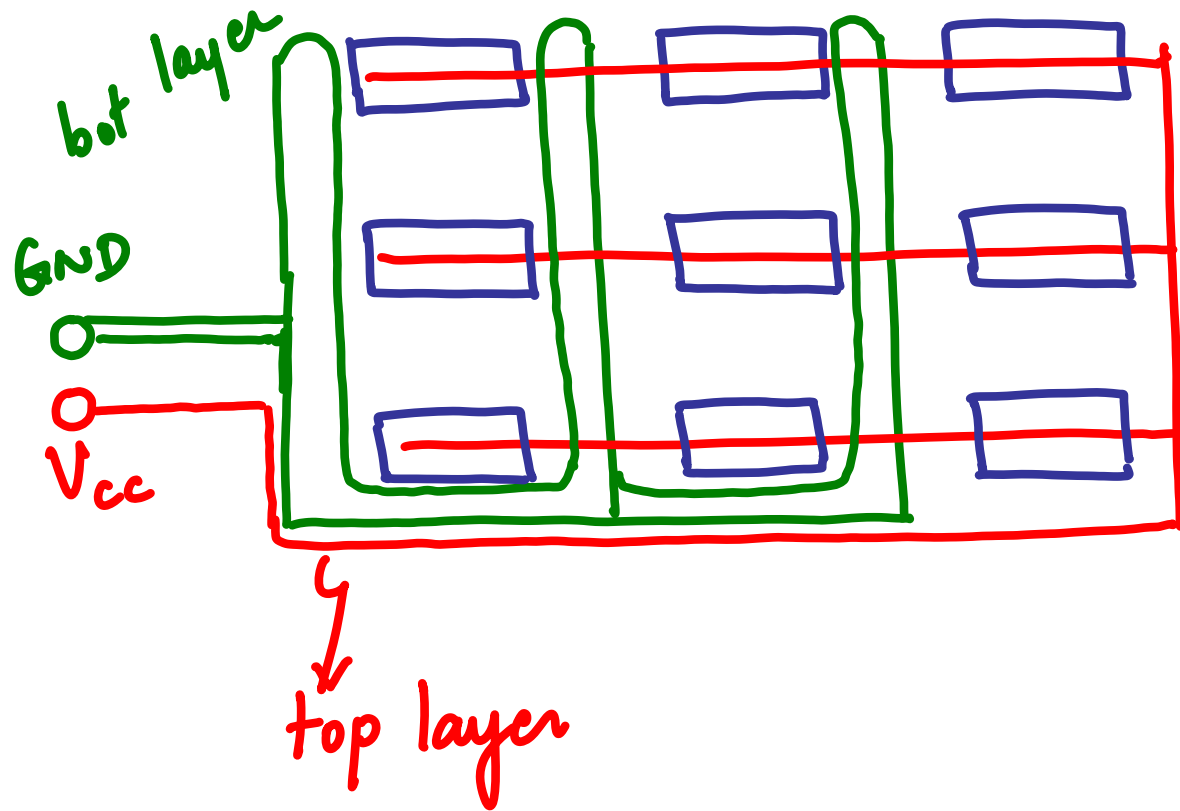

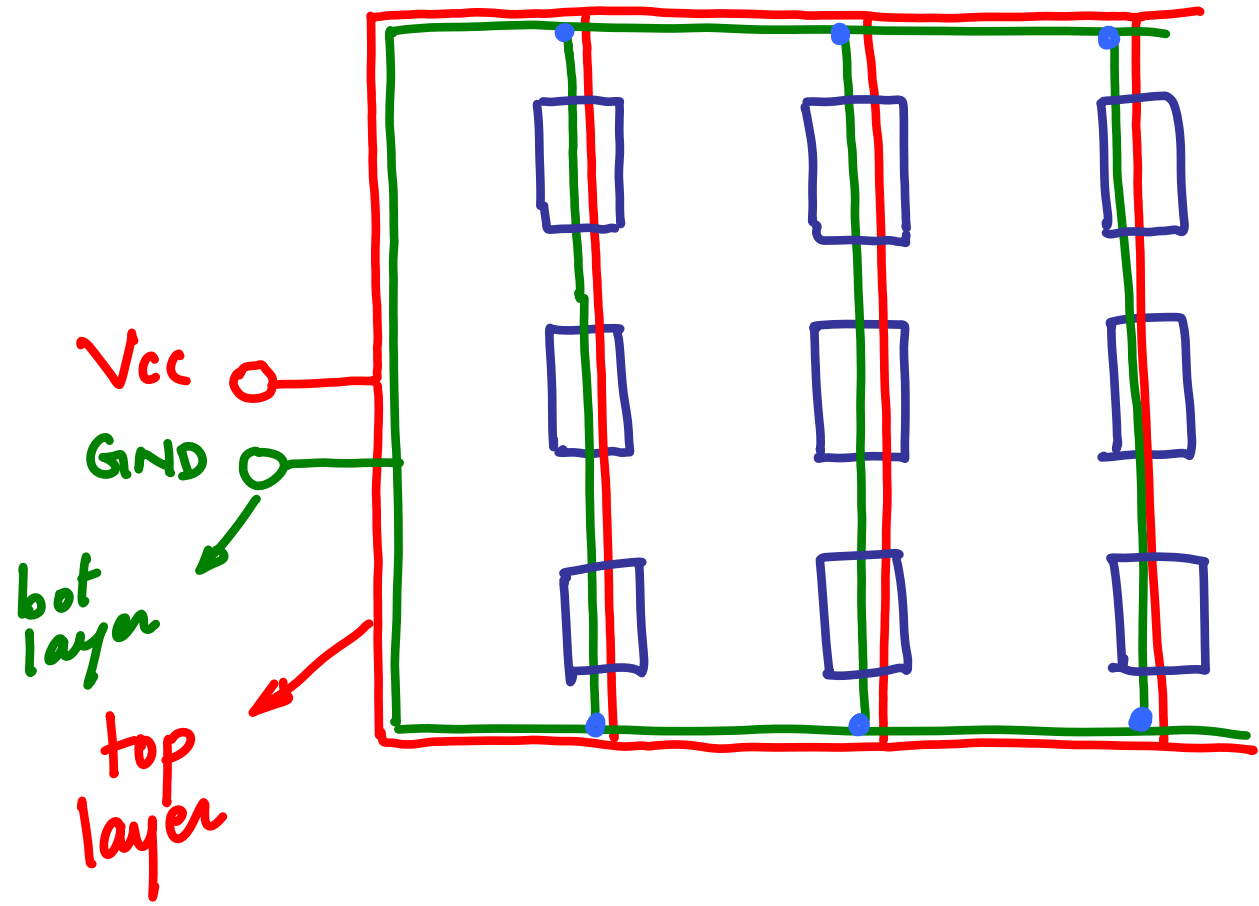

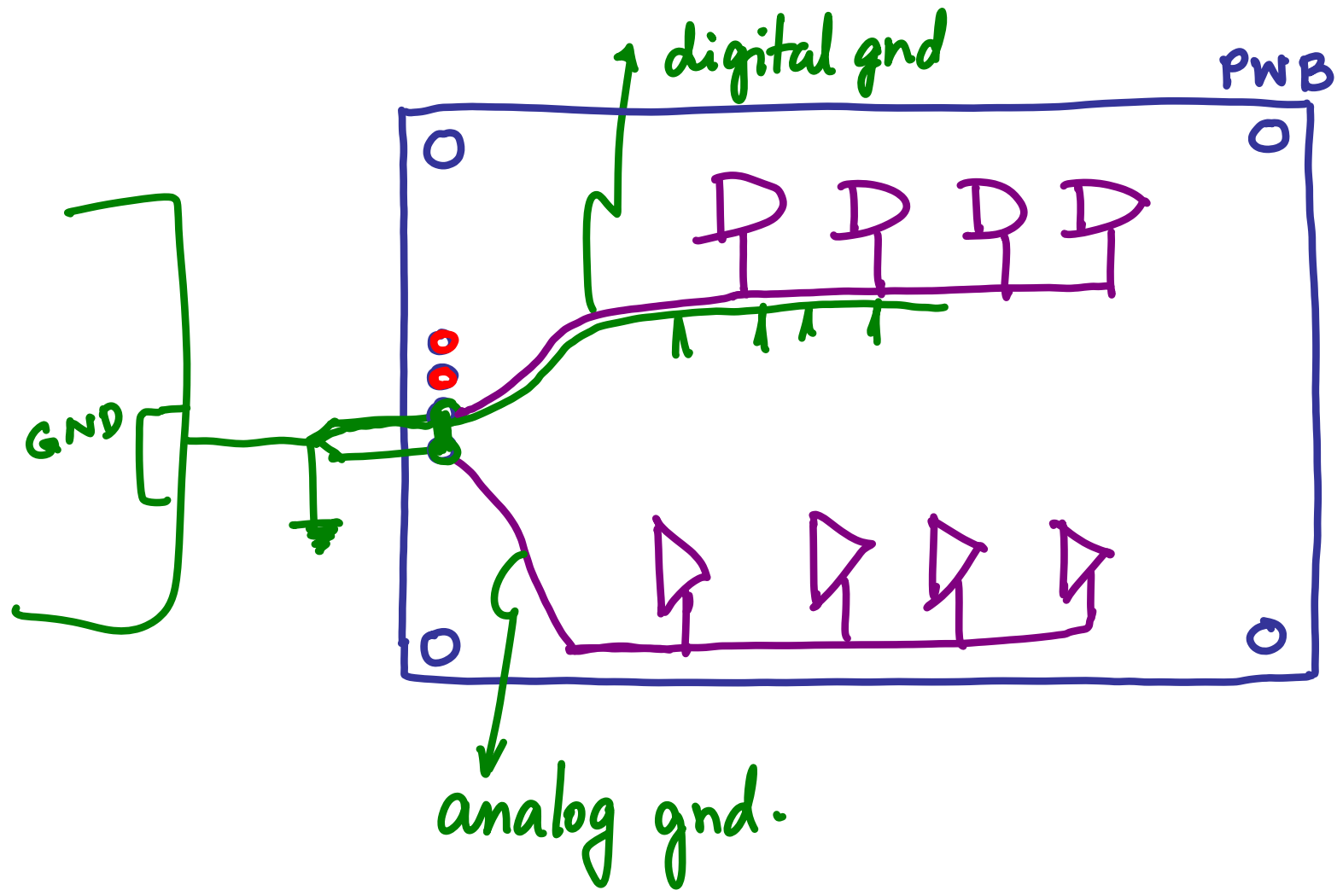

REFLECTIONS

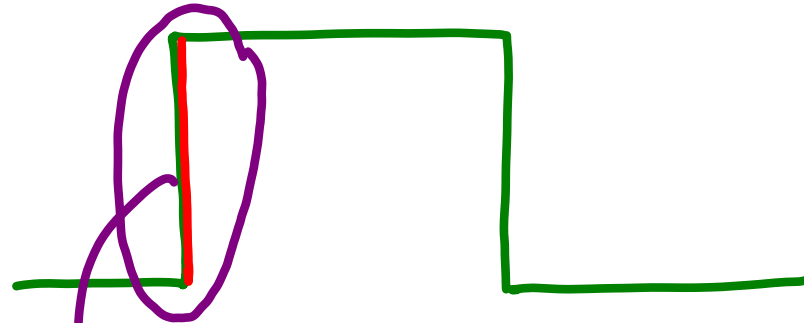


very high freq

t_r ns

bandwidth

$$= \frac{0.35}{t_r} =$$

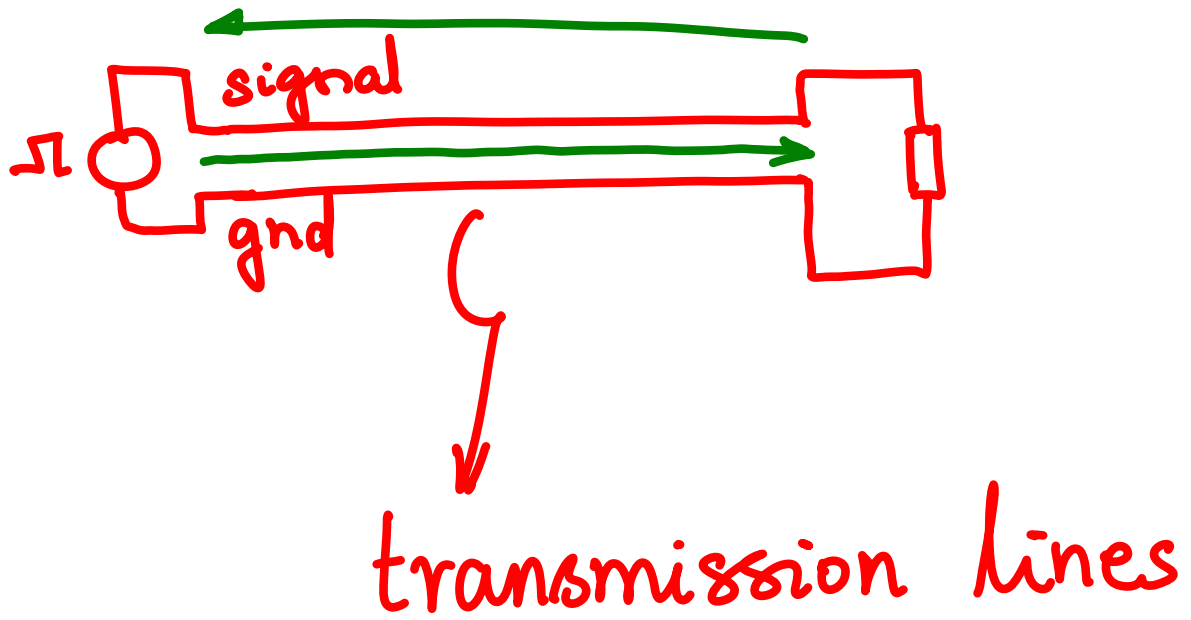

$$Z_w = \sqrt{\frac{L/\text{cm}}{C/\text{cm}}} \quad \begin{array}{l} \leftarrow \\ \equiv \\ \leftarrow \end{array}$$



Z_0





$$R_s = Z_w = \sqrt{\frac{L/cm}{C/cm}}$$


$$Z_w = R_o$$

Printed Capacitor

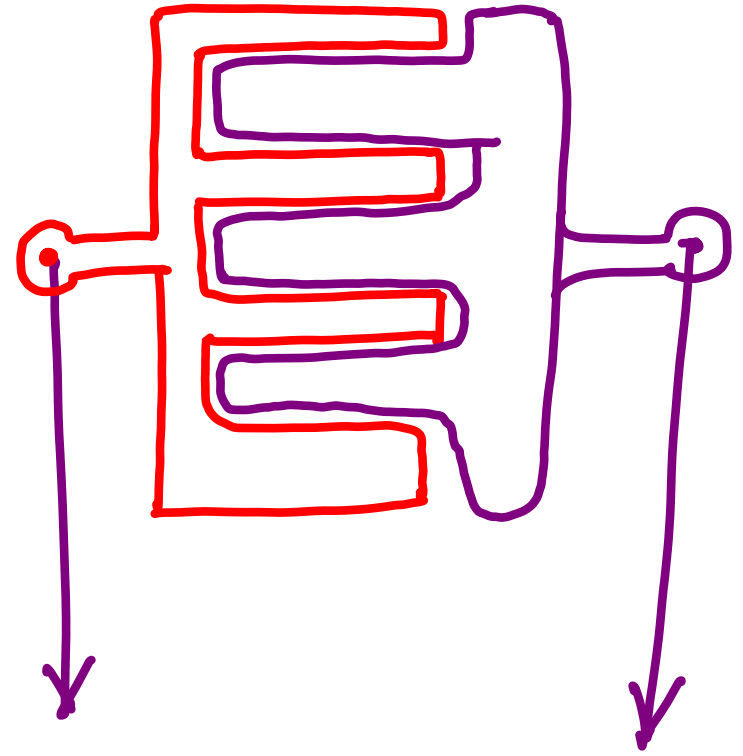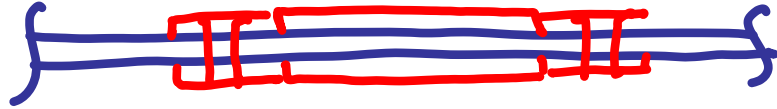


Printed Inductors

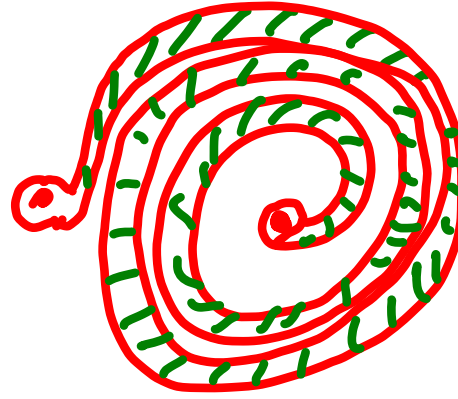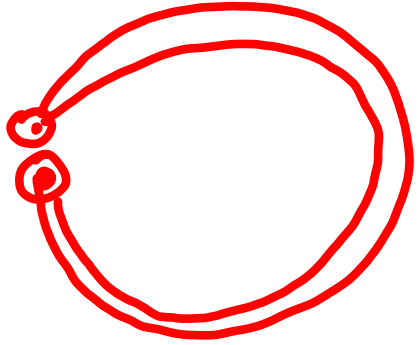

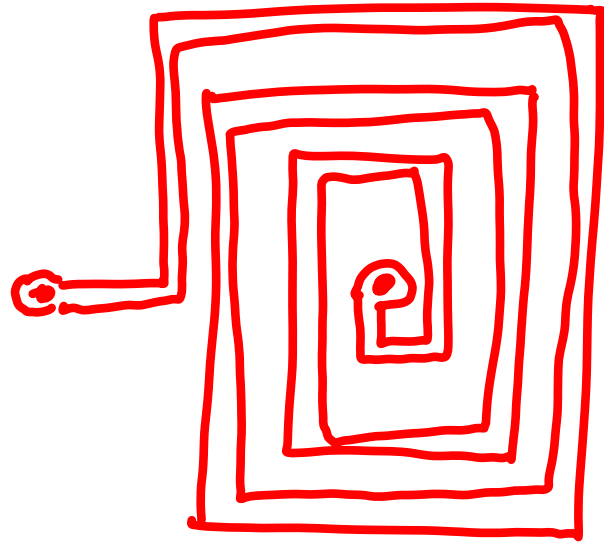



L

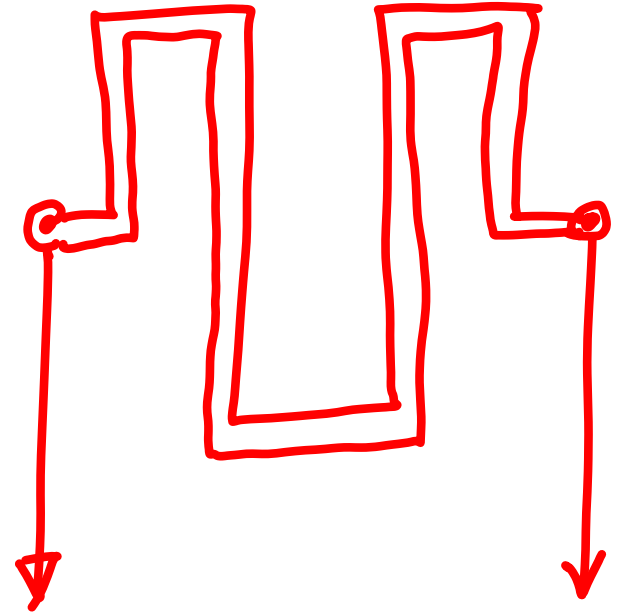

Connectors

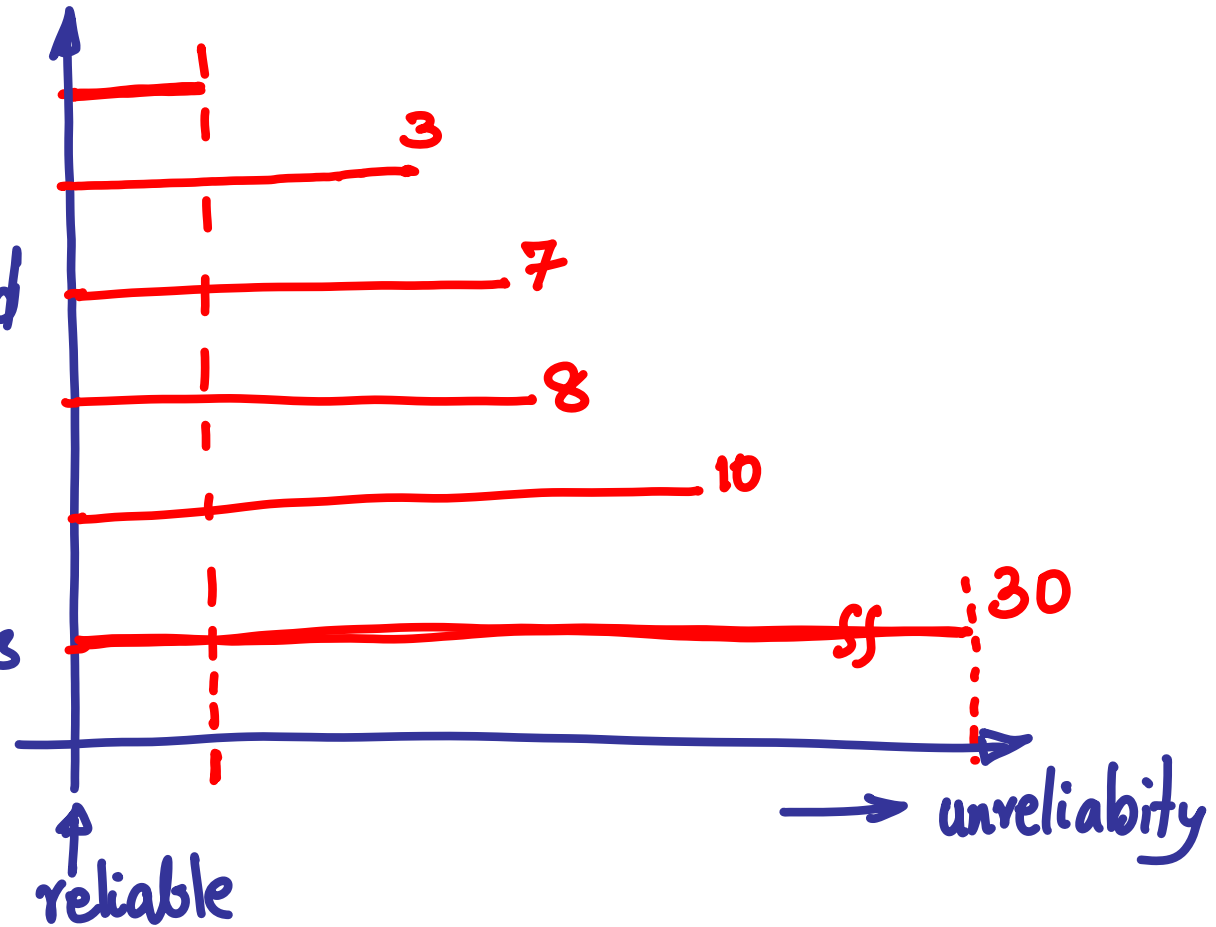1. Wrapped Joints
2. Welded joints
3. Machine soldered
4. Crimped Joints
5. Hand soldered
6. Edge connectors



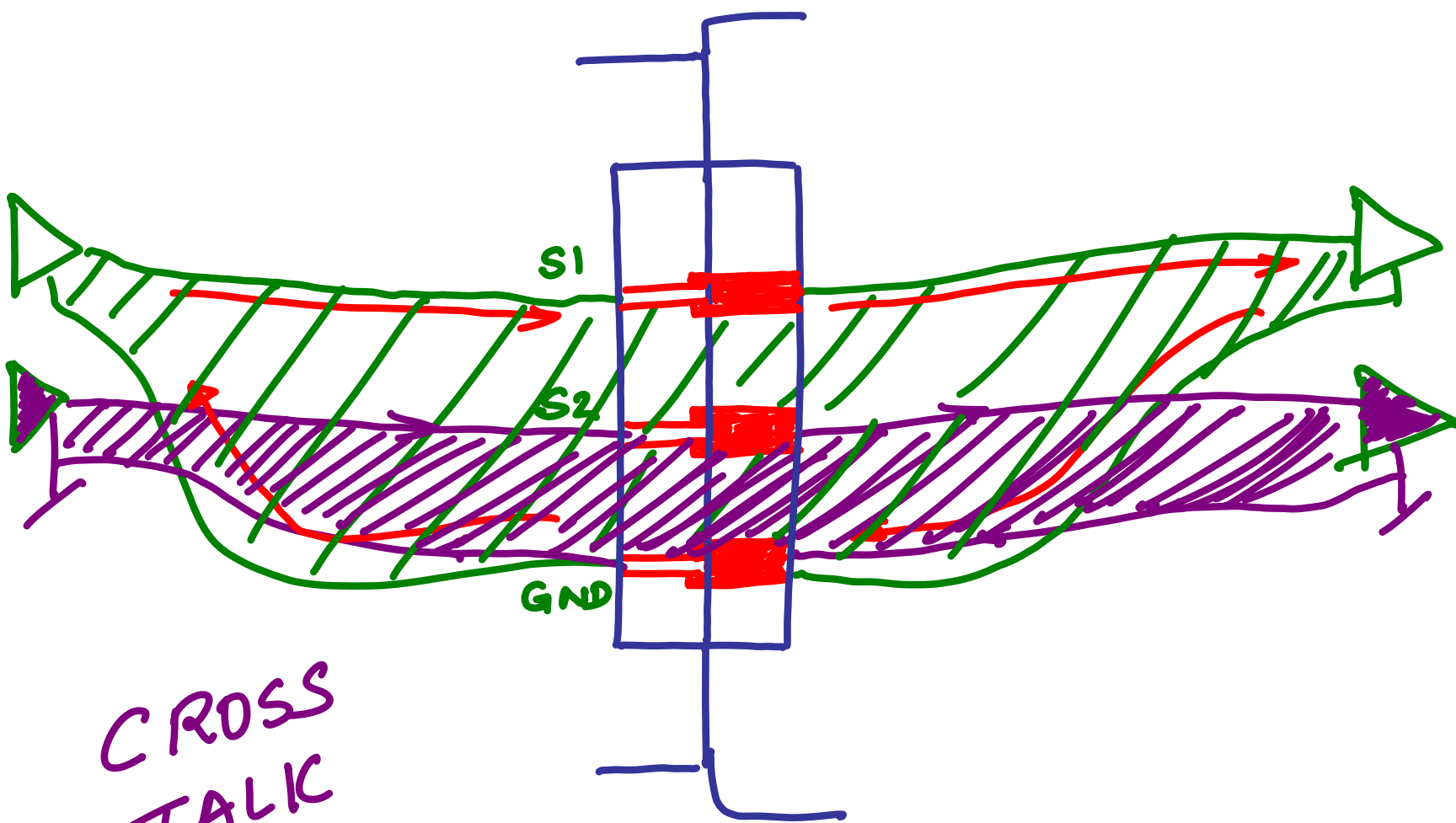


CROSS
TALK


cross talk \Rightarrow $\left(\begin{array}{c} \text{Mutual} \\ \text{Inductance} \end{array} \right) \cdot \frac{di}{dt}$

$\left(\begin{array}{c} \text{Loop} \\ \text{Area} \end{array} \right)$


\Downarrow
reduce

\Downarrow
reduce

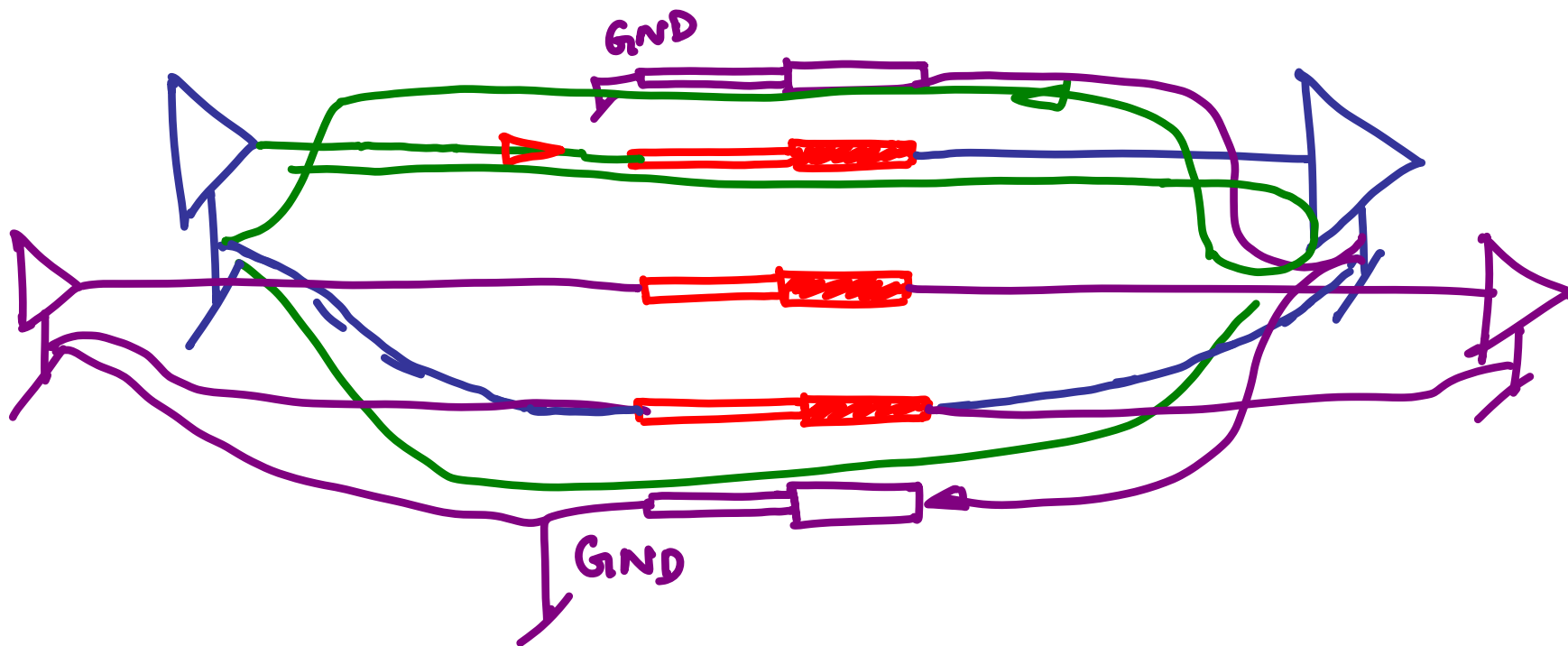

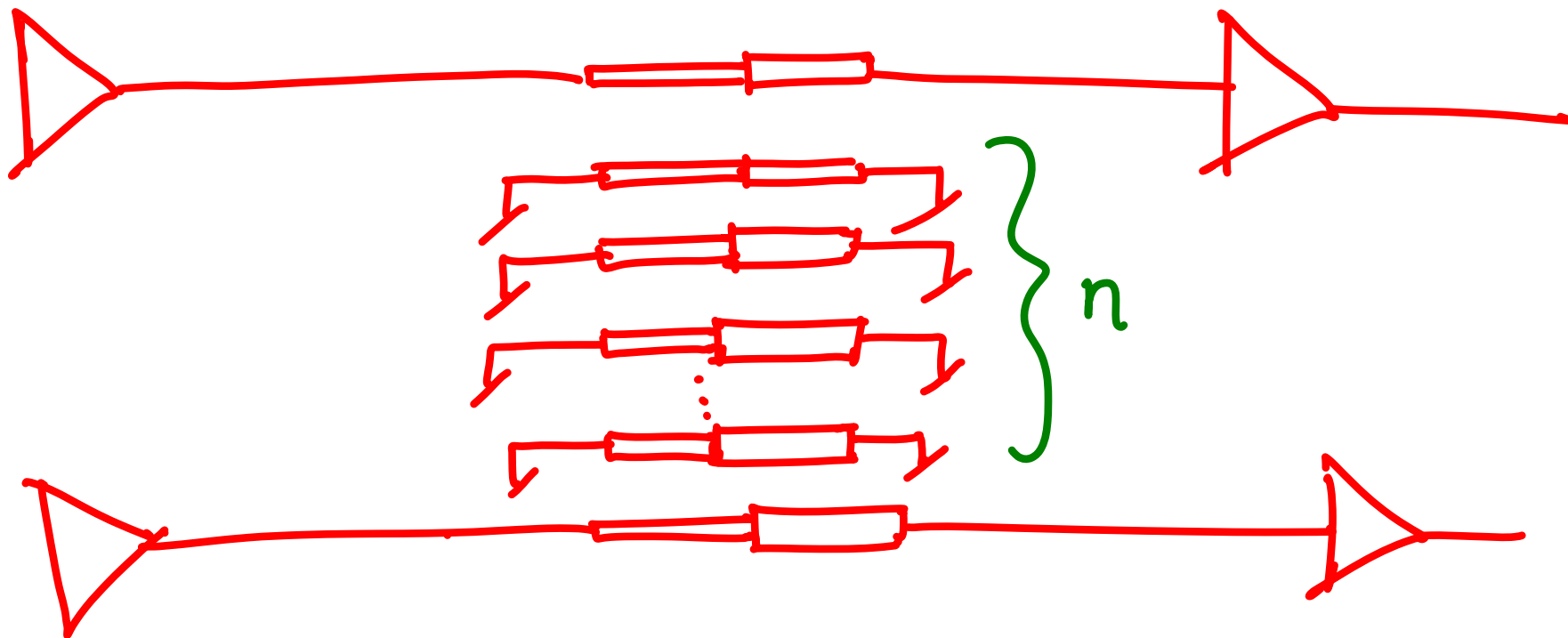



$$\frac{1}{n^2 + 1}$$

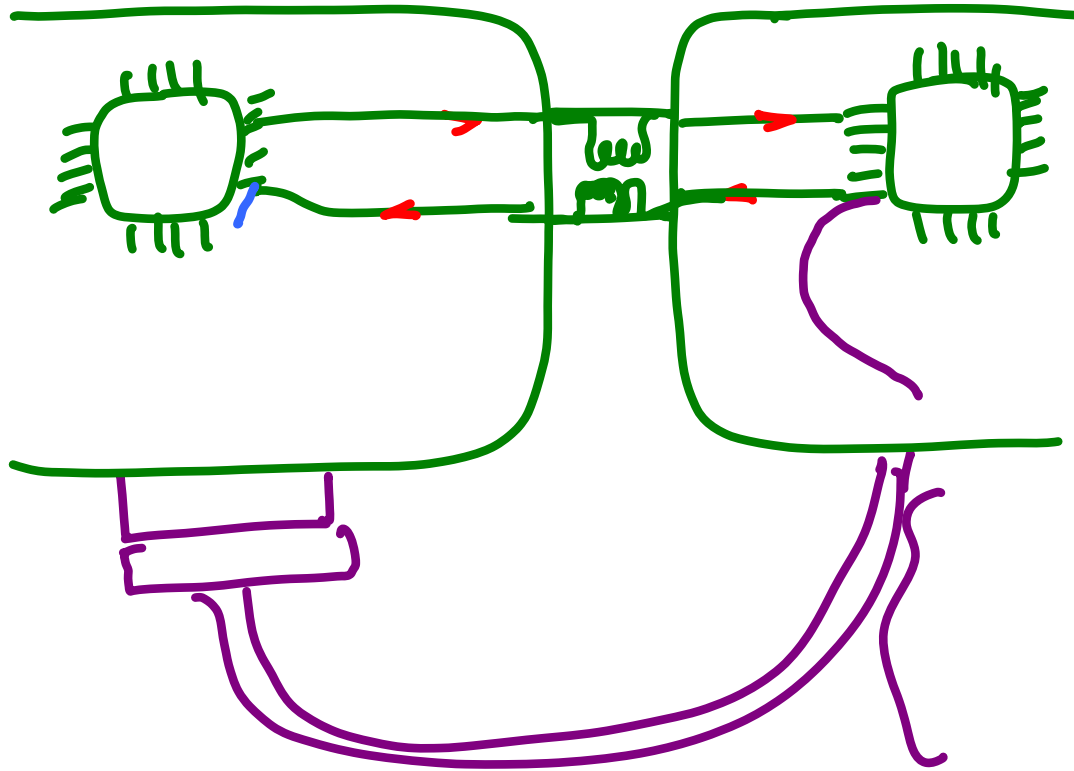

Reduce
Loop
area

high power line

guard line

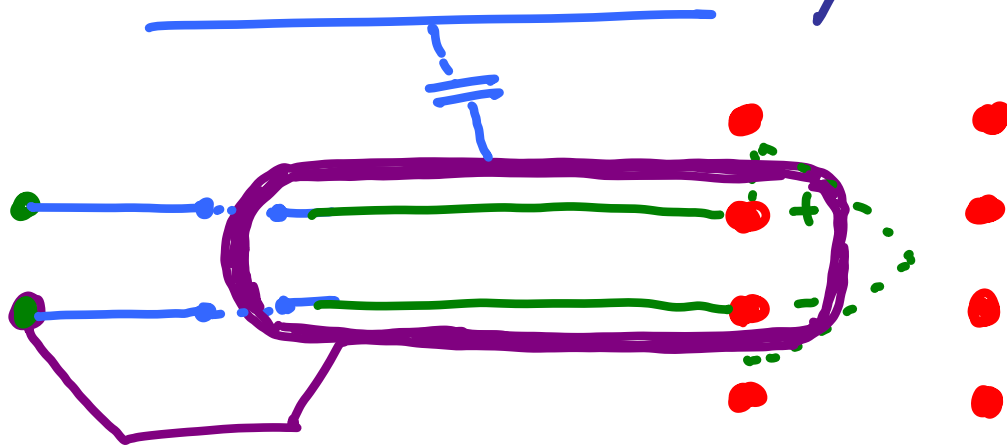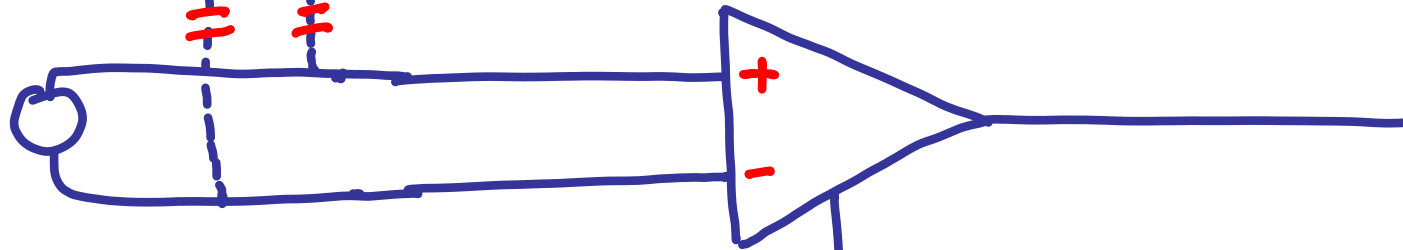


REFLECTION PROBLEM


REFLECTION PROBLEM




REFLECTION PROBLEM

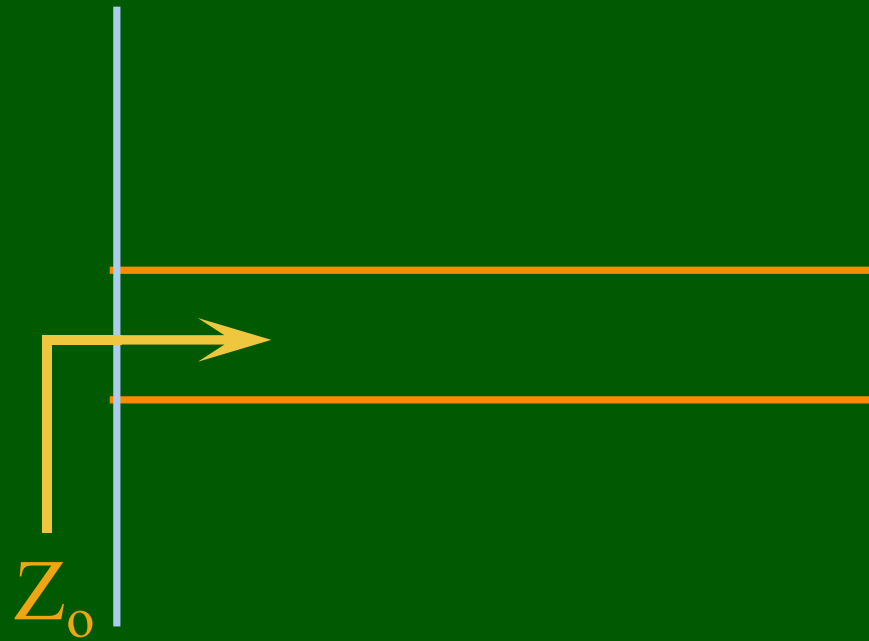


REFLECTION PROBLEM

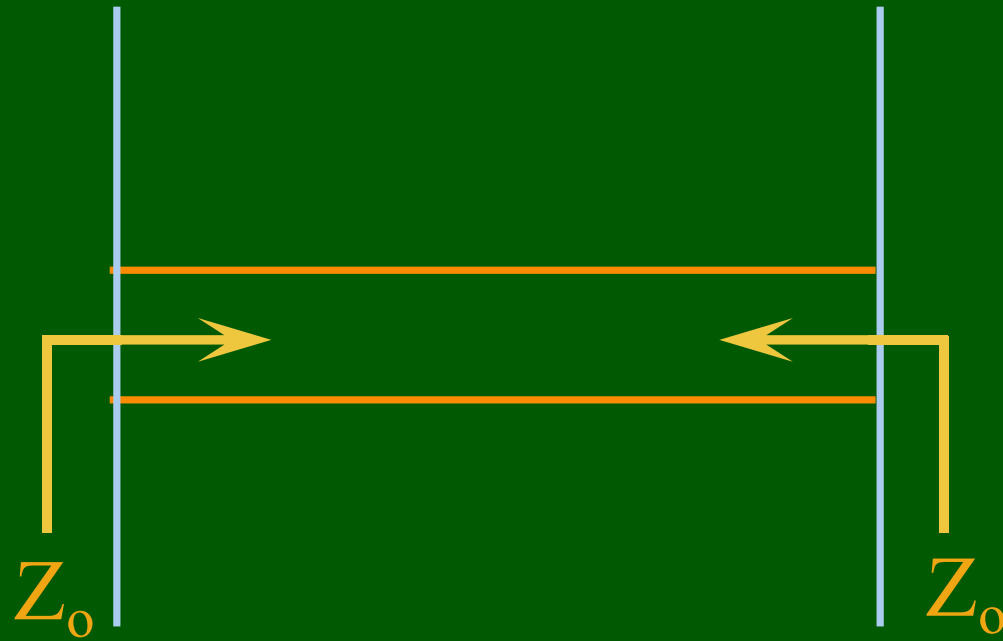


REFLECTION PROBLEM

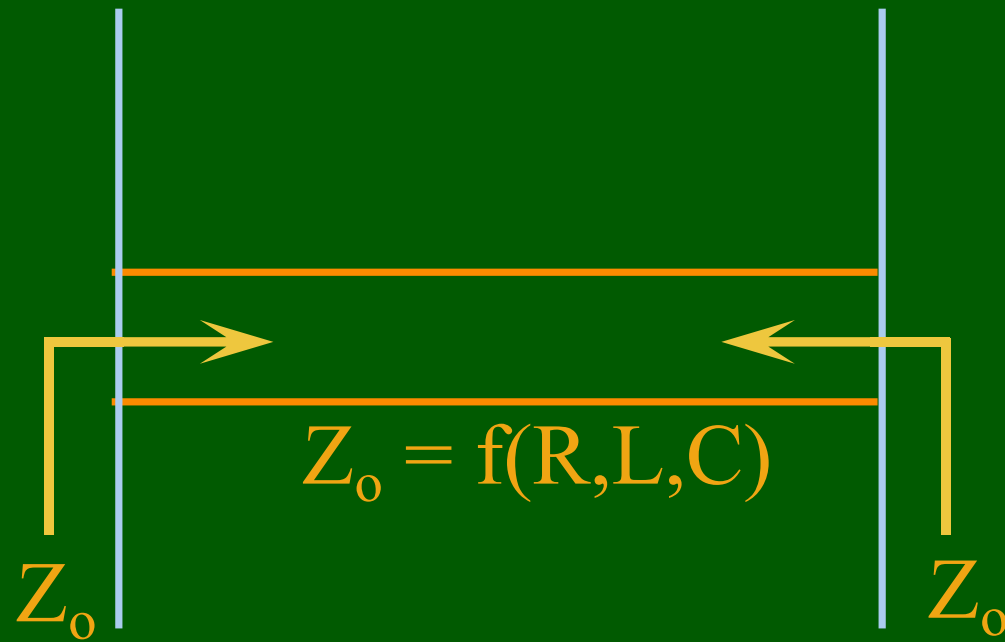


REFLECTION PROBLEM

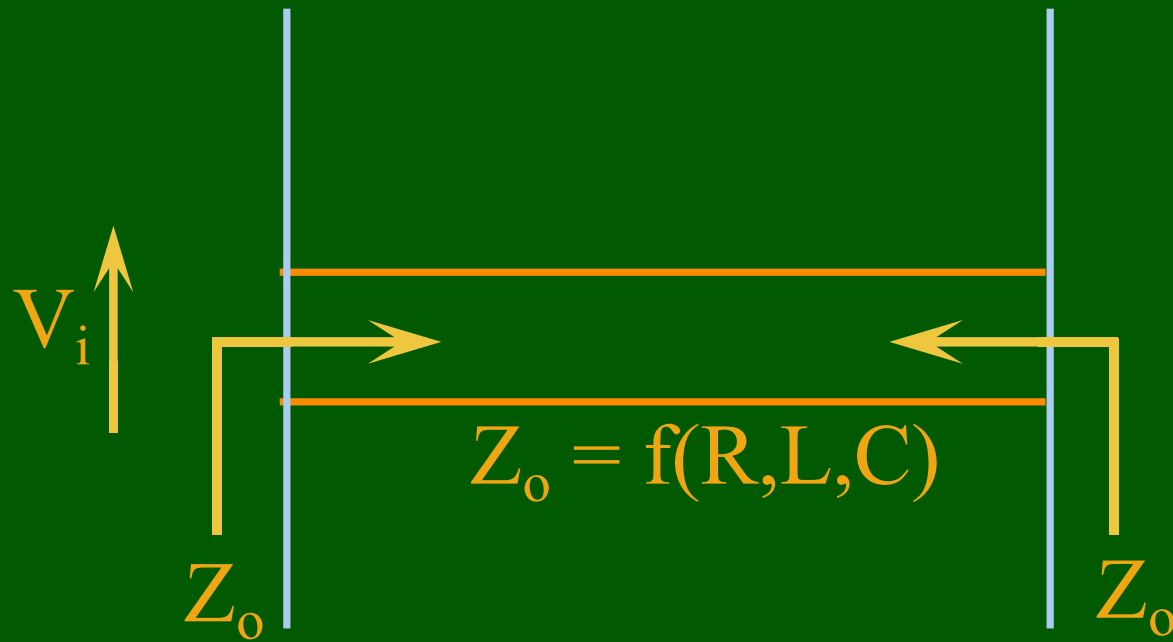


REFLECTION PROBLEM

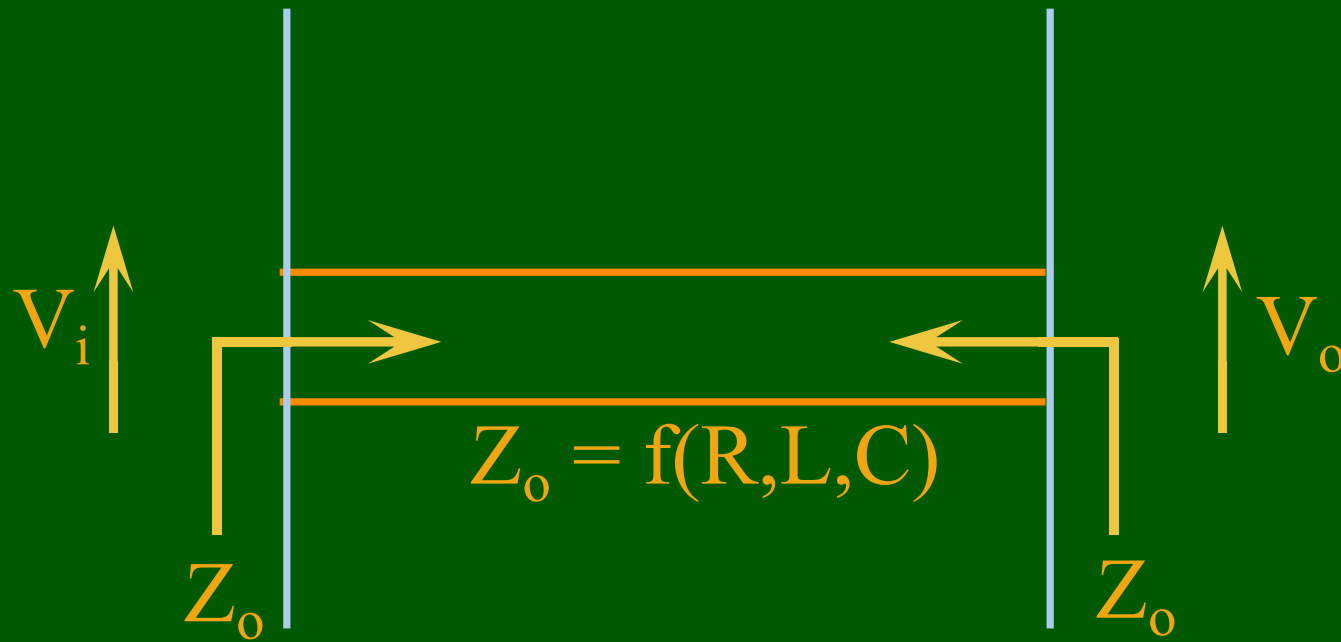


REFLECTION PROBLEM

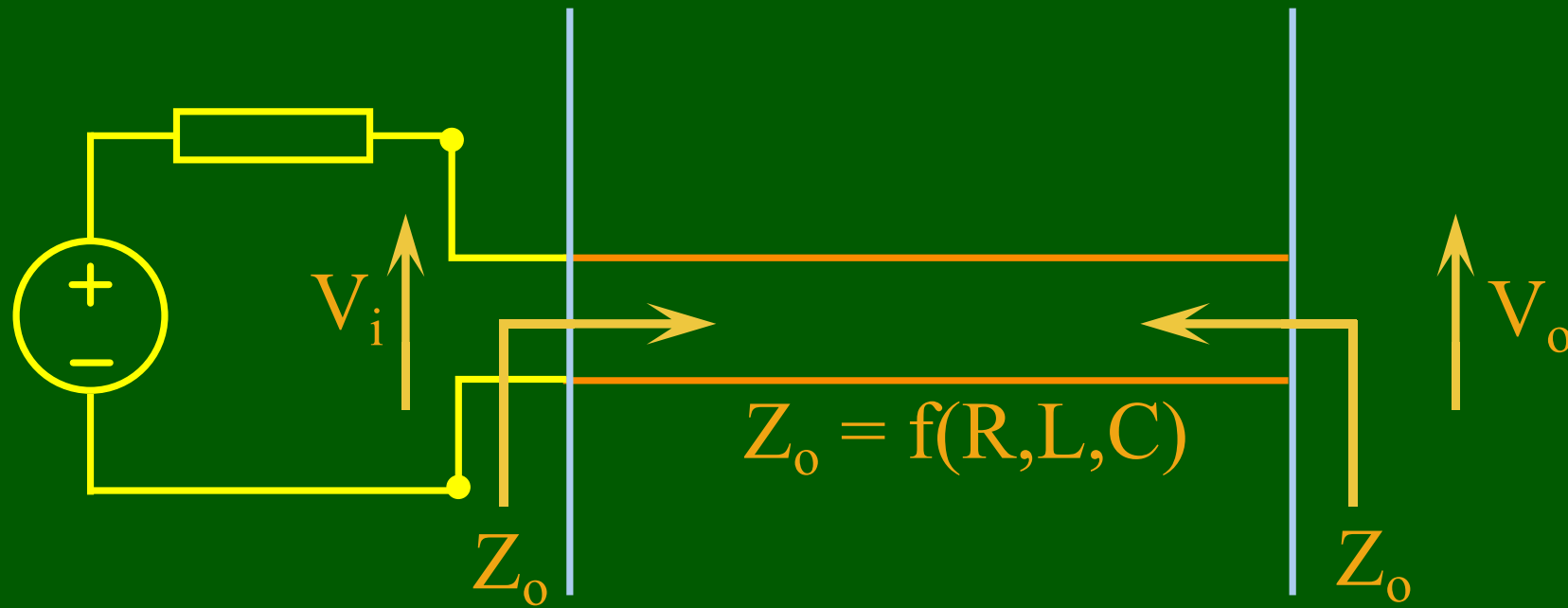


REFLECTION PROBLEM

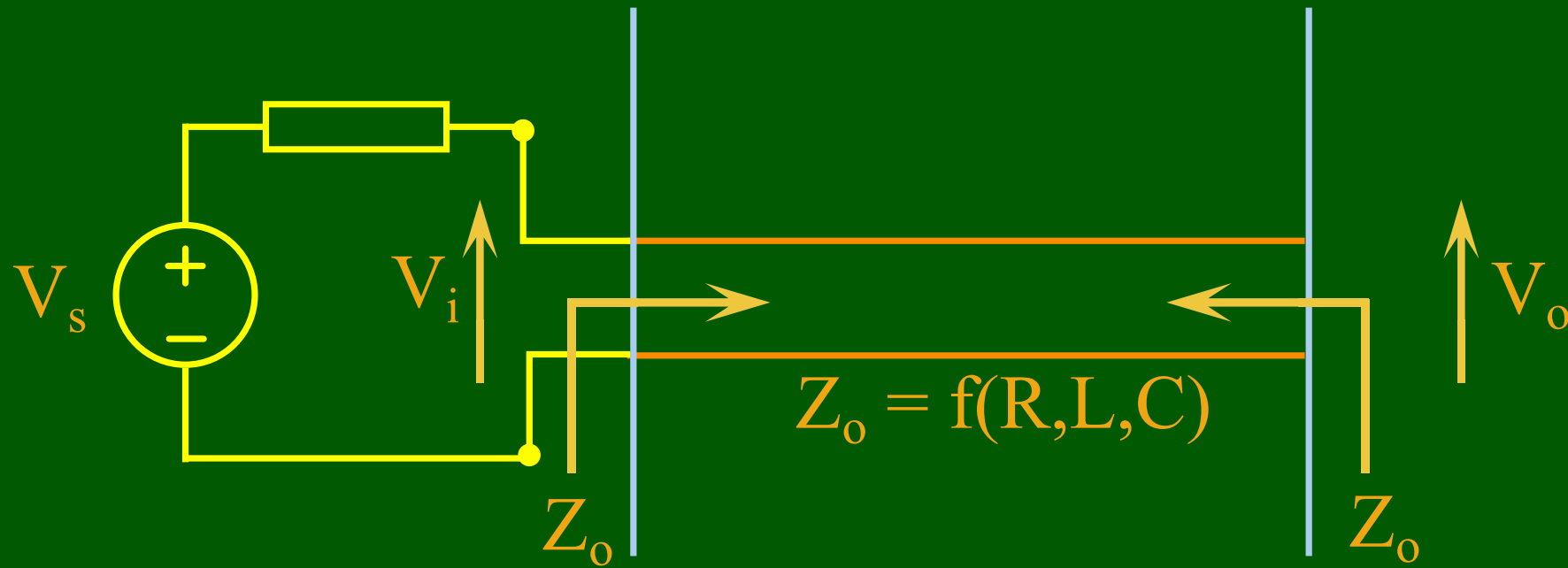


REFLECTION PROBLEM

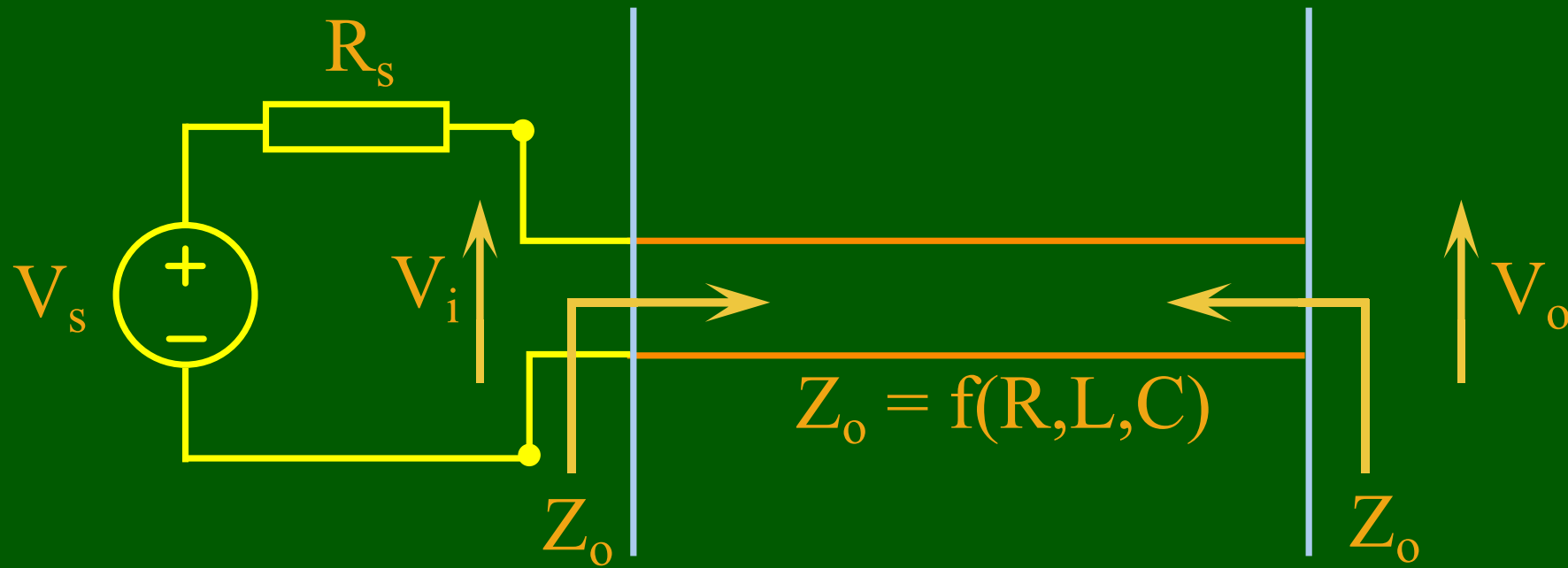


REFLECTION PROBLEM

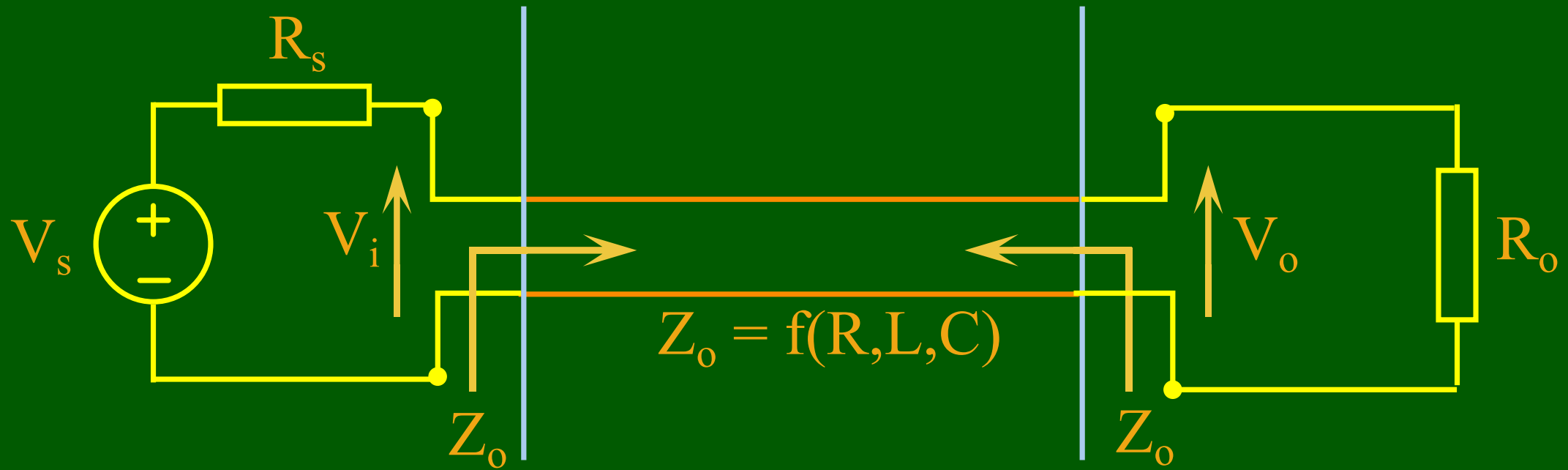

REFLECTION PROBLEM

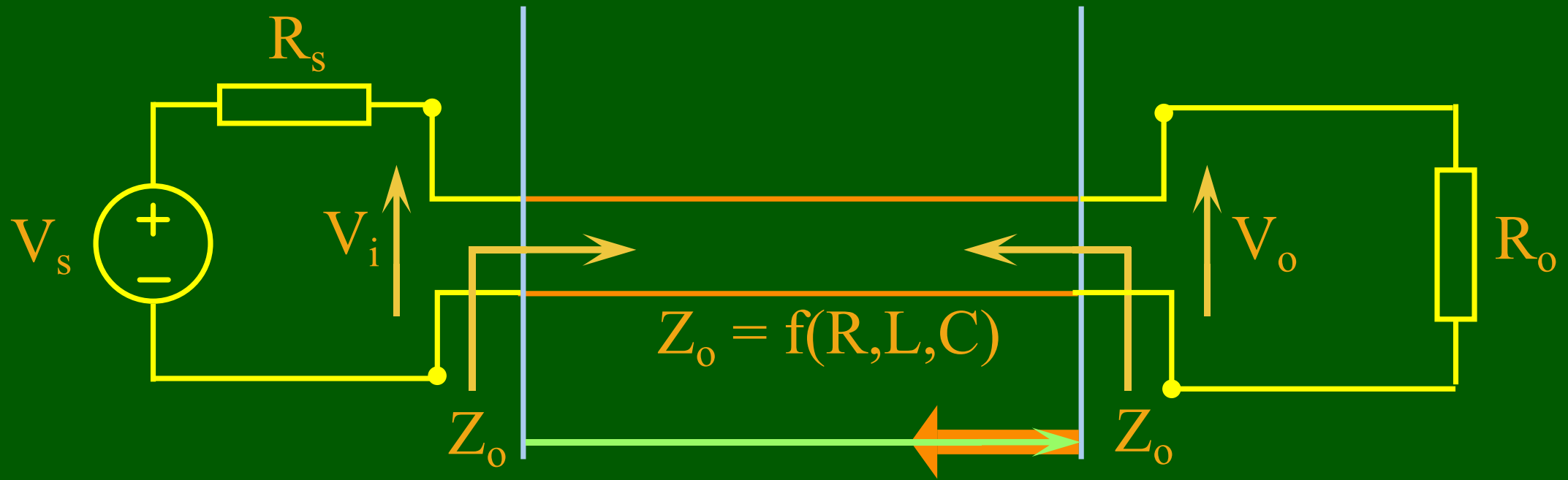


REFLECTION PROBLEM

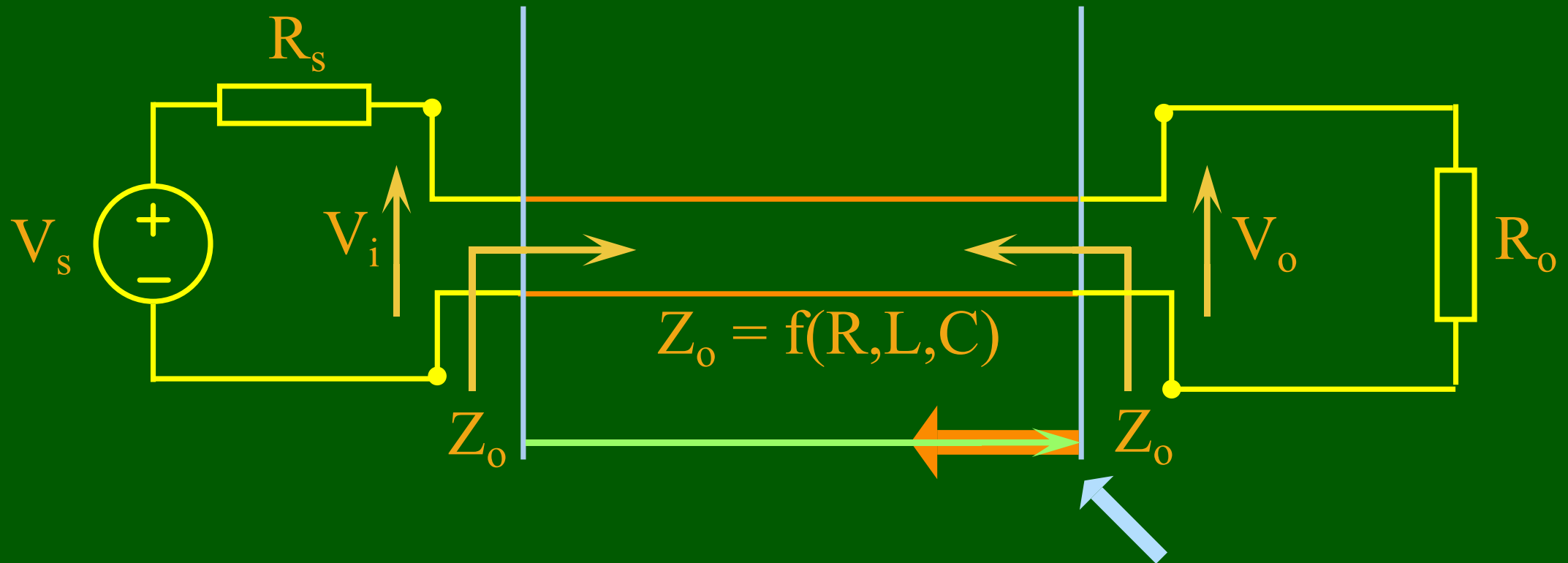


Coefficient of reflection

REFLECTION PROBLEM

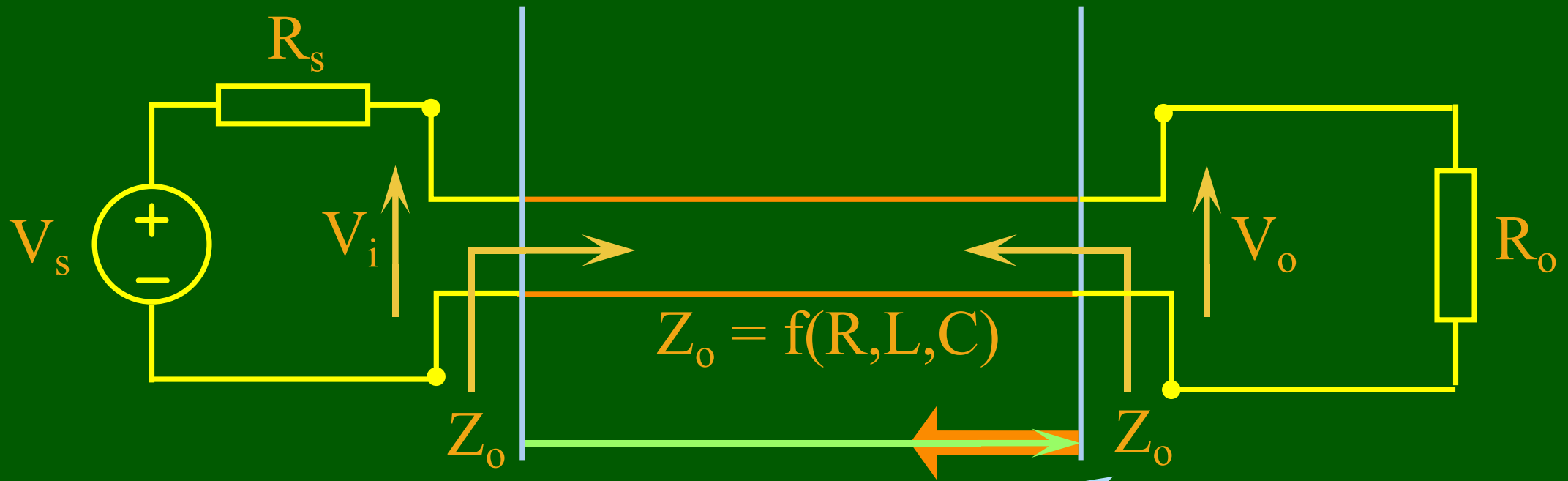

$$\rho_o = \left(\frac{R_o - Z_o}{R_o + Z_o} \right) \text{Coefficient of reflection}$$


REFLECTION PROBLEM

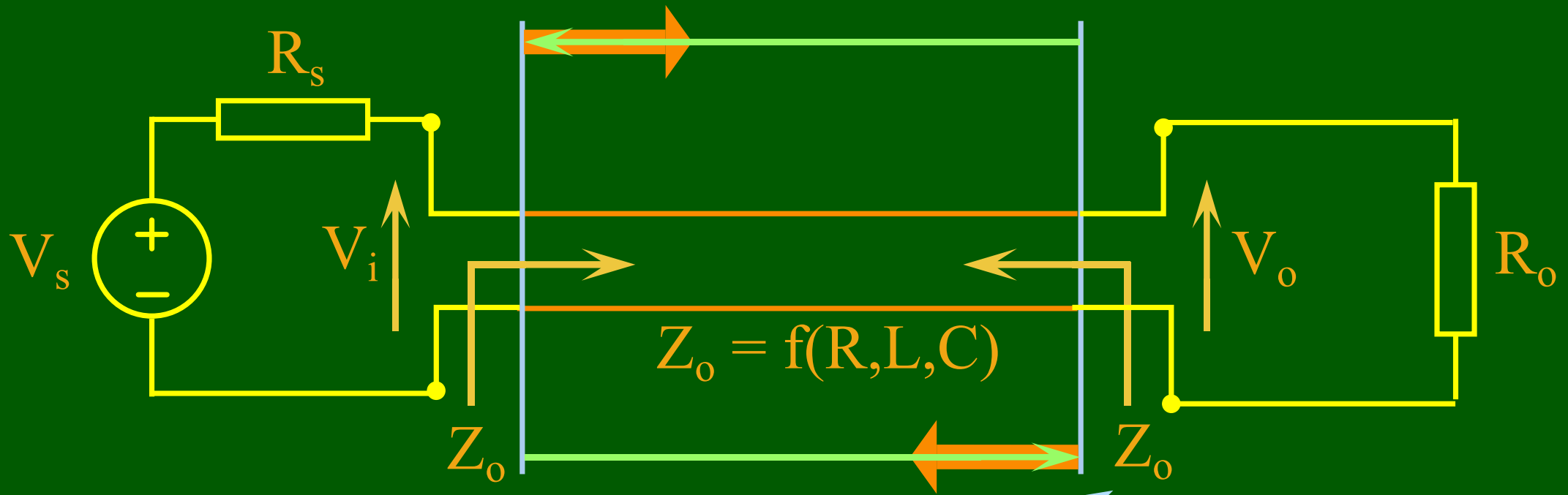

$$\rho_o = \left(\frac{R_o - Z_o}{R_o + Z_o} \right) \text{Coefficient of reflection}$$

REFLECTION PROBLEM
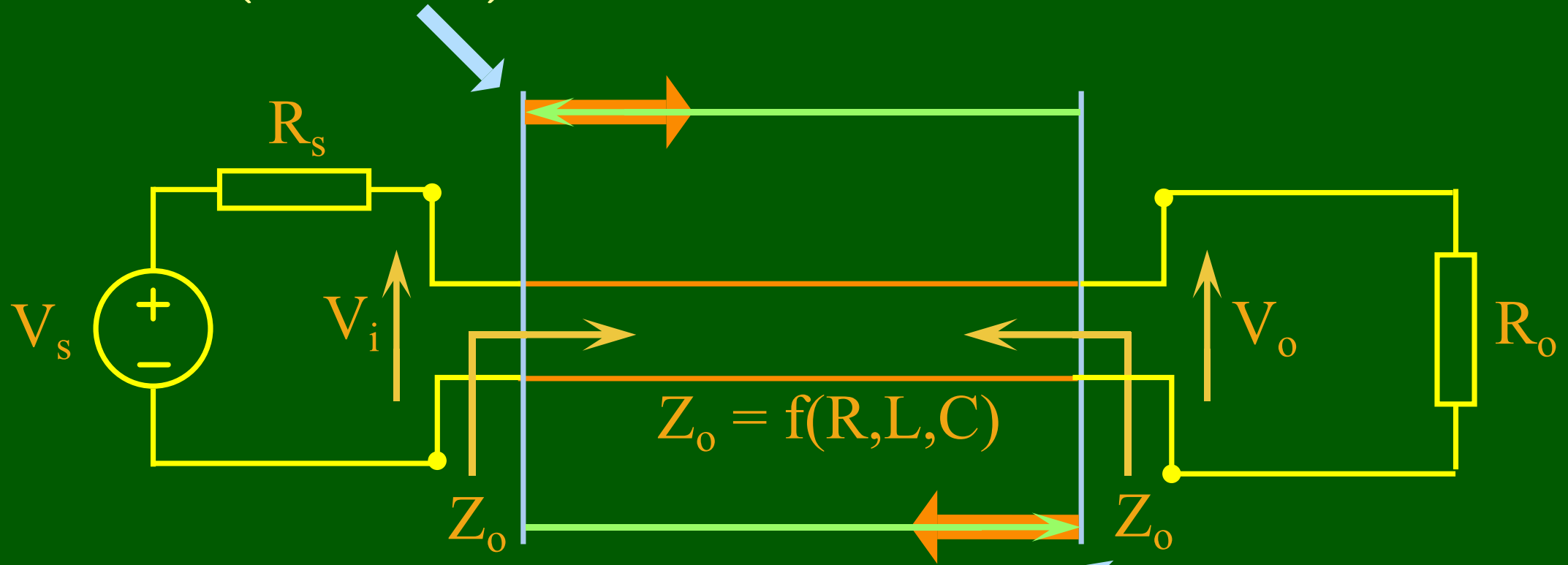
$$\rho_s = \left(\frac{R_s - Z_o}{R_s + Z_o} \right)$$



$$\rho_o = \left(\frac{R_o - Z_o}{R_o + Z_o} \right) \text{ Coefficient of reflection}$$

REFLECTION PROBLEM

REFLECTION PROBLEM

● $R_o = 300$ ohms

● $Z_o = 50$ ohms

● $R_s = 25$ ohms

REFLECTION PROBLEM

● $R_o = 300 \text{ ohms}$

● $Z_o = 50 \text{ ohms}$

● $R_s = 25 \text{ ohms}$

● $V_s = 3.6\text{V (TTL)}$

REFLECTION PROBLEM

● $R_o = 300 \text{ ohms}$

● $Z_o = 50 \text{ ohms}$

● $R_s = 25 \text{ ohms}$

● $V_s = 3.6\text{V (TTL)}$

$$\rho_o = \left(\frac{R_o - Z_o}{R_o + Z_o} \right) = 0.71$$

REFLECTION PROBLEM

● $R_o = 300$ ohms

● $Z_o = 50$ ohms

● $R_s = 25$ ohms

● $V_s = 3.6V$ (TTL)

$$\rho_o = \left(\frac{R_o - Z_o}{R_o + Z_o} \right) = \mathbf{0.71}$$

$$\rho_s = \left(\frac{R_s - Z_o}{R_s + Z_o} \right) = \mathbf{-0.33}$$

REFLECTION PROBLEM

● $R_o = 300$ ohms

● $Z_o = 50$ ohms

● $R_s = 25$ ohms

● $V_s = 3.6V$ (TTL)


$$\rho_o = \left(\frac{R_o - Z_o}{R_o + Z_o} \right) = \mathbf{0.71}$$

$$\rho_s = \left(\frac{R_s - Z_o}{R_s + Z_o} \right) = \mathbf{-0.33}$$


$$V_i = \left(\frac{Z_o}{R_s + Z_o} \right) \cdot V_s = \left(\frac{50}{50 + 25} \right) \cdot 3.6 = \mathbf{2.4V}$$




V_i

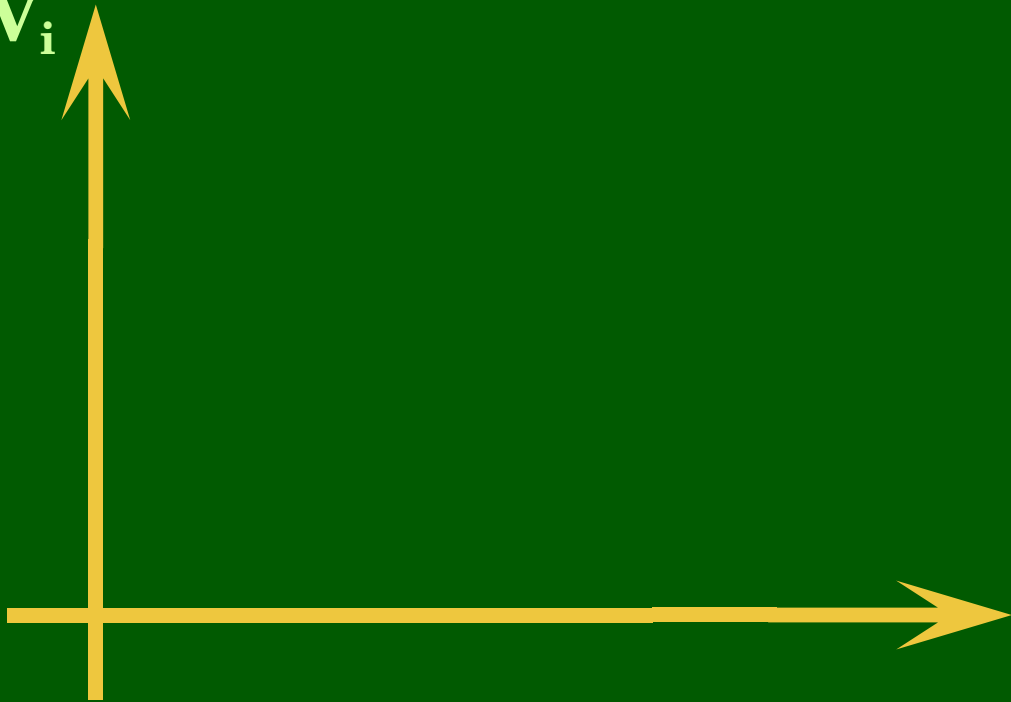


V_i

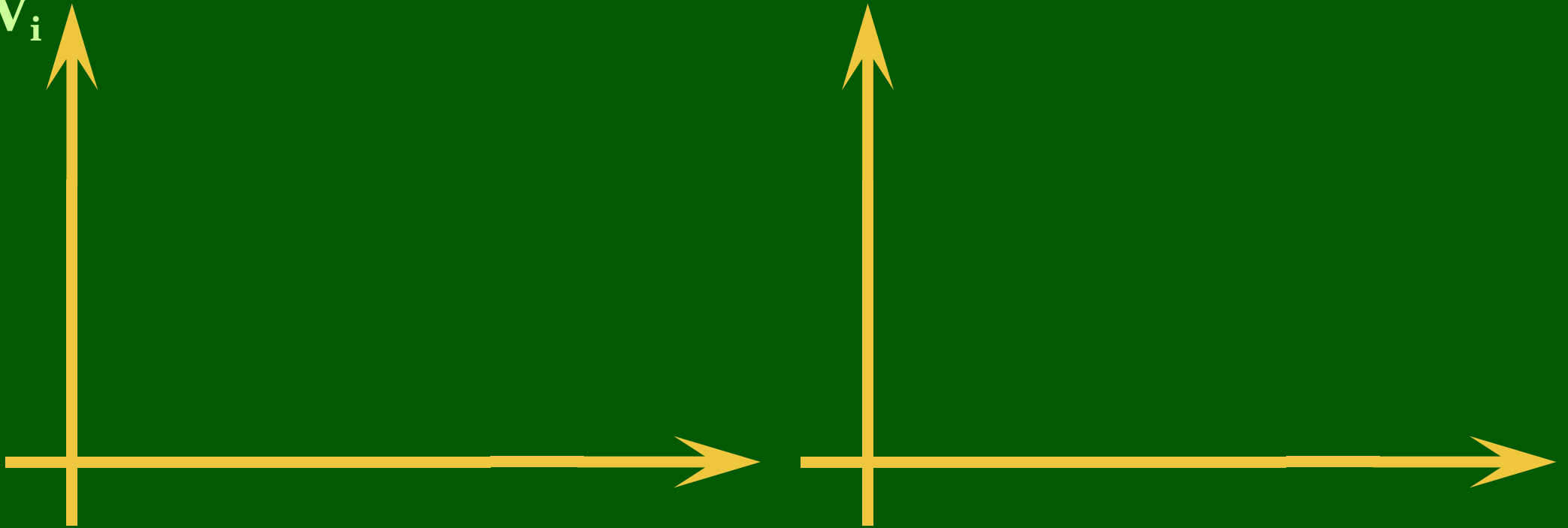




V_i

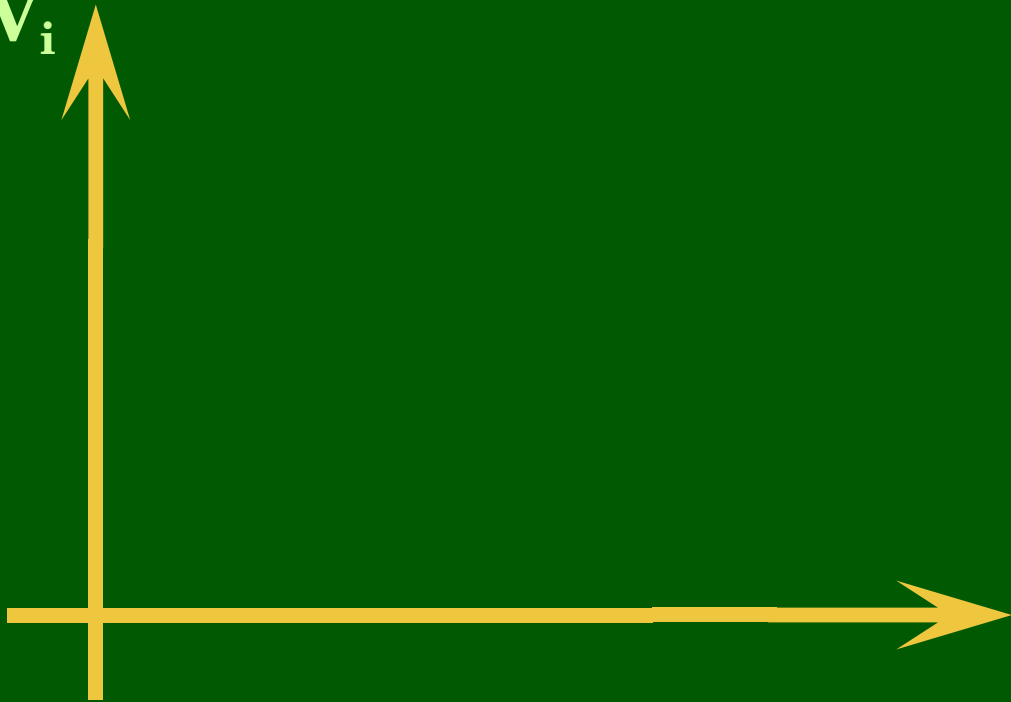




V_o

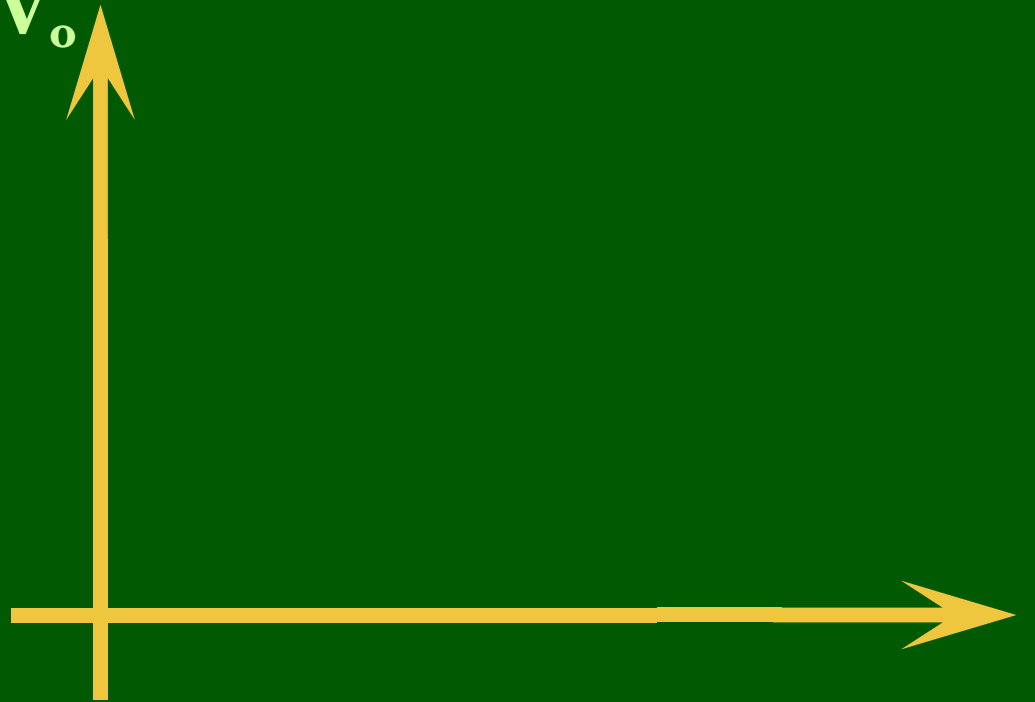

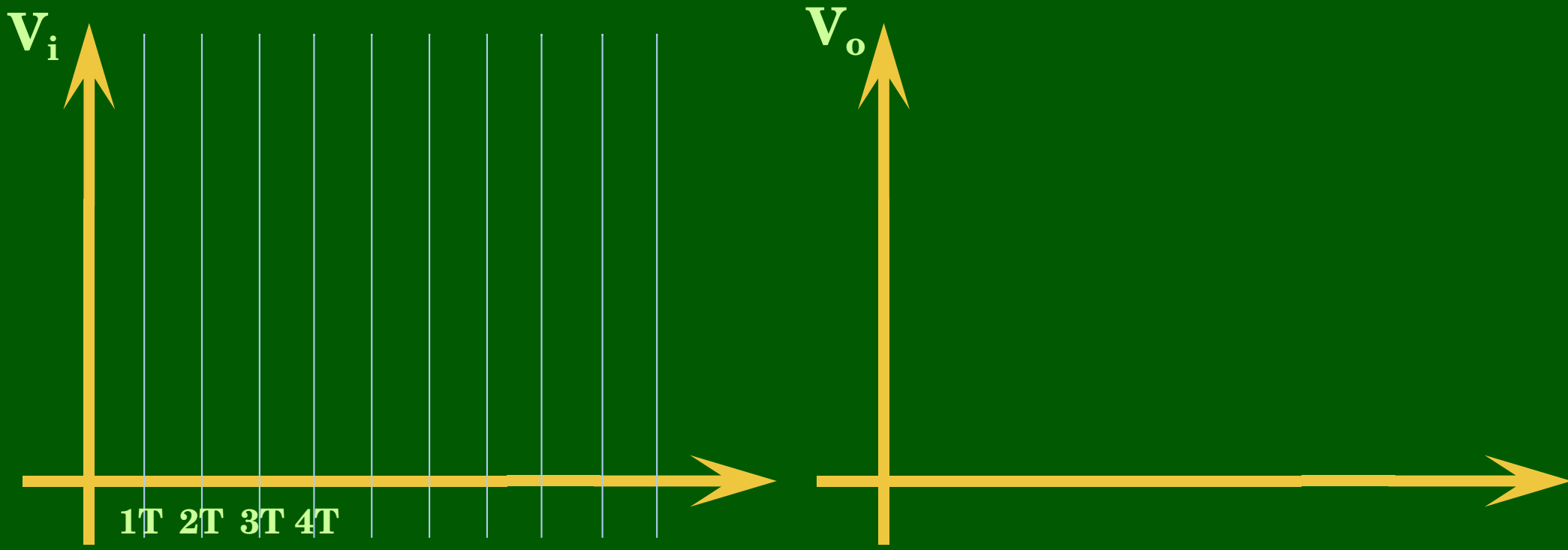

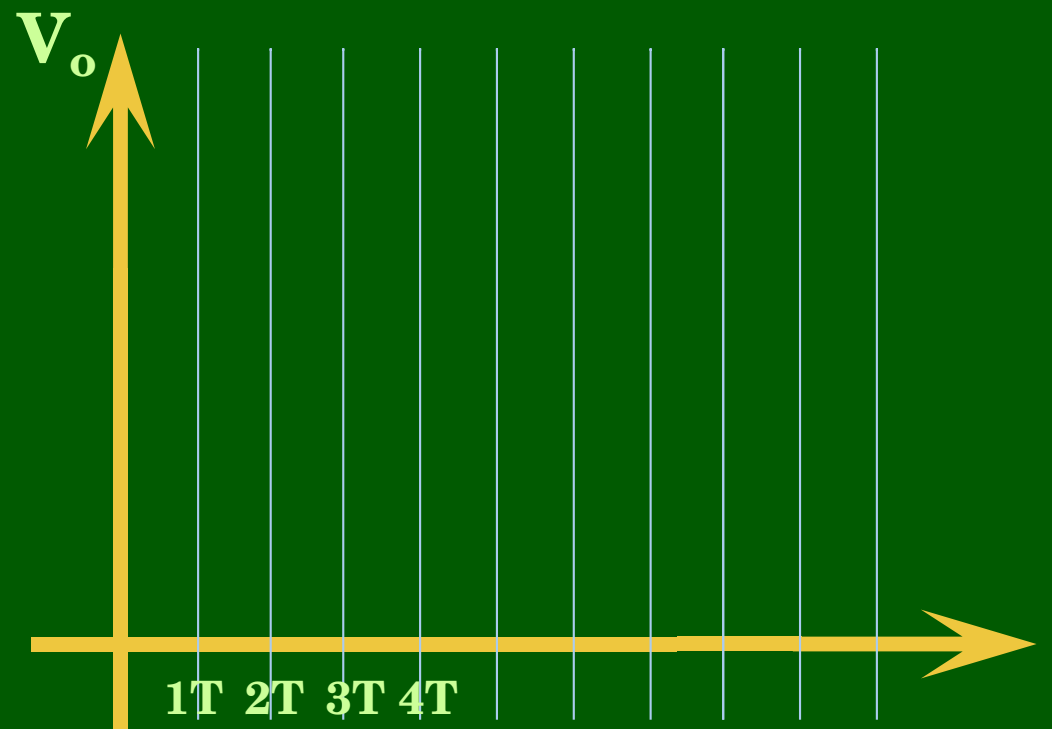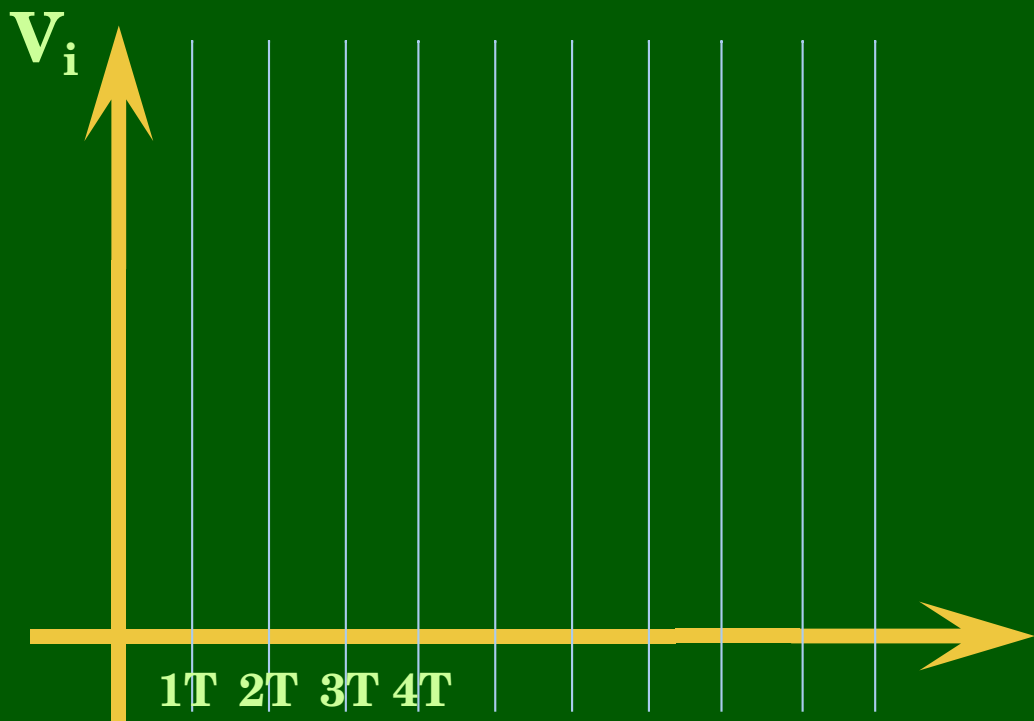


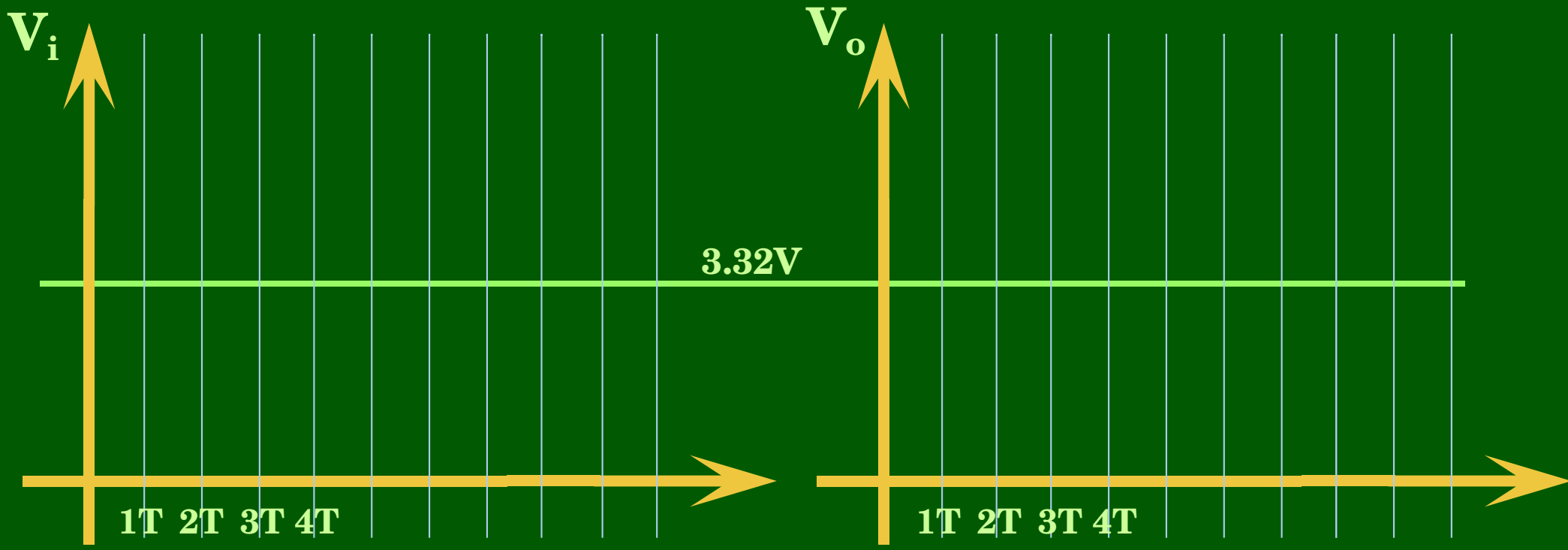

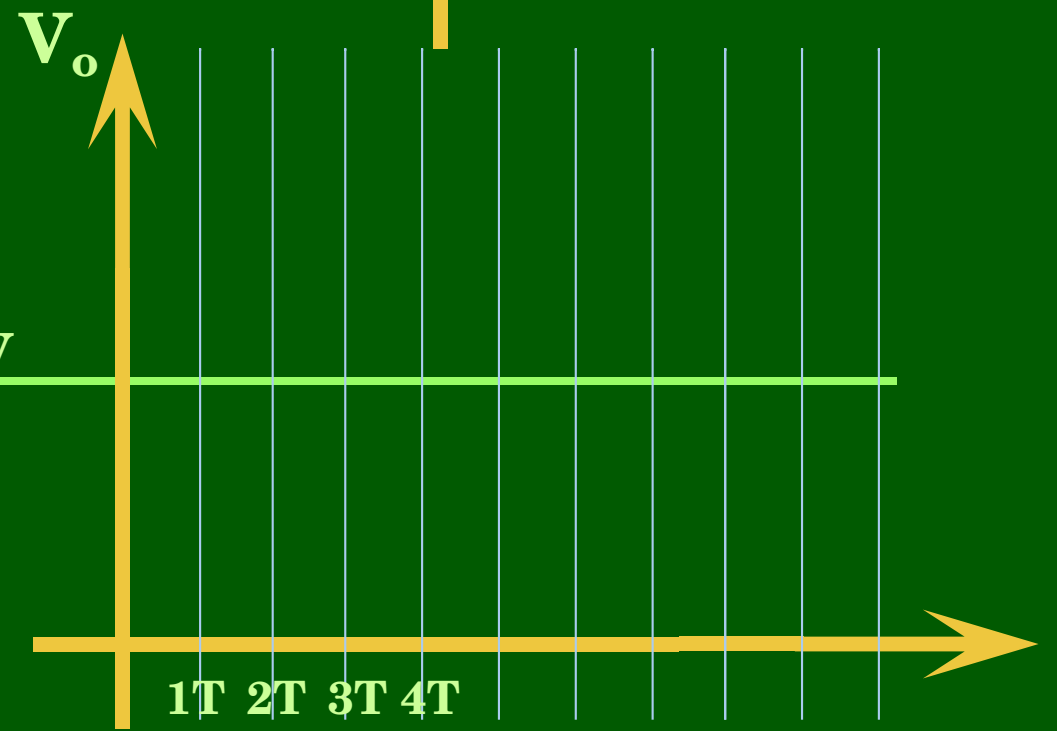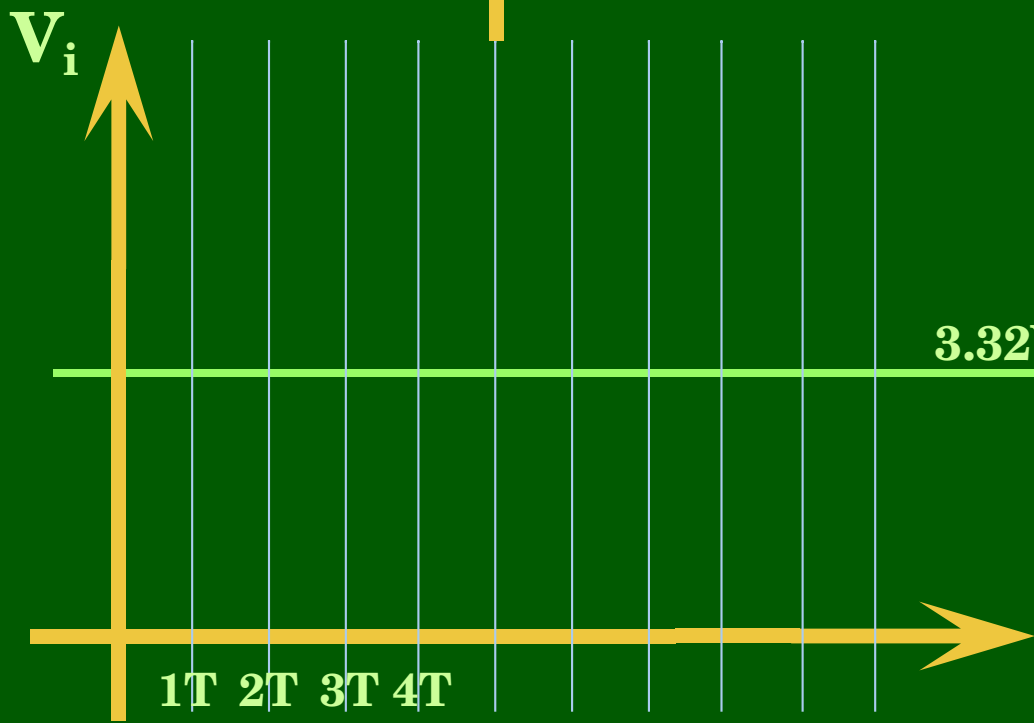

$$\rho_s = -0.33$$


$$\rho_o = 0.71$$

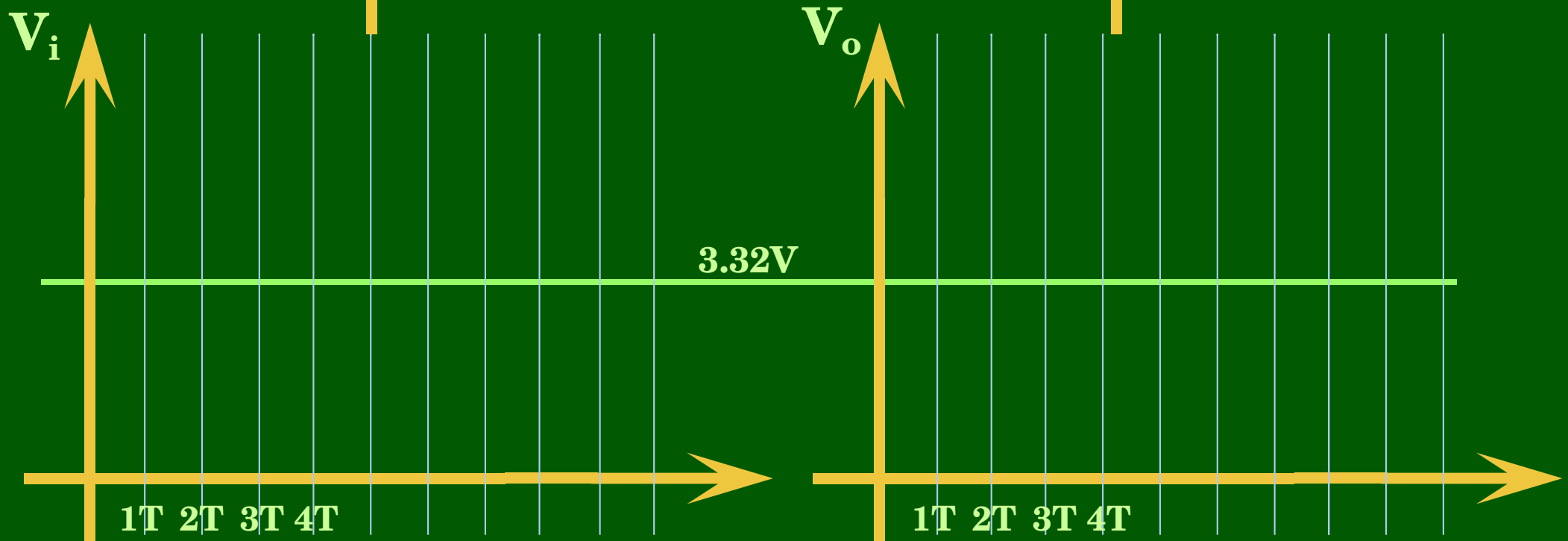

$$\rho_s = -0.33$$

2.4V 0T


$$\rho_o = 0.71$$

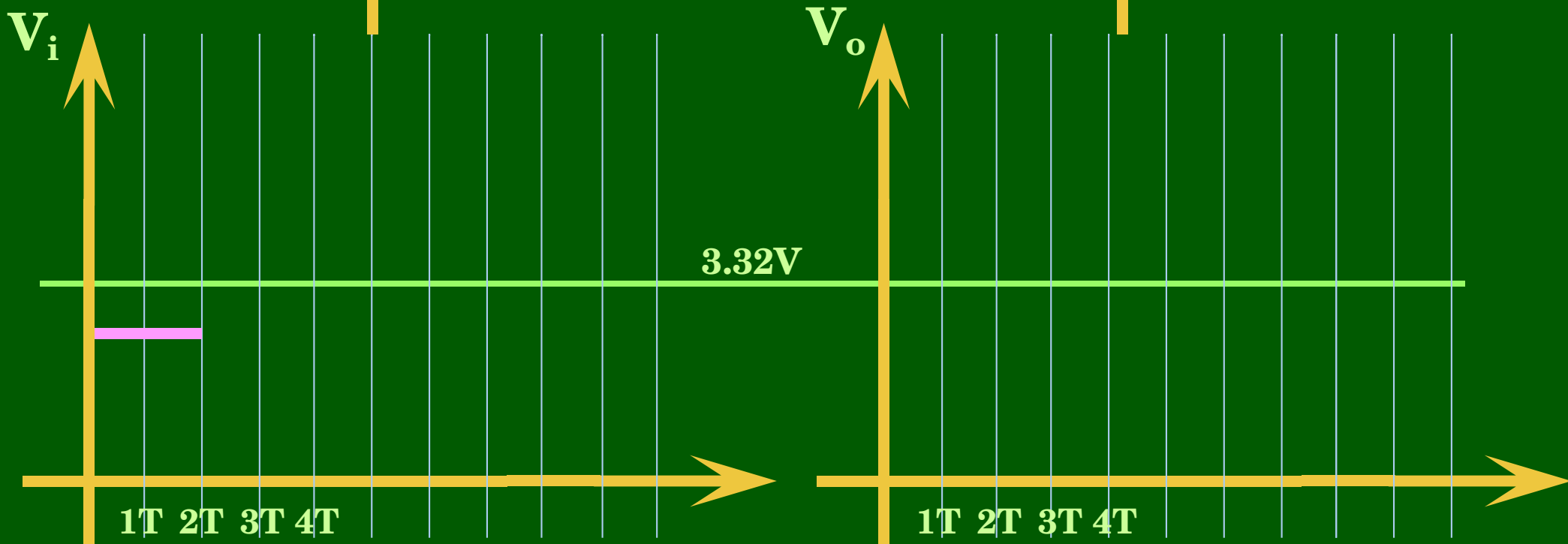

$\rho_s = -0.33$
2.4V 0T

$\rho_o = 0.71$
1T



2.4

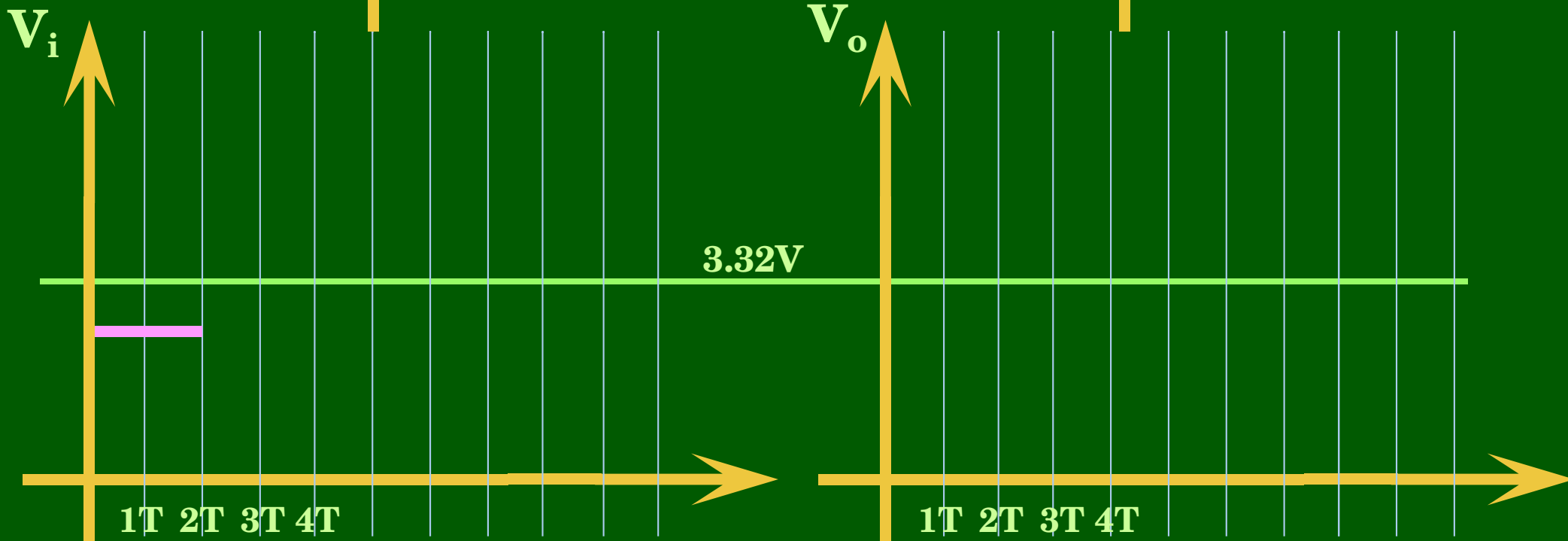

$$\rho_s = -0.33$$

2.4V 0T

$$\rho_o = 0.71$$

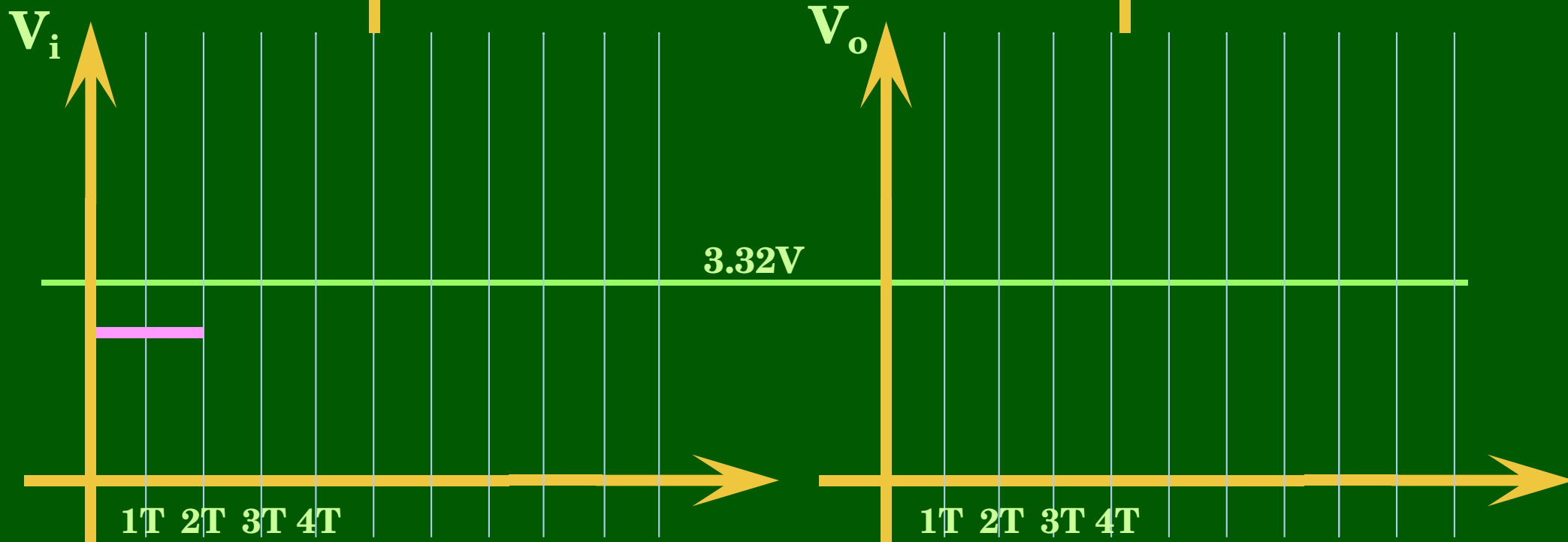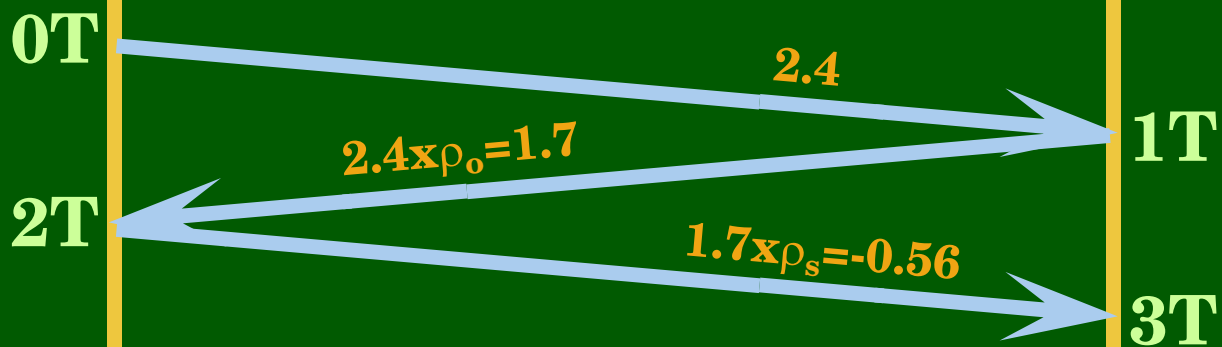

$$\rho_s = -0.33$$

$$\rho_o = 0.71$$

2.4V 0T

2.4

$2.4 \times \rho_o = 1.7$

1T

2T

$1.7 \times \rho_s = -0.56$

3T

4T

$-0.56 \times \rho_o = -0.40$


V_i

V_o

3.32V

1T 2T 3T 4T

1T 2T 3T 4T

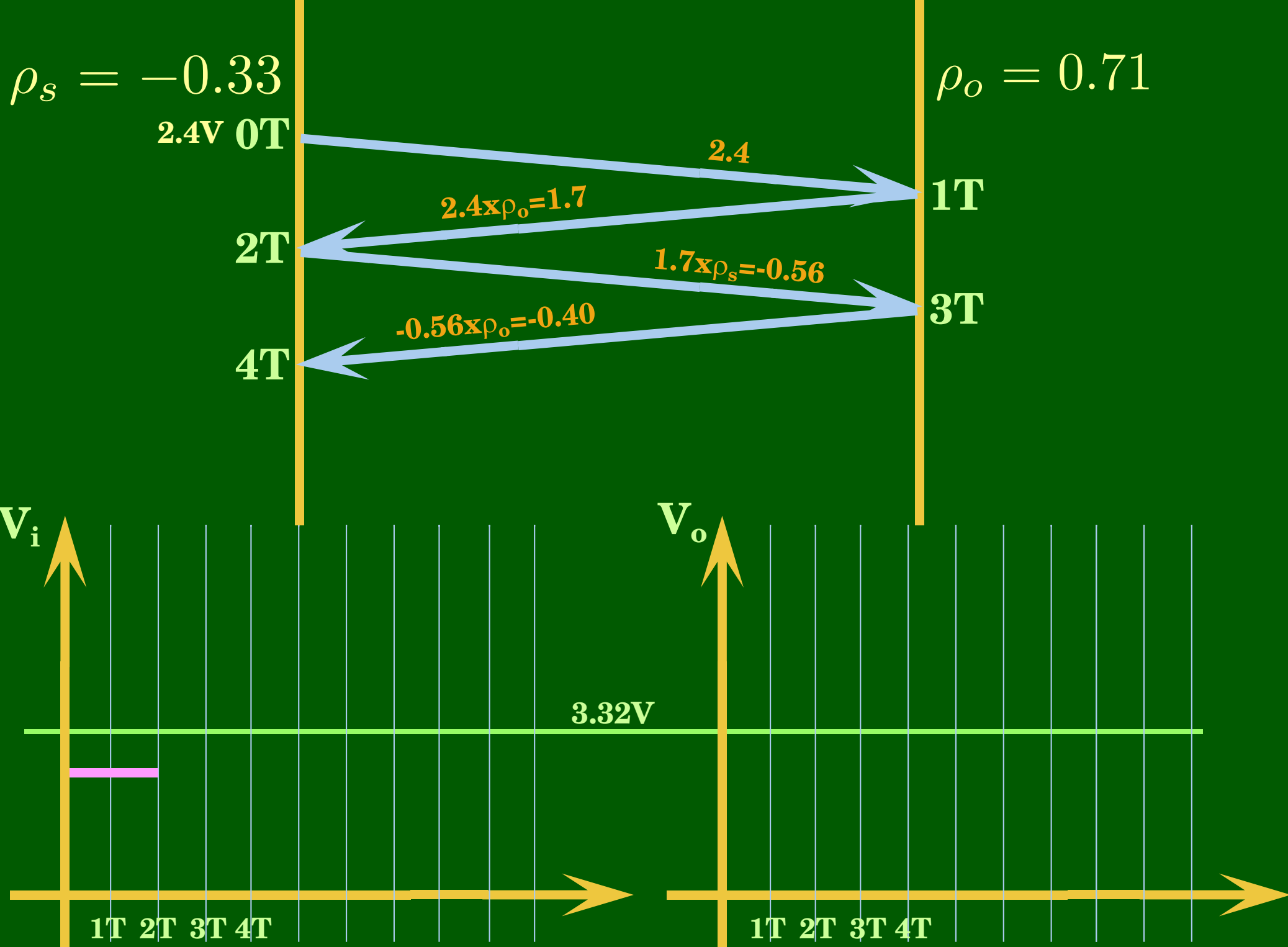

$$\rho_s = -0.33$$

$$\rho_o = 0.71$$

2.4V 0T

2.4

$2.4 \times \rho_o = 1.7$

1T

2T

$1.7 \times \rho_s = -0.56$

3T

4T

$-0.56 \times \rho_o = -0.40$

$-0.4 \times \rho_s = 0.13$

5T


V_i

V_o

3.32V

1T 2T 3T 4T

1T 2T 3T 4T

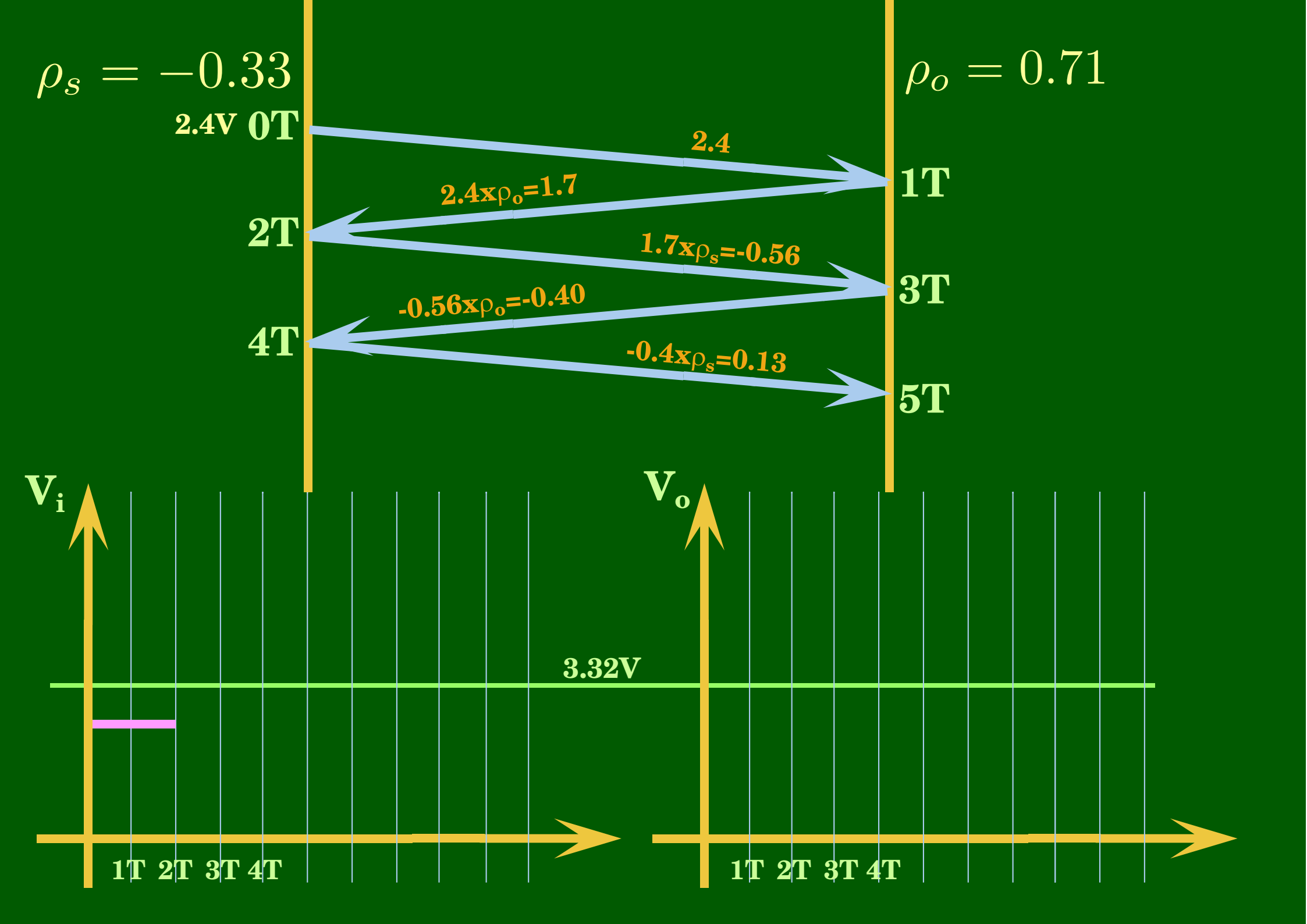

$$\rho_s = -0.33$$

$$\rho_o = 0.71$$

2.4V 0T

2.4

$$2.4 \times \rho_o = 1.7$$

1T

2T

$$1.7 \times \rho_s = -0.56$$

3T

4T

$$-0.56 \times \rho_o = -0.40$$

$$-0.4 \times \rho_s = 0.13$$

5T

6T

$$0.13 \times \rho_o = 0.09$$


V_i

V_o

3.32V

1T 2T 3T 4T

1T 2T 3T 4T

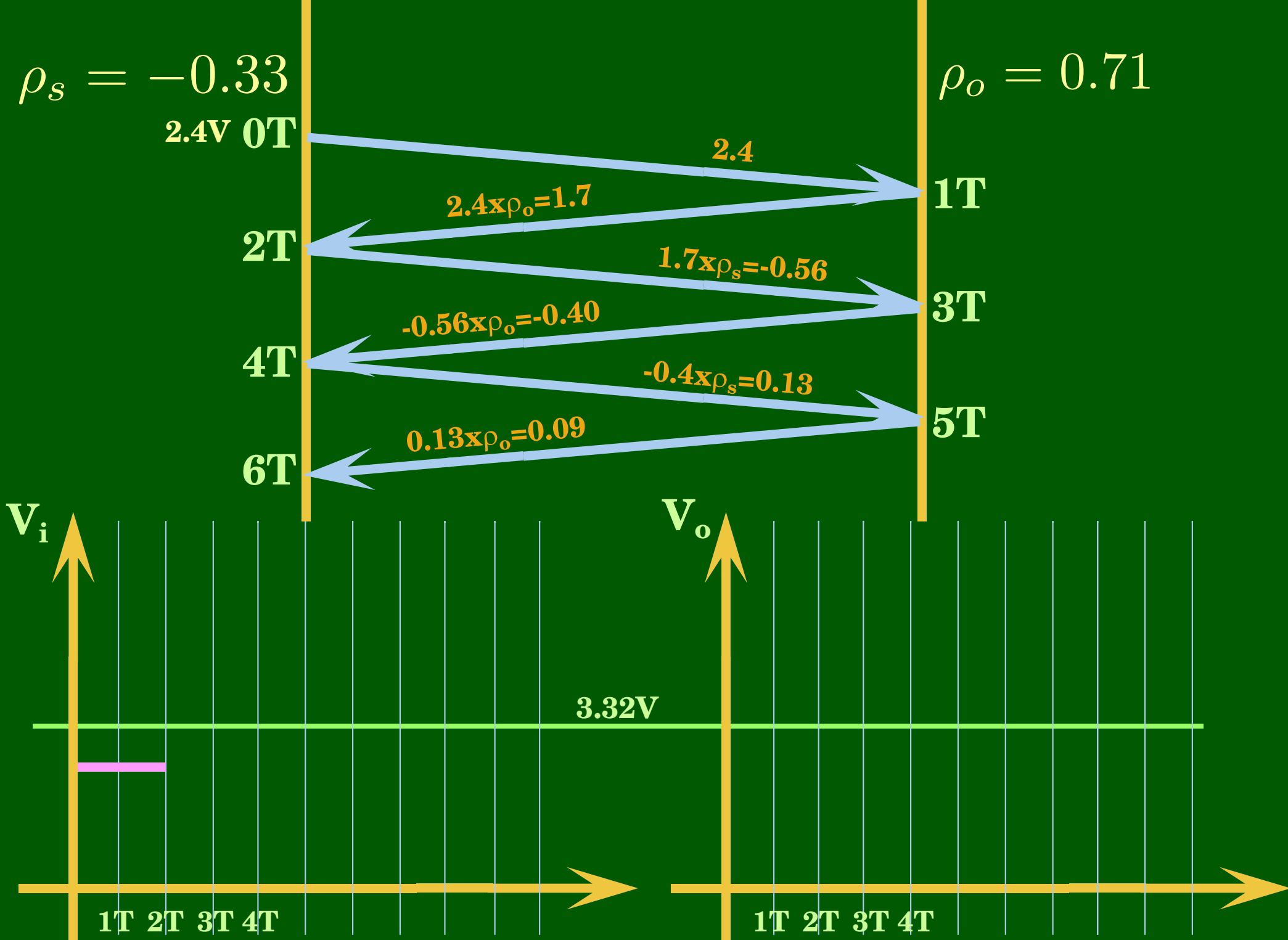

$$\rho_s = -0.33$$

$$\rho_o = 0.71$$

2.4V 0T

2.4

$$2.4 \times \rho_o = 1.7$$

1T 2.4+1.7=4.1V

2T

$$1.7 \times \rho_s = -0.56$$

3T

$$-0.56 \times \rho_o = -0.40$$

4T

$$-0.4 \times \rho_s = 0.13$$

5T

$$0.13 \times \rho_o = 0.09$$

6T


V_i

V_o

3.32V

1T 2T 3T 4T

1T 2T 3T 4T

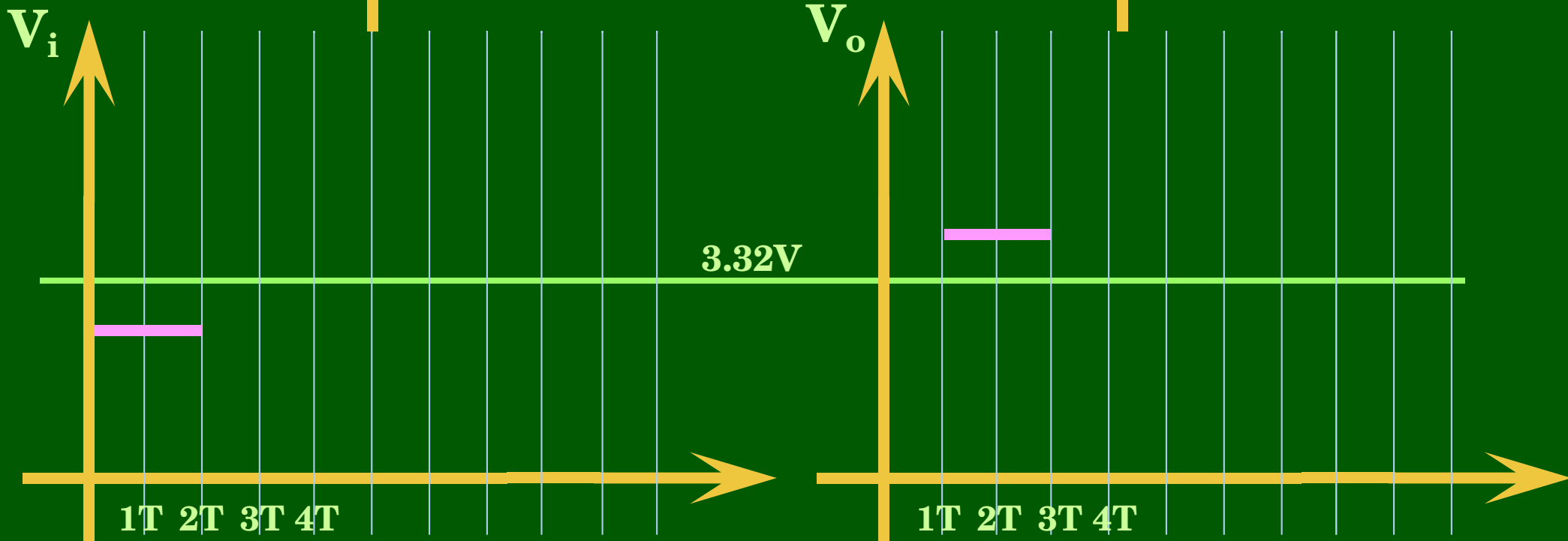

$$\rho_s = -0.33$$

$$\rho_o = 0.71$$

2.4V 0T

2.4

$$2.4 \times \rho_o = 1.7$$

1T 2.4+1.7=4.1V

$$2.4 + 1.7 - 0.56 = 3.54V$$

2T

$$1.7 \times \rho_s = -0.56$$

3T

$$-0.56 \times \rho_o = -0.40$$

4T

$$-0.4 \times \rho_s = 0.13$$

5T

$$0.13 \times \rho_o = 0.09$$

6T


V_i

V_o

3.32V

1T 2T 3T 4T

1T 2T 3T 4T

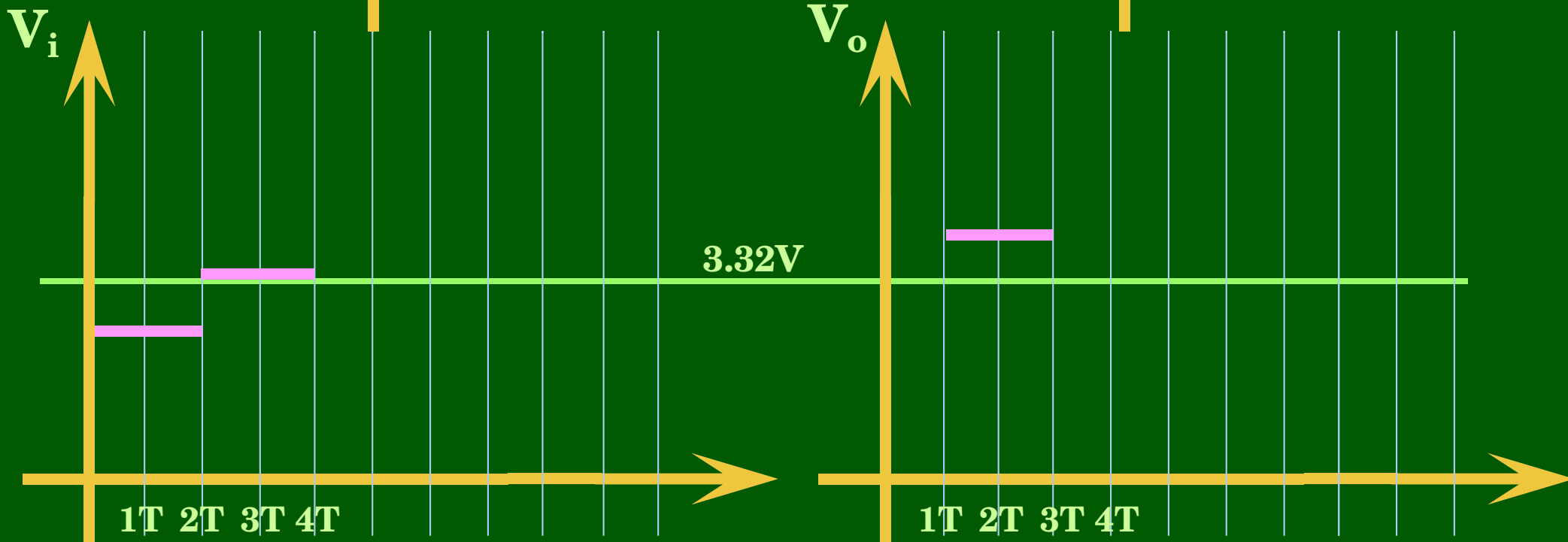

$$\rho_s = -0.33$$

$$\rho_o = 0.71$$

2.4V 0T

2.4

$$2.4 \times \rho_o = 1.7$$

1T 2.4+1.7=4.1V

$$2.4 + 1.7 - 0.56 = 3.54V$$

2T

$$1.7 \times \rho_s = -0.56$$

$$-0.56 \times \rho_o = -0.40$$

3T 4.1 - 4.1 \times 0.7 \times 0.33 = 4.1 - 0.96 = 3.14V


4T

$$-0.4 \times \rho_s = 0.13$$

5T

$$0.13 \times \rho_o = 0.09$$

6T

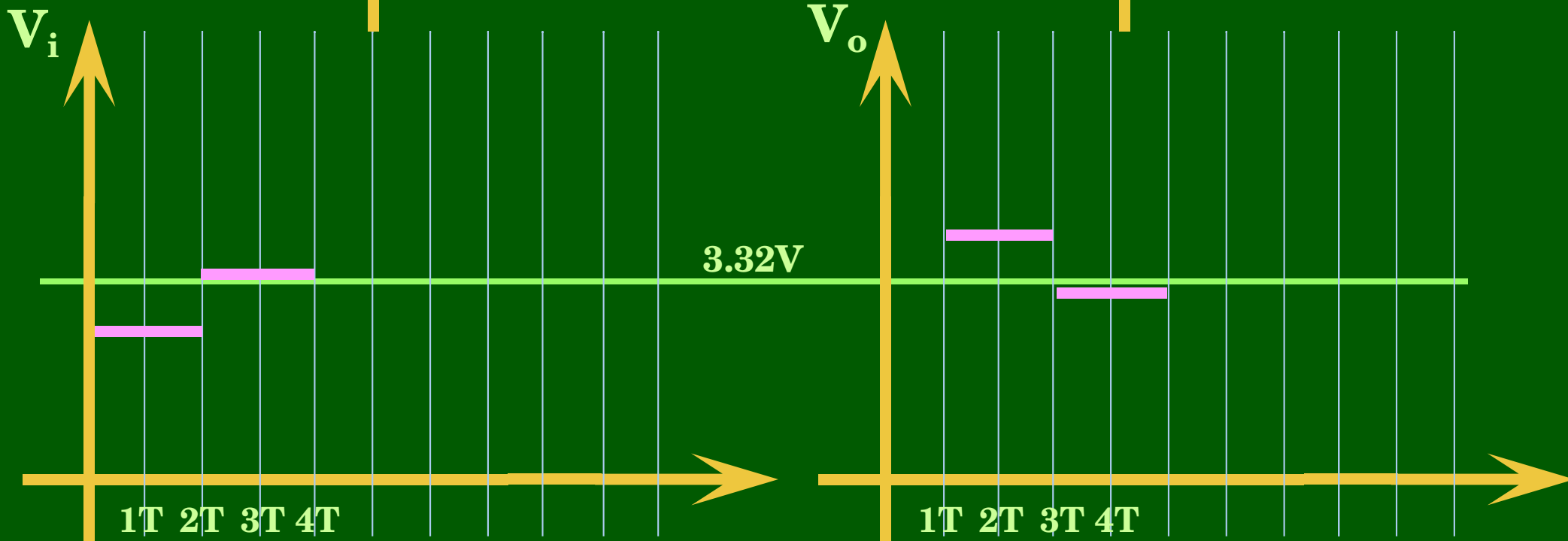

$$\rho_s = -0.33$$

$$\rho_o = 0.71$$

2.4V 0T

2.4

$$2.4 \times \rho_o = 1.7$$

1T 2.4+1.7=4.1V

2.4+1.7-0.56
=3.54V 2T

$$1.7 \times \rho_s = -0.56$$

3T 4.1-4.1x0.7x0.33
=4.1-0.96=3.14V

$$-0.56 \times \rho_o = -0.40$$


3.54-0.4+0.13
=3.27V 4T

$$-0.4 \times \rho_s = 0.13$$

5T

$$0.13 \times \rho_o = 0.09$$

6T

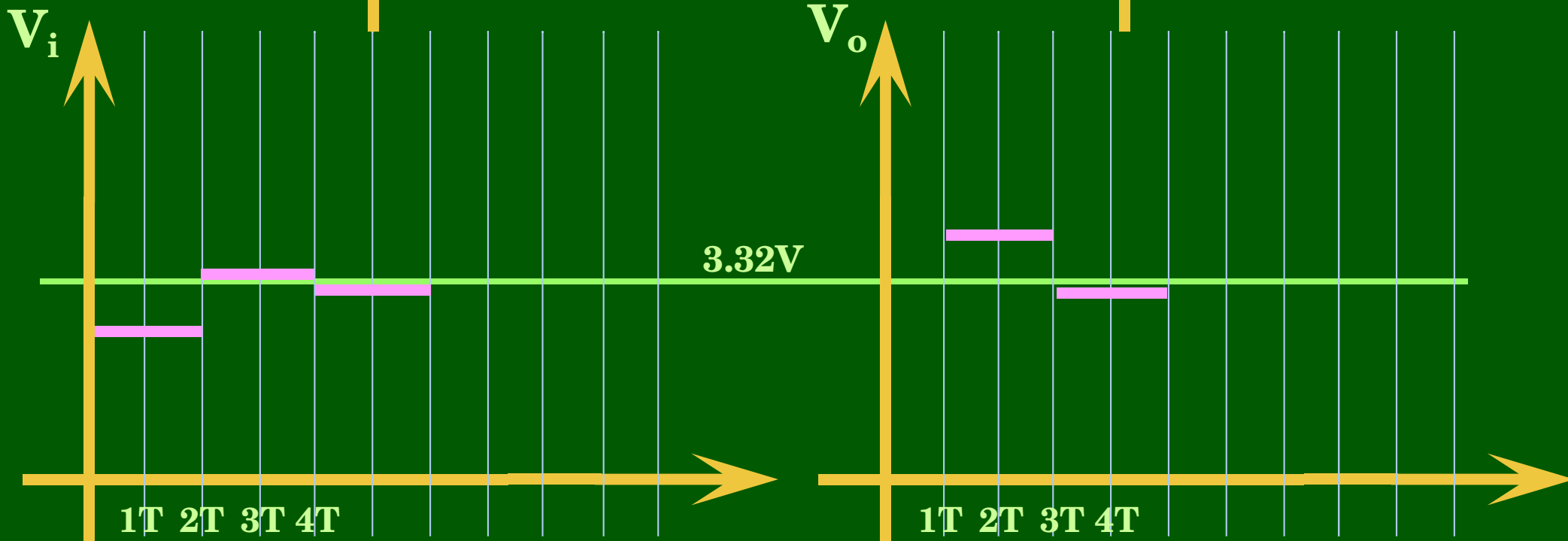

$$\rho_s = -0.33$$

$$\rho_o = 0.71$$

2.4V 0T

2.4

$$2.4 \times \rho_o = 1.7$$

1T 2.4+1.7=4.1V

2.4+1.7-0.56
=3.54V 2T

$$1.7 \times \rho_s = -0.56$$

3T 4.1-4.1x0.7x0.33
=4.1-0.96=3.14V

$$-0.56 \times \rho_o = -0.40$$


3.54-0.4+0.13
=3.27V 4T

$$-0.4 \times \rho_s = 0.13$$

5T 3.14+0.22
=3.36V

$$0.13 \times \rho_o = 0.09$$

6T

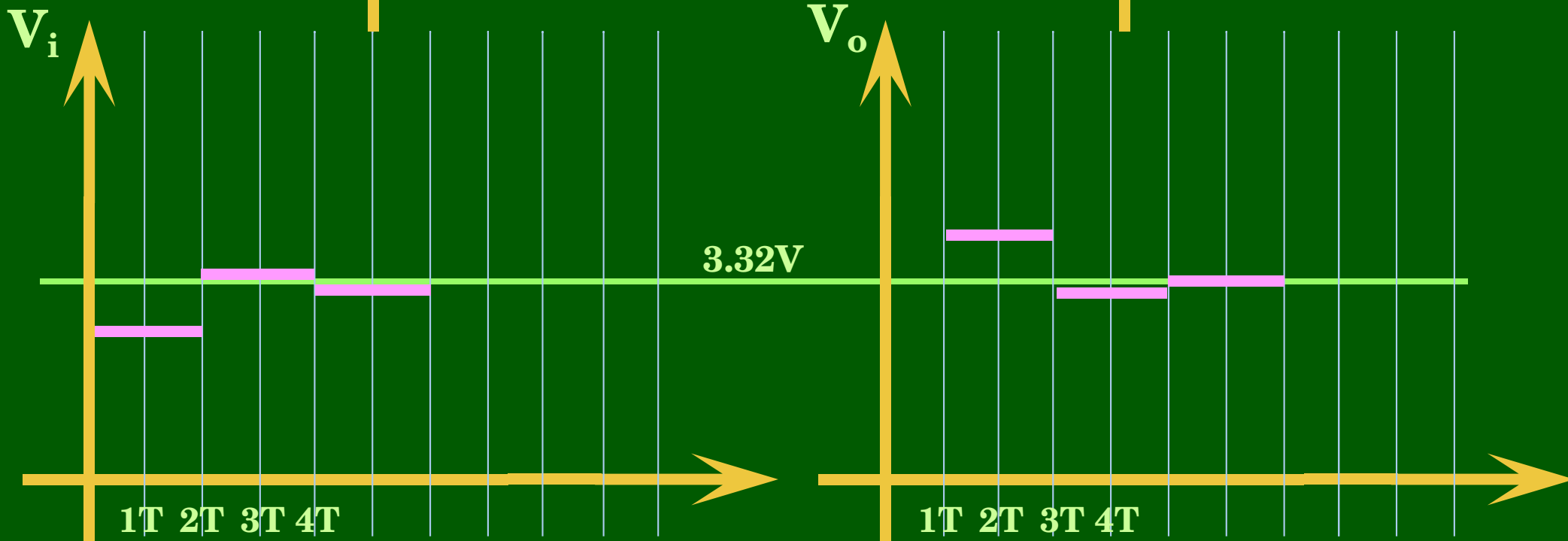

$$\rho_s = -0.33$$

$$\rho_o = 0.71$$

2.4V 0T

2.4

$$2.4 \times \rho_o = 1.7$$

1T 2.4+1.7=4.1V

2.4+1.7-0.56
=3.54V 2T

$$1.7 \times \rho_s = -0.56$$

3T 4.1-4.1x0.7x0.33
=4.1-0.96=3.14V

$$-0.56 \times \rho_o = -0.40$$

3.54-0.4+0.13
=3.27V 4T

$$-0.4 \times \rho_s = 0.13$$

5T 3.14+0.22
=3.36V

$$0.13 \times \rho_o = 0.09$$

6T

