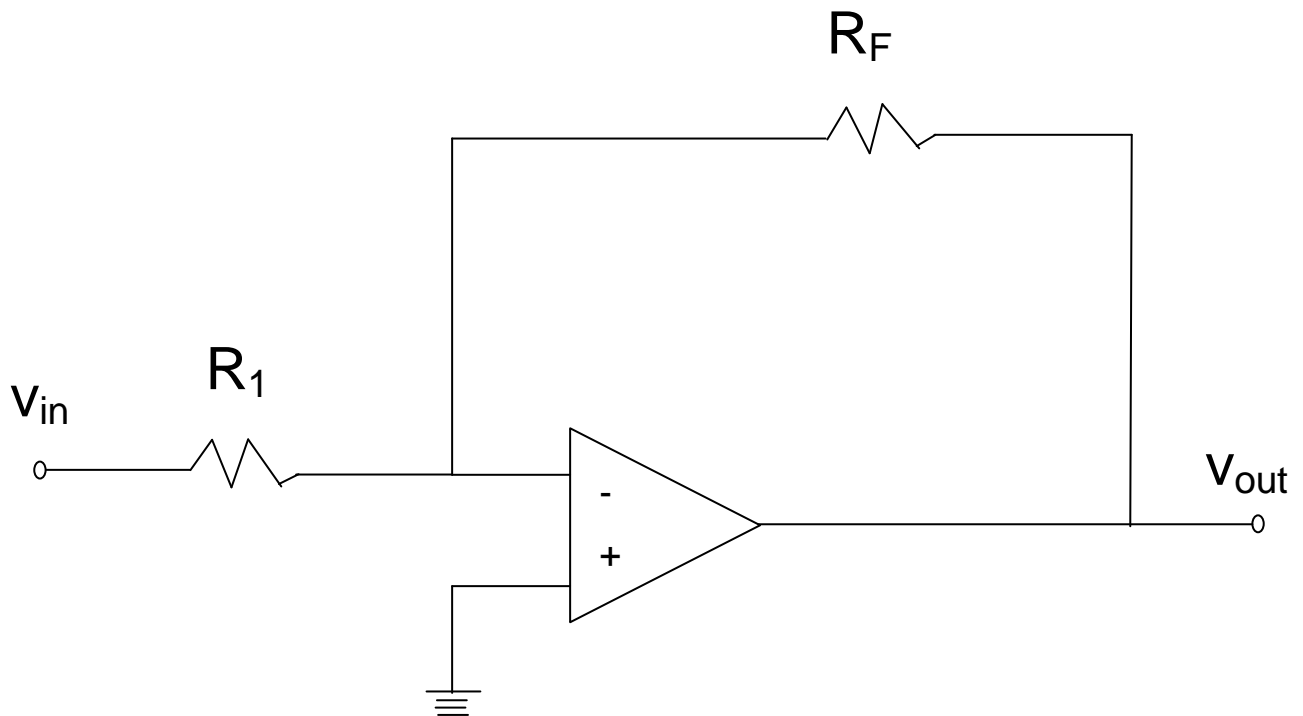


## UNIT – VII

### Operational Amplifiers

- 7.1 The open-loop gain of an op-amp is  $10^5$ . An input signal of 1mv is applied to the inverting input with the non-inverting connected to the ground. The supply voltage is  $\pm 10V$ . The output of the amplifier will be close to,
- (a) + 100V
  - (b) – 100V
  - (c) + 10V
  - (d) – 10V
- 7.2 An op-amp has an open-loop gain of  $10^5$  and an open-loop upper cut-off frequency is 10 Hz. If this op-amp is connected as an amplifier with a closed loop gain of 100, then the new upper cut-off frequency is
- (a) 10 Hz
  - (b) 100 Hz
  - (c) 10 kHz
  - (d) 100 kHz
- 7.3 In the inverting amplifier shown it is desired to realize the input resistance seen by the small signal source to be as large as possible while keeping the voltage gain between -10 and -25. The upper limit of  $R_F$  is 1 M $\Omega$ . The value of  $R_1$  should be,




- (a) Infinity
- (b) 1 M $\Omega$
- (c) 100 k $\Omega$
- (d) 40 k $\Omega$

7.4 In the inverting amplifier shown, The resistance  $R_g$  is chosen as  $R_1 \parallel R_2$  in order to


- (a) Increase gain
- (b) Reduce off set current
- (c) Reduce offset voltage
- (d) Increase CMRR

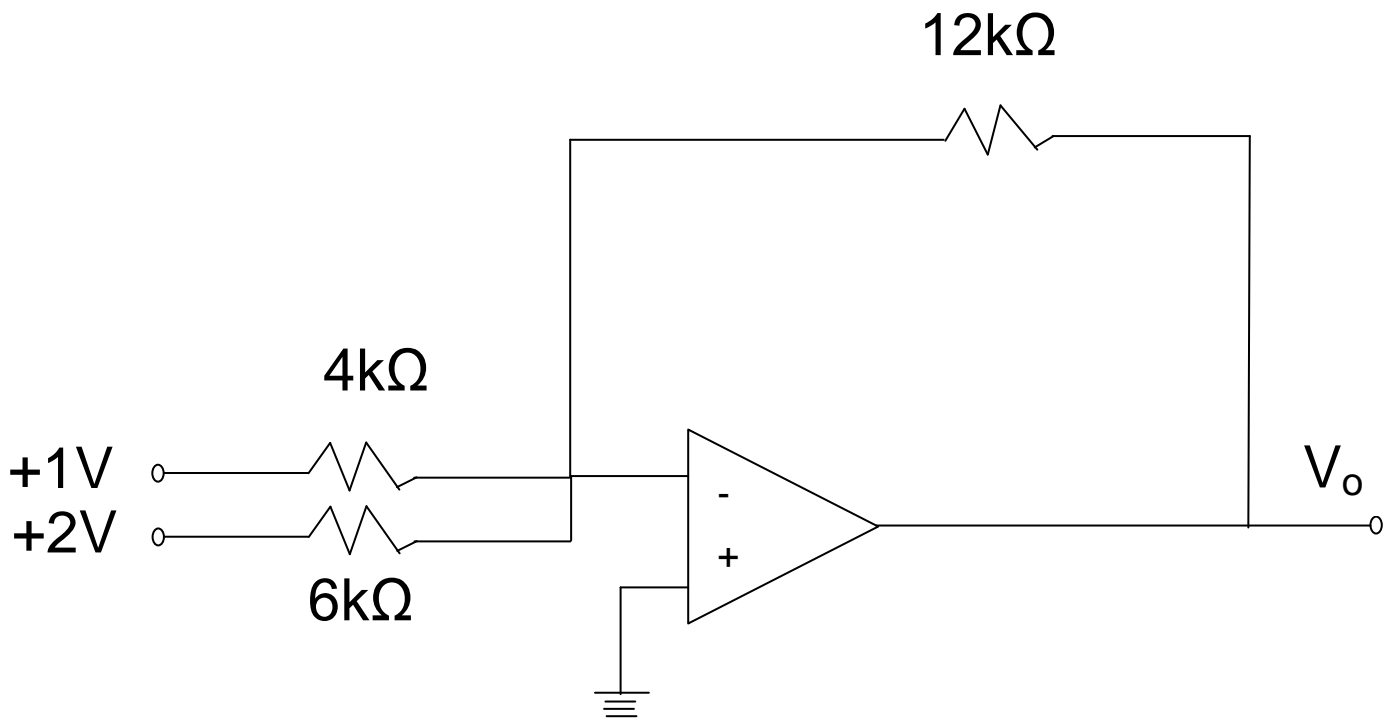7.5 In the circuit shown, the output voltage,  $V_o$ , is




- (a) + 3V
- (b) - 3V
- (c) - 7V
- (d) + 7V

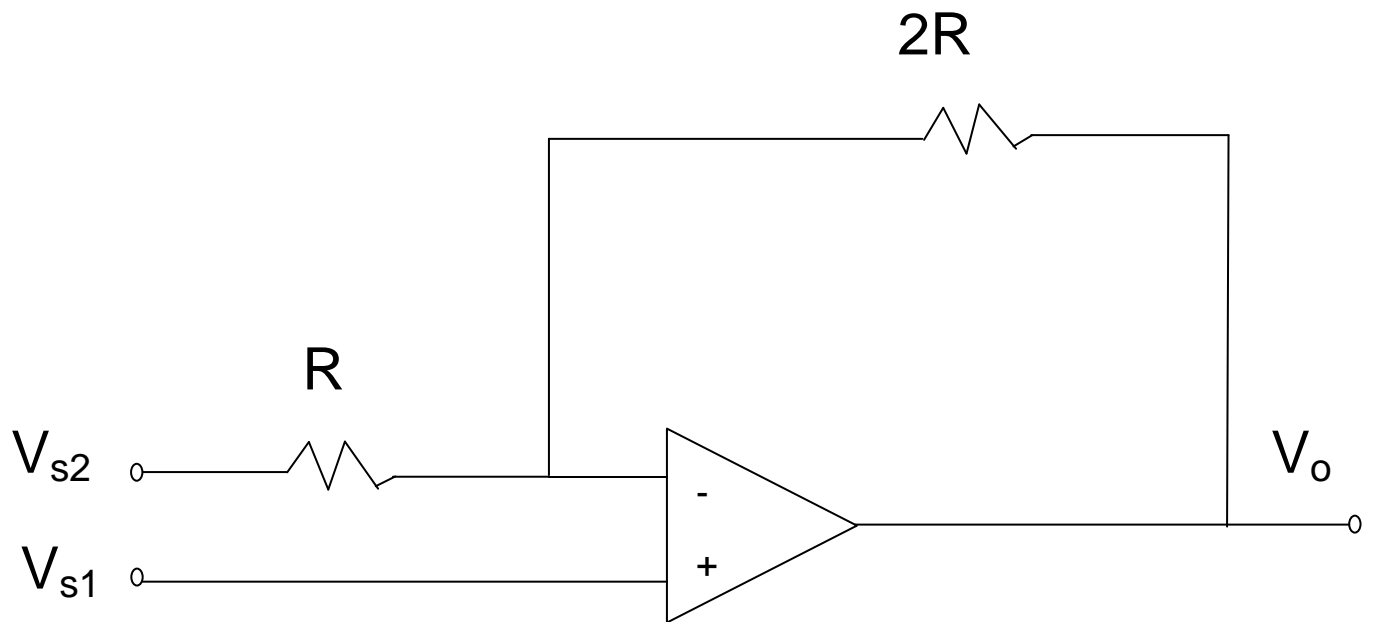7.6 In the op-amp circuit shown, the voltage  $V_o$  is,



- (a)  $3 V_{s1} - 6 V_{s2}$
- (b)  $2 V_{s1} - 3 V_{s2}$
- (c)  $2 V_{s1} - 2 V_{s2}$
- (d)  $3 V_{s1} - 2 V_{s2}$

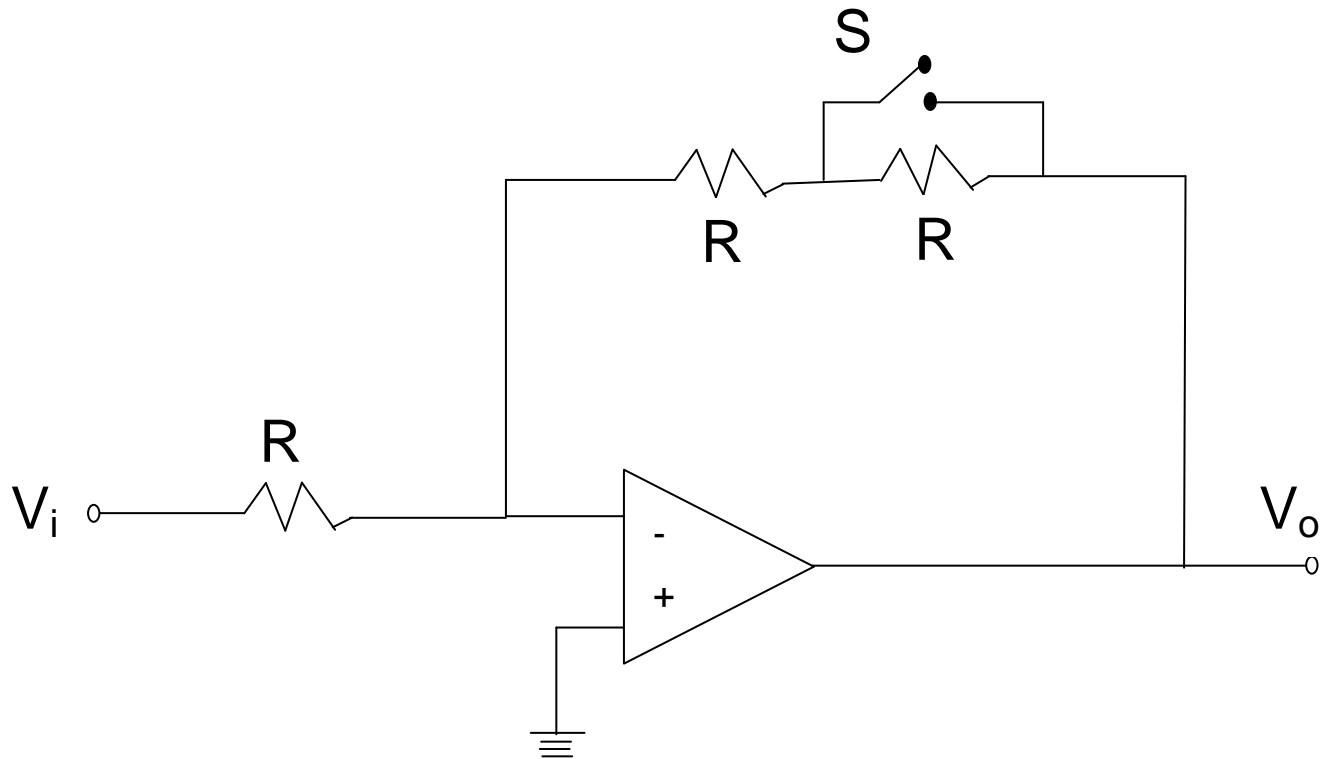7.7 Let the magnitude of the gain in the inverting op-amp amplifier circuit shown be  $x$  with switch  $S_1$  open, when the switch  $S_1$  is closed the magnitude of gain becomes



- (a)  $x/2$
- (b)  $-x$
- (c)  $2x$
- (d)  $-2x$

7.8 A differential amplifier has a differential gain of 2000 and a common mode gain of 0.2. The CMRR in dB is equal to

- (a) 10000
- (b) 400
- (c) 80
- (d) 40

7.9 An op-amp is used in the circuit as shown. Current  $I_o$  is

- (a)  $V_s \times \frac{R_L}{R_s R_L + R_s}$
- (b)  $\frac{V_s}{R_s}$

(c)  $\frac{V_s}{R_L}$

(d)  $V_s \left( \frac{1}{R_s} + \frac{1}{R_L} \right)$

7.10 The slew rate of an op-amp is 0.5 V/ $\mu$ S. The maximum frequency of a sinusoidal input of 2V rms that can be handled without excessive distortion is

- (a) 3 kHz
- (b) 30 kHz
- (c) 200 kHz
- (d) 2 MHz

Answers:

7.1 (d), 7.2 (c) 7.3 (c) 7.4 (b) 7.5 (c) 7.6 (d) 7.7 (a)

7.8 (c) 7.9 (b) 7.10 (b)